

# Elaborato di Architettura dei Sistemi di Elaborazione

## Gruppo 21

Alessandro Placido Luise - Mat. M63/818      Giuseppina Tuoro - Mat. M63/811

18 gennaio 2020

# Indice

<b>1</b>	<b>Esercizio 1</b>	<b>1</b>
1.1	Traccia . . . . .	1
1.2	Soluzione . . . . .	1
1.2.1	Schematici . . . . .	2
1.2.2	Codice . . . . .	3
1.2.2.1	Multiplexer 2:1 . . . . .	3
1.2.2.2	Multiplexer 4:1 . . . . .	4
1.2.2.3	Multiplexer 8:1 . . . . .	4
1.3	Simulazione . . . . .	6
<b>2</b>	<b>Esercizio 2</b>	<b>8</b>
2.1	Traccia . . . . .	8
2.2	Soluzione . . . . .	8
2.2.1	Schematici . . . . .	8
2.2.2	Codice . . . . .	9
2.2.2.1	Display 7 Segmenti . . . . .	9
2.2.2.2	Anodes Manager . . . . .	11
2.2.2.3	Cathodes manager . . . . .	12
2.2.2.4	Counter . . . . .	14
2.2.2.5	Clock Filter . . . . .	15
2.2.3	File UCF . . . . .	16
<b>3</b>	<b>Esercizio 3</b>	<b>17</b>
3.1	Traccia . . . . .	17
3.2	Flip Flop D Edge Triggered - Prof. Mazzeo . . . . .	17
3.2.1	Schematici . . . . .	18
3.2.2	Codice . . . . .	19
3.2.2.1	Flip Flop D Edge Triggered sul fronte di discesa . . . . .	19
3.2.2.2	Flip Flop D Edge Triggered sul fronte di salita . . . . .	21
3.3	Simulazione . . . . .	23
3.3.0.1	TestBench Flip Flop Edge Triggered . . . . .	23
3.4	Flip Flop D Edge Triggered - Prof. Sami . . . . .	24
3.4.1	Schematici . . . . .	25
3.4.2	Codice . . . . .	25
3.4.2.1	Flip Flop D Edge Triggered sul fronte di salita . . . . .	25
3.4.2.2	Flip Flop D Edge Triggered sul fronte di discesa . . . . .	27

3.5	Simulazione . . . . .	29
3.6	Flip Flop D Master Slave - Prof. Antonino Mazzeo . . . . .	31
3.6.1	Schematici . . . . .	32
3.6.2	Codice . . . . .	32
3.7	Simulazione . . . . .	35
3.8	Flip Flop D Master Slave - Prof. Sami . . . . .	36
3.8.1	Schematici . . . . .	37
3.8.2	Codice . . . . .	37
3.9	Simulazione . . . . .	39
<b>4</b>	<b>Esercizio 4</b>	<b>41</b>
4.1	Traccia . . . . .	41
4.2	Soluzione . . . . .	41
4.2.1	Schematici . . . . .	42
4.2.2	Codice . . . . .	44
4.2.2.1	Ripple Carry Adder 8 bit . . . . .	44
4.2.2.2	Ripple Carry Adder 4 bit . . . . .	46
4.2.2.3	Full Adder . . . . .	47
4.2.2.4	Half Adder . . . . .	48
4.3	Simulazione . . . . .	49
4.4	Sintesi su board FPGA . . . . .	52
4.4.1	File UCF . . . . .	52
4.4.2	Sintesi finale . . . . .	53
<b>5</b>	<b>Esercizio 5</b>	<b>57</b>
5.1	Traccia . . . . .	57
5.2	Soluzione . . . . .	57
5.2.1	Schematici . . . . .	58
5.2.2	Codice . . . . .	58
5.2.2.1	Registro a scorrimento circolare . . . . .	58
5.2.2.2	FFD sul fronte di discesa con reset . . . . .	61
5.3	Simulazione . . . . .	63
5.3.0.1	Test 1 . . . . .	65
5.3.0.2	Test 2 . . . . .	66
5.3.0.3	Test 3 . . . . .	66
5.4	Sintesi su board FPGA . . . . .	66
5.4.0.1	Debouncer . . . . .	69
5.4.0.2	File UCF . . . . .	71
<b>6</b>	<b>Esercizio 6</b>	<b>72</b>
6.1	Traccia . . . . .	72
6.2	Soluzione . . . . .	72
6.2.1	Schematici . . . . .	73
6.2.1.1	Flip Flop T . . . . .	73

6.2.1.2	Contatore Parallelo Mod-16	74
6.2.1.3	Contatore Seriale Mod-16	75
6.2.2	Codice	76
6.2.2.1	Flip Flop T	76
6.2.2.2	Contatore Parallelo Mod-16	77
6.2.2.3	Contatore in serie Mod-16	79
6.3	Simulazione	80
6.3.0.1	Test Contatore Parallelo	82
6.3.0.2	Test Contatore Serie	82
6.4	Sintesi su board FPGA	82
6.4.1	Bin2bcd	82
6.4.2	Sintesi finale	83
6.4.3	File UCF	86
<b>7</b>	<b>Esercizio 7</b>	<b>88</b>
7.1	Traccia	88
7.2	Soluzione	88
7.2.1	Schematici	89
7.2.2	Codice	90
7.2.2.1	Arbitro 2 su 3	90
7.3	Simulazione	91
7.4	Sintesi su board FPGA	93
<b>8</b>	<b>Esercizio 8</b>	<b>94</b>
8.1	Traccia	94
8.2	Soluzione e sintesi	94
8.2.1	Schematici	95
8.2.2	Codice	95
8.2.2.1	Orologio	95
8.2.2.2	Contatore	97
8.2.2.3	Orologio FPGA	99
8.2.2.4	Clock Divider	103
8.2.2.5	Test UCF	104
8.3	Simulazione	105
<b>9</b>	<b>Esercizio 9</b>	<b>109</b>
9.1	Traccia	109
9.2	Soluzione	109
9.2.1	Schematici	110
9.2.2	Codice	111
9.2.2.1	Carry Save Adder	111
9.3	Simulazione	114
9.4	Sintesi su board FPGA	116
9.4.1	File UCF	118

<b>10 Esercizio 10</b>	<b>120</b>
10.1 Traccia . . . . .	120
10.2 Soluzione . . . . .	120
10.2.1 Schematici . . . . .	122
10.2.2 Codice . . . . .	123
10.2.2.1 Moltiplicatore di Robertson . . . . .	123
10.2.2.2 PC . . . . .	126
10.2.2.3 Registro . . . . .	129
10.2.2.4 Mux Bus . . . . .	130
10.2.2.5 Adder - Subtractor . . . . .	131
10.3 Simulazione . . . . .	133
10.4 Sintesi su board FPGA . . . . .	136
10.4.1 Sintesi Robertson . . . . .	136
10.4.2 File UCF . . . . .	138
<b>11 Esercizio 11</b>	<b>140</b>
11.1 Traccia . . . . .	140
11.2 UART RS232 . . . . .	140
11.2.1 Schematici . . . . .	143
11.2.2 Codice . . . . .	143
11.2.2.1 RS232RefComp2 . . . . .	143
11.3 Soluzione a) Uart Tappo . . . . .	160
11.3.1 Schematici . . . . .	160
11.3.2 Codice . . . . .	160
11.3.2.1 UART Tappo . . . . .	160
11.4 Sintesi su board FPGA . . . . .	162
11.5 Soluzione b) 2 UART . . . . .	163
11.5.1 Schematici . . . . .	163
11.5.2 Codice . . . . .	164
11.5.2.1 2UART . . . . .	164
11.6 Sintesi su board FPGA . . . . .	165
11.7 Soluzione c) UART_PC (facoltativo) . . . . .	166
11.7.1 Schematici . . . . .	168
11.7.2 Codice . . . . .	169
11.7.2.1 UART_PC . . . . .	169
11.7.2.2 File UCF . . . . .	171
<b>12 Esercizio 12</b>	<b>173</b>
12.1 Traccia . . . . .	173
12.2 Soluzione a) . . . . .	173
12.2.1 Schematici . . . . .	175
12.2.2 Codice . . . . .	176
12.3 Simulazione . . . . .	177
12.4 Soluzione b) IADD modificata . . . . .	180
12.4.1 Schematici . . . . .	181

12.4.2 Codice . . . . .	181
12.5 Simulazione . . . . .	186
12.6 Soluzione b) ISUB modificata . . . . .	187
12.6.1 Codice . . . . .	187
12.7 Simulazione . . . . .	197
<b>13 Esercizio 13</b>	<b>200</b>
13.1 Traccia . . . . .	200
13.2 Soluzione . . . . .	200
13.2.1 Schematici . . . . .	202
13.2.2 Codice . . . . .	203
13.2.2.1 OmegaNetwork . . . . .	203
13.2.2.2 PO (Parte Operativa) . . . . .	205
13.2.2.3 Switch . . . . .	207
13.2.2.4 Demultiplexer 1:2 . . . . .	208
13.2.2.5 PC (Parte di Controllo) . . . . .	209
13.2.2.6 Arbiter . . . . .	210
13.2.2.7 Demultiplexer 1:4 . . . . .	211
13.3 Simulazione . . . . .	212
13.3.1 Codice . . . . .	212
13.3.2 Risultati . . . . .	214
13.4 Sintesi su board FPGA . . . . .	215
13.4.1 File UCF . . . . .	219

# Capitolo 1


## Esercizio 1

### 1.1 Traccia

Progettare ed implementare in VHDL un multiplexer 8:1 indirizzabile utilizzando una descrizione di tipo structural che componga opportunamente multiplexer più piccoli. Nota: il progetto deve fare uso di almeno un multiplexer 4:1, progettato con una tecnica a scelta dello studente.

 
### 1.2 Soluzione

Si è scelto di implementare il multiplexer 8:1 utilizzando due multiplexer 4:1 e uno 2:1 collegati in cascata. Lo schema è riportato nell'immagine seguente :




Il multiplexer da 8 è stato implementato utilizzando una descrizione strutturale, mentre per gli altri è stata utilizzata una descrizione di tipo DataFlow.

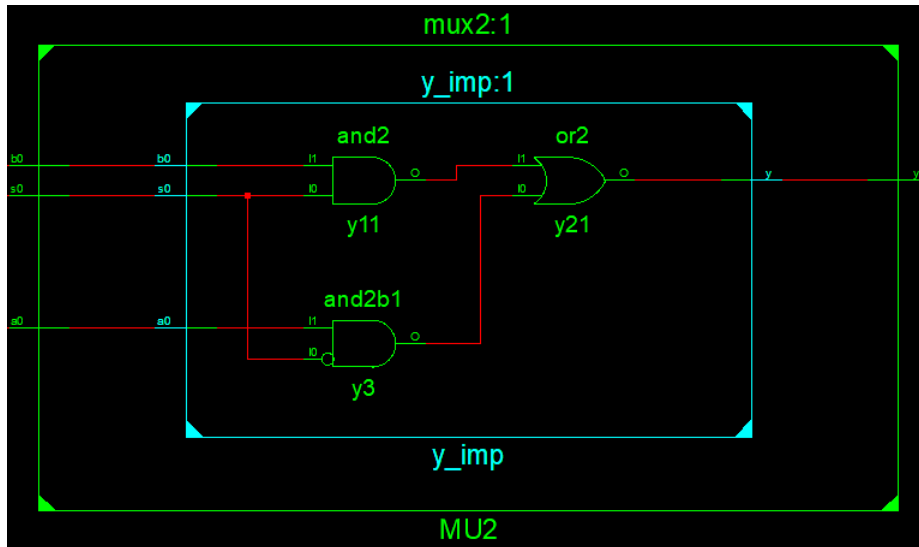Di seguito è mostrato lo schematico del multiplexer 2:1 implementato.




 
Il multiplexer 4:1 è stato sviluppato seguendo la stessa logica DataFlow.


  
### 1.2.1 Schematici

Lo schematico del mux 8:1 che ne segue è composizione dei due visti precedentemente.





## 1.2.2 Codice

### 1.2.2.1 Multiplexer 2:1

Il Mux 2:1 pone l'uscita pari ad a0 se s0 è pari a 0, a b0 se s0 è pari ad 1. In tutti gli altri casi l'uscita è un "don't care".

```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity mux2 is
5     PORT (
6         s0 : in  std_logic;
```

```

7      a0,b0: in  std_logic;
8      y : out std_logic
9      );
10 end mux2;
11
12 architecture DataFlow of mux2 is
13 begin
14 y<=  a0 when (s0 = '0') else
15      b0 when (s0 = '1') else
16      '-';
17 end DataFlow;

```

Codice Componente 1.1: Definizione del componente Bit String Comparator Generic

### 1.2.2.2 Multiplexer 4:1

Discorso simile per il Mux 4:1, che possiede invece un segnale di selezione a 2 bit.

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity mux4 is
5  PORT (
6      S1 : in  std_logic_vector(1 downto 0);
7      D1 : in  std_logic_vector(3 downto 0);
8      y : out std_logic );
9  end mux4;
10
11 architecture DataFlow of mux4 is
12 begin
13 y <= D1(0)  when S1 = "00" else
14      D1(1)  when S1 = "01" else
15      D1(2)  when S1 = "10" else
16      D1(3)  when S1 = "11" else
17      '-';
18 end DataFlow;

```

Codice Componente 1.2: Definizione del componente Bit String Comparator Generic

### 1.2.2.3 Multiplexer 8:1

Il Mux 8:1 viene descritto con una logica strutturale, come richiesto dalla traccia, ed utilizzando almeno un Mux 4:1.

```

1
2  library IEEE;
3  use IEEE.STD_LOGIC_1164.ALL;
4
5  entity Mux8 is
6  PORT (

```

```

7      S : in  std_logic_vector(2 downto 0);
8      D : in  std_logic_vector(7 downto 0);
9      y : out std_logic
10     );
11 end Mux8;
12
13 architecture Structural of Mux8 is
14
15 Component mux4
16   PORT (
17     S1 : in  std_logic_vector(1 downto 0);
18     D1 : in  std_logic_vector(3 downto 0);
19     y : out std_logic );
20 end Component;
21
22 Component mux2
23   PORT (
24     s0 : in  std_logic;
25     a0,b0: in  std_logic;
26     y : out std_logic );
27 end Component;
28
29 signal c0, c1 : std_logic := '0';
30
31 begin
32
33 MU4_1 : mux4 port map (
34   D1(0) => D(0),
35   D1(1) => D(1),
36   D1(2) => D(2),
37   D1(3) => D(3),
38   S1(0) => S(1),
39   S1(1) => S(0),
40   y  => c0
41 );
42 MU4_2 : mux4 port map (
43   D1(0) => D(4),
44   D1(1) => D(5),
45   D1(2) => D(6),
46   D1(3) => D(7),
47   S1(0) => S(1),
48   S1(1) => S(0),
49   y  => c1
50 );
51 MU2 : mux2 port map (
52   a0 => c0,
53   b0 => c1,
54   s0 => S(2),
55   y  => y

```

```

56     );
57
58 end Structural;

```

Codice Componente 1.3: Definizione del componente Bit String Comparator Generic

## 1.3 Simulazione

Nel seguente testbench il multiplexer prende in ingresso la stringa D di 8 bit. Ciò ci permette di osservare, al variare del segnale di selezione S, tutti i possibili valori di uscita y.


```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3  ENTITY test_mux IS
4  END test_mux;
5
6  ARCHITECTURE behavior OF test_mux IS
7
8  COMPONENT Mux8
9  PORT (
10     S : IN  std_logic_vector(2 downto 0);
11     D : IN  std_logic_vector(7 downto 0);
12     y : OUT std_logic
13 );
14 END COMPONENT;
15
16 --Inputs
17 signal S : std_logic_vector(2 downto 0) := (others => '0');
18 signal D : std_logic_vector(7 downto 0) := (others => '0');
19 --Outputs
20 signal y : std_logic;
21
22 BEGIN
23     uut: Mux8 PORT MAP ( S => S, D => D, y => y );
24
25     stim_proc: process
26     begin
27         wait for 100 ns;
28         D <= "11101001";
29         S <= "000";
30         wait for 100 ns;
31         S <= "001";
32         wait for 50 ns;
33         S <= "010";
34         wait for 50 ns;
35         S <= "011";
36         wait for 50 ns;
37         S <= "100";

```

```
38 wait for 50 ns;  
39 S <= "101";  
40 wait for 50 ns;  
41 S <= "110";  
42 wait for 50 ns;  
43 S <= "111";  
44 wait for 50 ns;  
45 wait;  
46 end process;  
47  
48 END;
```

 La simulazione ISim mostra che il multiplexer seleziona correttamente i valori di output, al variare del segnale di selezione, per la stringa data 11101001.



# Capitolo 2


## Esercizio 2

### 2.1 Traccia

Progettare un controller per un display a 7 segmenti che, data una stringa in ingresso di 4 bit che codifica un numero naturale fra 0 e 15, fornisca in uscita i segnali a,b,c,d,e,f,g (in figura) che consentono di rappresentare sul display il numero fornito in ingresso rappresentato nella codifica esadecimale (cifre 0..9 A.. F). Il controller deve essere sintetizzato sulla board e deve utilizzare gli switch per acquisire l'input e una cifra delle 4 disponibili per visualizzare l'output.


 
### 2.2 Soluzione

Il componente implementato consente di visualizzare su display a 7 segmenti, lettere e numeri che vanno da 0 a 9 e dalla A alla F.


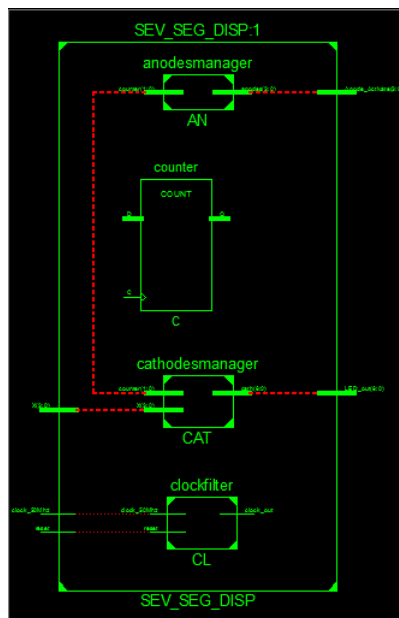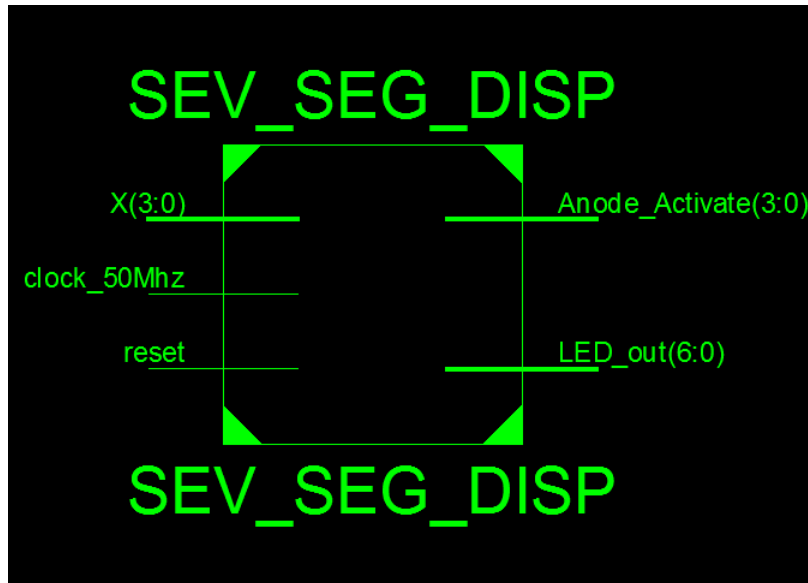
#### 2.2.1 Schematici

La macchina prende in ingresso il dato su 4 bit da visualizzare, il clock e un segnale di reset. In uscita ci sono i bit relativi agli anodi e ai catodi da accendere.



## 2.2.2 Codice

Il display è formato da diversi componenti principali : un gestore degli anodi, uno dei catodi, un clock filter e un contatore.

### 2.2.2.1 Display 7 Segmenti

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4 use IEEE.std_logic_unsigned.all;
5
6
```

```

7 entity SEV_SEG_DISP is
8     Port ( clock_50Mhz : in STD_LOGIC;
9           reset : in STD_LOGIC;
10          X: in STD_LOGIC_VECTOR (3 downto 0);
11          Anode_Activate : out STD_LOGIC_VECTOR (3 downto 0);
12          LED_out : out STD_LOGIC_VECTOR (6 downto 0)
13          );
14
15 end SEV_SEG_DISP;
16 architecture Behavioral of SEV_SEG_DISP is
17
18 Component counter
19 port (
20     clockfx,reset: in std_logic;
21     counter: out std_logic_vector(1 downto 0)
22 );
23 end component;
24
25
26 Component clockfilter
27 port (
28     clock_50Mhz : in STD_LOGIC;
29     reset : in STD_LOGIC;
30     clock_out:out std_logic
31 );
32 );
33 end component;
34
35 Component anodesmanager
36 port (
37     counter: in std_logic_vector(1 downto 0);
38     anodes: out STD_LOGIC_VECTOR (3 downto 0)
39 );
40 );
41 );
42 end component;
43
44
45 Component cathodesmanager
46 port (
47     counter:in std_logic_vector(1 downto 0);
48     X: in STD_LOGIC_VECTOR (3 downto 0);
49     cath : out STD_LOGIC_VECTOR (6 downto 0)
50 );
51 );
52 end component;
53
54 signal clk: std_logic:='0';
55 signal count: std_logic_vector(1 downto 0):=(others=>'0');

```



```

56
57 begin
58
59 C: counter port map(
60     clockfx=>clk,
61     reset=>reset,
62     counter=>count
63
64 );
65
66
67 AN: anodesmanager port map(
68
69     counter=>count,
70     anodes=>Anode_Activate
71
72 );
73
74
75
76 CAT: cathodesmanager port map(
77     counter=>count,
78     X=>X,
79     cath=> LED_out
80 );
81
82
83
84 CL: clockfilter port map(
85     clock_50Mhz=>clock_50Mhz,
86     reset=>reset,
87     clock_out=>clk
88
89 );
90
91
92 end Behavioral;

```

Codice Componente 2.1: Definizione del Display a 7 segmenti

### 2.2.2.2 Anodes Manager

Il ruolo del gestore degli anodi è quello di alternare l'attivazione dei 4 anodi disponibili tramite l'analisi dell'ingresso counter (corrispondente all'uscita del contatore). Tale compito è svolto dal process, che nel caso di valori differenti dai precedenti pone l'ingresso degli anodi a "1111".

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;

```

```

4
5 entity anodesmanager is
6 port (
7     counter: in std_logic_vector(1 downto 0);
8     anodes: out STD_LOGIC_VECTOR (3 downto 0)
9 );
10 end anodesmanager;
11
12 architecture Behavioral of anodesmanager is
13
14 signal Anode_Activate: STD_LOGIC_VECTOR (3 downto 0) := (others=>'0');
15
16 begin
17
18
19
20 process(counter)
21 begin
22     case counter is
23     when "00" =>
24         Anode_Activate <= "0111";
25     when "01" =>
26         Anode_Activate <= "1011";
27     when "10" =>
28         Anode_Activate <= "1101";
29     when "11" =>
30         Anode_Activate <= "1110";
31     when others =>
32         Anode_Activate <= (others => '1');
33     end case;
34 end process;
35
36
37 anodes<= Anode_Activate;
38
39 end Behavioral;

```

Codice Componente 2.2: Definizione di Anodes Manager

### 2.2.2.3 Cathodes manager

Mentre il gestore degli anodi tiene attivi questi ultimi secondo la frequenza dettata dal contatore, il gestore dei catodi pone il valore dei bit in ingresso in LED\_BCD. Inoltre controlla che, in base al valore di quest'ultimo, venga inserita la giusta combinazione di led accesi/spenti che consenta di visualizzare il dato corretto.

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;

```

```

4
5 entity cathodesmanager is
6 port (
7     counter:in STD_LOGIC_VECTOR (1 downto 0);
8     X: in STD_LOGIC_VECTOR (3 downto 0);
9     cath : out STD_LOGIC_VECTOR (6 downto 0)
10 );
11 end cathodesmanager;
12
13 architecture Behavioral of cathodesmanager is
14
15 signal LED_BCD: STD_LOGIC_VECTOR (3 downto 0) := (others=>'0');
16 signal LED_out: STD_LOGIC_VECTOR (6 downto 0) := (others=>'0');
17 signal displayed_number: STD_LOGIC_VECTOR (15 downto 0) := (others=>'0');
18 constant zero: STD_LOGIC_VECTOR (11 downto 0) := (others=>'0');
19
20 begin
21
22 process(counter,displayed_number)
23 begin
24     case counter is
25     when "00" =>
26         LED_BCD <= displayed_number(15 downto 12);
27     when "01" =>
28         LED_BCD <= displayed_number(11 downto 8);
29     when "10" =>
30         LED_BCD <= displayed_number(7 downto 4);
31     when "11" =>
32         LED_BCD <= displayed_number(3 downto 0);
33     when others =>
34         LED_BCD <= (others => '1');
35     end case;
36 end process;
37
38 displayed_number<= zero & X;
39
40
41
42 process(LED_BCD)
43 begin
44     case LED_BCD is
45     when "0000" => LED_out <= "0000001"; -- "0"
46     when "0001" => LED_out <= "1001111"; -- "1"
47     when "0010" => LED_out <= "0010010"; -- "2"
48     when "0011" => LED_out <= "0000110"; -- "3"
49     when "0100" => LED_out <= "1001100"; -- "4"
50     when "0101" => LED_out <= "0100100"; -- "5"
51     when "0110" => LED_out <= "0100000"; -- "6"
52     when "0111" => LED_out <= "0001111"; -- "7"

```

```

53   when "1000" => LED_out <= "0000000"; -- "8"
54   when "1001" => LED_out <= "0000100"; -- "9"
55   when "1010" => LED_out <= "0001000"; -- A
56   when "1011" => LED_out <= "1100000"; -- b
57   when "1100" => LED_out <= "0110001"; -- C
58   when "1101" => LED_out <= "1000010"; -- d
59   when "1110" => LED_out <= "0110000"; -- E
60   when "1111" => LED_out <= "0111000"; -- F
61   when others => LED_out <= "1111111";
62   end case;
63 end process;
64
65 cath<=LED_out;
66
67 end Behavioral;

```

Codice Componente 2.3: Definizione di Cathodes Manager

#### 2.2.2.4 Counter

Il contatore permette di incrementare il segnale di uscita (counter) di 1, sul fronte di salita del clock clockfx. Il reset pone il contatore a 0.

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5
6  entity counter is
7  port(
8      clockfx,reset: in std_logic;
9      counter: out std_logic_vector(1 downto 0) -- 2 bit contatore mod 4
10 );
11 end counter;
12
13 architecture Behavioral of counter is
14
15 signal c: std_logic_vector(1 downto 0):=(others=>'0');
16
17 begin
18
19
20 process(clockfx,reset)
21 begin
22     if(reset='1') then
23         c <= (others => '0');
24     elsif(rising_edge(clockfx)) then
25         c <= std_logic_vector(unsigned(c) + 1);
26     end if;

```

```

27 end process;
28
29 counter<=c;
30
31 end Behavioral;

```

Codice Componente 2.4: Definizione del contatore

### 2.2.2.5 Clock Filter

Il clock filter permette di ridurre la frequenza del clock in ingresso. In questo caso abbiamo ottenuto in uscita un clock di 50 kHz.

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4
5 entity clockfilter is
6 port (
7     clock_50Mhz : in STD_LOGIC;
8     reset       : in STD_LOGIC;
9     clock_out:out std_logic
10
11 );
12 end clockfilter;
13
14 architecture Behavioral of clockfilter is
15
16 signal clockfx: std_logic:='0';
17
18 begin
19
20 clkfilter: process(clock_50Mhz, reset)
21 variable counter : integer := 1;
22 begin
23
24 if (reset = '1') then
25     counter := 1;
26     clockfx <= '0';
27 elsif(rising_edge(clock_50Mhz)) then
28     if (counter = 1000) then
29         clockfx <= not clockfx;
30         counter := 1;
31     else
32         counter := counter + 1;
33     end if;
34
35 end if;
36

```

```

37 end process;
38
39 clock_out<=clockfx;
40
41 end Behavioral;

```

Codice Componente 2.5: Definizione del Clock Filter

### 2.2.3 File UCF

Il file ucf utilizzato per la sintesi sull'FPGA Nexys 2 è riportato di seguito.

```

1
2 NET "LED_out<6>" LOC = "L18"; # Bank = 1, Pin name = IO_L10P_1, Type = I/O,
  Sch name = CA
3 NET "LED_out<5>" LOC = "F18"; # Bank = 1, Pin name = IO_L19P_1, Type = I/O,
  Sch name = CB
4 NET "LED_out<4>" LOC = "D17"; # Bank = 1, Pin name = IO_L23P_1/HDC, Type =
  DUAL, Sch name = CC
5 NET "LED_out<3>" LOC = "D16"; # Bank = 1, Pin name = IO_L23N_1/LDC0, Type =
  DUAL, Sch name = CD
6 NET "LED_out<2>" LOC = "G14"; # Bank = 1, Pin name = IO_L20P_1, Type = I/O,
  Sch name = CE
7 NET "LED_out<1>" LOC = "J17"; # Bank = 1, Pin name = IO_L13P_1/A6/RHCLK4/
  IRDY1, Type = RHCLK/DUAL, Sch name = CF
8 NET "LED_out<0>" LOC = "H14"; # Bank = 1, Pin name = IO_L17P_1, Type = I/O,
  Sch name = CG
9
10 NET "clock_50Mhz" LOC = "B8"; # Bank = 0, Pin name = IP_L13P_0/GCLK8, Type
  = GCLK, Sch name = GCLK0
11 NET "Anode_Activate<0>" LOC = "F17"; # Bank = 1, Pin name = IO_L19N_1, Type
  = I/O, Sch name = AN0
12 NET "Anode_Activate<1>" LOC = "H17"; # Bank = 1, Pin name = IO_L16N_1/A0,
  Type = DUAL, Sch name = AN1
13 NET "Anode_Activate<2>" LOC = "C18"; # Bank = 1, Pin name = IO_L24P_1/LDC1,
  Type = DUAL, Sch name = AN2
14 NET "Anode_Activate<3>" LOC = "F15"; # Bank = 1, Pin name = IO_L21P_1, Type
  = I/O, Sch name = AN3
15
16 NET "X<0>" LOC = "G18"; # Sch name = SW0
17 NET "X<1>" LOC = "H18"; # Sch name = SW1
18 NET "X<2>" LOC = "K18"; # Sch name = SW2
19 NET "X<3>" LOC = "K17"; # Sch name = SW3

```

Codice Componente 2.6: ucf display a 7 segmenti

# Capitolo 3


## Esercizio 3

### 3.1 Traccia

Implementare in VHDL e simulare un Flip-flop D edge-triggered e master slave secondo i due differenti modelli visti a lezione (Mazzeo e Sami).
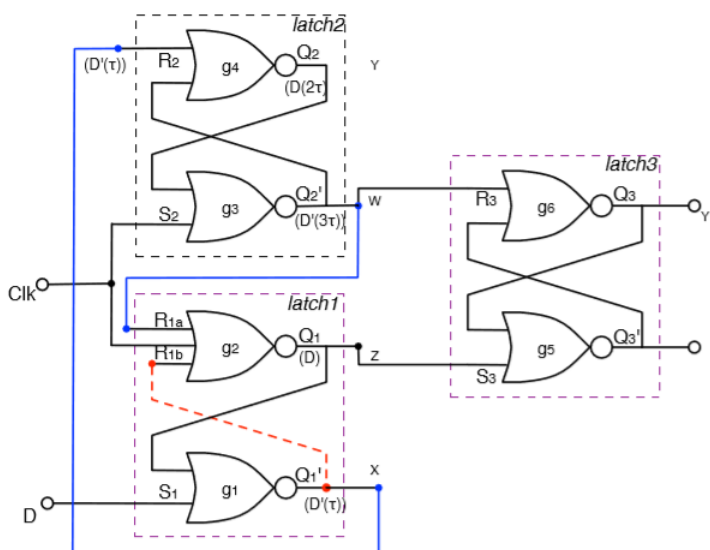
### 3.2 Flip Flop D Edge Triggered - Prof. Mazzeo


Il Flip Flop D Edge Triggered è un dispositivo bistabile con due ingressi (Dato e Clock) e due uscite (Q e Q negato). Il Flip Flop effettua una transizione di stato in corrispondenza del fronte di salita (o discesa) del segnale di Clock. Esso memorizza il dato ricevuto da D e fornisce attraverso l'uscita Q il dato stesso e attraverso Q negato il segnale invertito. Tale dispositivo è composto in questo caso da 3 Latch RS asincroni fondamentali, che possono essere realizzati sia con porte NAND (edge triggered attivo su fronte di salita) che con porte NOR (edge triggered attivo su fronte di discesa). Entrambe le soluzioni saranno mostrate.



L'immagine mostra il progetto di un Flip Flop D Edge Triggered sul fronte di discesa, realizzato mediante porte NOR. La NOR è una porta logica 0-attiva : presenta una uscita alta solo quando i suoi ingressi sono entrambi bassi, negli altri casi fornisce solo una uscita bassa.

A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

 Si riporta anche la versione del dispositivo su fronte di salita realizzato con porte NAND.




La porta NAND è 1-attiva. Essa ci consente di ottenere commutazione del dato sul fronte di salita del clock.

A	B	A NAND B
0	0	1
0	1	1
1	0	1
1	1	0

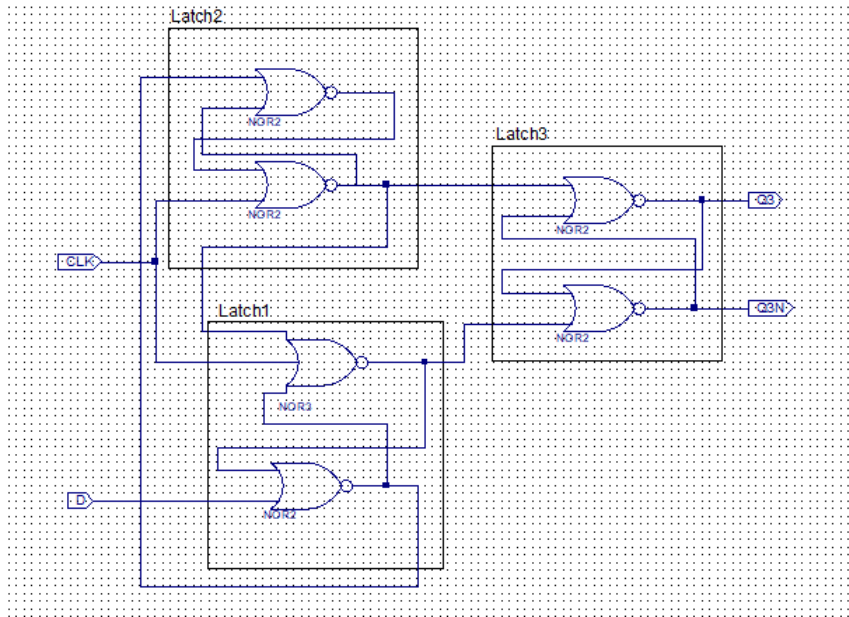
### 3.2.1 Schematici

Il flip flop edge triggered su fronte di discesa (così come quello su fronte di salita) è stato sviluppato col tool grafico di Xilinx ISE.





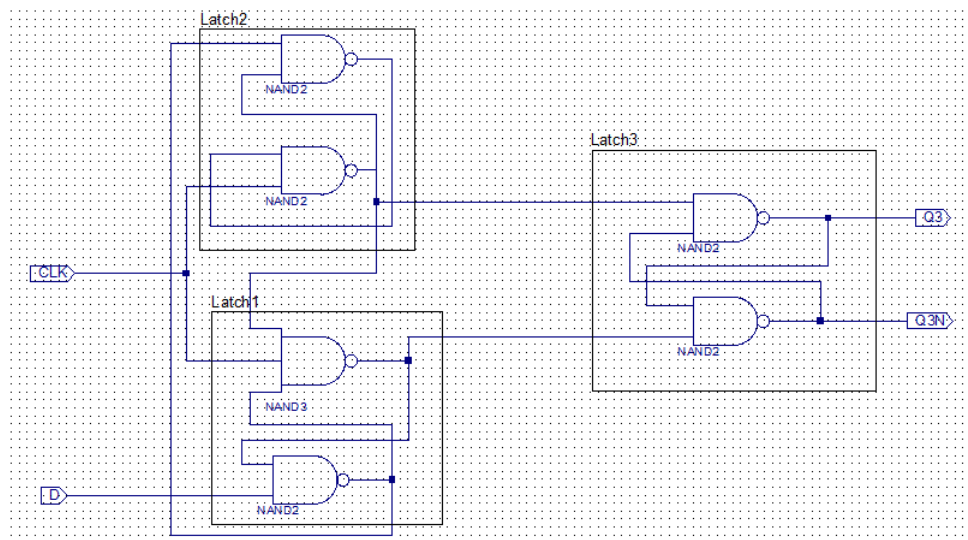Segue implementazione con porte NAND della sua versione sul fronte di salita:



### 3.2.2 Codice

Il codice HDL functional model è autogenerato da Xilinx ISE e implementa la soluzione utilizzando un approccio di tipo strutturale

#### 3.2.2.1 Flip Flop D Edge Triggered sul fronte di discesa

```

1
2 library ieee;
3 use ieee.std_logic_1164.ALL;
4 use ieee.numeric_std.ALL;
5 library UNISIM;

```

```

6 use UNISIM.Vcomponents.ALL;
7
8 entity FFD is
9     port ( CLK : in      std_logic;
10           D   : in      std_logic;
11           Q3  : out     std_logic;
12           Q3N : out     std_logic);
13 end FFD;
14
15 architecture BEHAVIORAL of FFD is
16     attribute BOX_TYPE : string ;
17     signal Q1          : std_logic;
18     signal Q1N         : std_logic;
19     signal Q2          : std_logic;
20     signal Q2N         : std_logic;
21     signal Q3_DUMMY    : std_logic;
22     signal Q3N_DUMMY   : std_logic;
23
24 component NOR2
25     port (
26         I0 : in      std_logic;
27         I1 : in      std_logic;
28         O  : out     std_logic);
29 end component;
30
31 attribute BOX_TYPE of NOR2 : component is "BLACK_BOX";
32 component NOR3 port (
33     I0 : in      std_logic;
34     I1 : in      std_logic;
35     I2 : in      std_logic;
36     O  : out     std_logic);
37 end component;
38
39 attribute BOX_TYPE of NOR3 : component is "BLACK_BOX";
40 begin
41 Q3 <= Q3_DUMMY;
42 Q3N <= Q3N_DUMMY;
43
44 g1 : NOR2
45     port map (I0=>D,
46               I1=>Q1,
47               O=>Q1N);
48 g2 : NOR3
49     port map (I0=>Q1N,
50               I1=>CLK,
51               I2=>Q2N,
52               O=>Q1);
53 g3 : NOR2
54     port map (I0=>CLK,

```

```

55         I1=>Q2,
56         O=>Q2N);
57     g4 : NOR2
58     port map (I0=>Q2N,
59               I1=>Q1N,
60               O=>Q2);
61     g5 : NOR2
62     port map (I0=>Q1,
63               I1=>Q3_DUMMY,
64               O=>Q3N_DUMMY);
65     g6 : NOR2
66     port map (I0=>Q3N_DUMMY,
67               I1=>Q2N,
68               O=>Q3_DUMMY);
69
70
71 end BEHAVIORAL;

```

Codice Componente 3.1: Definizione del Flip Flop D Edge Triggered sul fronte di discesa

### 3.2.2.2 Flip Flop D Edge Triggered sul fronte di salita

```

1
2 library ieee;
3 use ieee.std_logic_1164.ALL;
4 use ieee.numeric_std.ALL;
5 library UNISIM;
6 use UNISIM.Vcomponents.ALL;
7
8 entity FFDMazzeoFronteSalita is
9     port ( CLK : in    std_logic;
10           D   : in    std_logic;
11           Q3  : out   std_logic;
12           Q3N : out   std_logic);
13 end FFDMazzeoFronteSalita;
14
15 architecture BEHAVIORAL of FFDMazzeoFronteSalita is
16     attribute BOX_TYPE : string ;
17     signal Q1          : std_logic;
18     signal Q1N         : std_logic;
19     signal Q2          : std_logic;
20     signal Q2N         : std_logic;
21     signal Q3_DUMMY    : std_logic;
22     signal Q3N_DUMMY   : std_logic;
23
24     component NAND2
25     port ( I0 : in    std_logic;
26           I1 : in    std_logic;

```

```

27         O : out    std_logic);
28     end component;
29
30     attribute BOX_TYPE of NAND2 : component is "BLACK_BOX";
31     component NAND3
32     port ( I0 : in    std_logic;
33           I1 : in    std_logic;
34           I2 : in    std_logic;
35           O  : out    std_logic);
36     end component;
37
38     attribute BOX_TYPE of NAND3 : component is "BLACK_BOX";
39
40     begin
41     Q3 <= Q3_DUMMY;
42     Q3N <= Q3N_DUMMY;
43
44     g1 : NAND2
45         port map (I0=>D,
46                 I1=>Q1,
47                 O=>Q1N);
48     g2 : NAND3
49         port map (I0=>Q1N,
50                 I1=>CLK,
51                 I2=>Q2N,
52                 O=>Q1);
53     g3 : NAND2
54         port map (I0=>CLK,
55                 I1=>Q2,
56                 O=>Q2N);
57     g4 : NAND2
58         port map (I0=>Q2N,
59                 I1=>Q1N,
60                 O=>Q2);
61     g5 : NAND2
62         port map (I0=>Q1,
63                 I1=>Q3_DUMMY,
64                 O=>Q3N_DUMMY);
65     g6 : NAND2
66         port map (I0=>Q3N_DUMMY,
67                 I1=>Q2N,
68                 O=>Q3_DUMMY);
69
70
71 end BEHAVIORAL;

```

Codice Componente 3.2: Definizione del Flip Flop D Edge Triggered sul fronte di salita

## 3.3 Simulazione

### 3.3.0.1 TestBench Flip Flop Edge Triggered

Il seguente codice è valido per entrambe le implementazioni, dunque ne viene riportato solamente uno.

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3
4  ENTITY FFD_FFD_sch_tb1 IS
5  END FFD_FFD_sch_tb1;
6
7  ARCHITECTURE behavior OF FFD_FFD_sch_tb1 IS
8
9      COMPONENT FFD
10     PORT (
11         CLK : IN  std_logic;
12         D : IN  std_logic;
13         Q3 : OUT std_logic;
14         Q3N : OUT std_logic
15     );
16     END COMPONENT;
17
18     signal CLK : std_logic := '0';
19     signal D : std_logic := '0';
20
21     signal Q3 : std_logic;
22     signal Q3N : std_logic;
23
24     constant CLK_period : time := 10 ns;
25 BEGIN
26     uut: FFD PORT MAP (
27         CLK => CLK, D => D, Q3 => Q3, Q3N => Q3N );
28
29     CLK_process : process
30     begin
31         CLK <= '0';
32         wait for CLK_period/2;
33         CLK <= '1';
34         wait for CLK_period/2;
35     end process;
36
37     stim_proc: process
38
39     begin
40     wait for 20 ns;
41
42     D<= '0', '1' after 17 ns, '0' after 47 ns, '1' after 53 ns;
43     wait;

```


```

44
45     end process;
46 END;


```

Codice Componente 3.3: Definizione del testbench per ffd Mazzeo

 Nell'implementazione con le porte NOR, vediamo come l'uscita commuta soltanto in occasione del fronte di discesa del clock:




 Nell'implementazione con le porte NAND, vediamo come l'uscita commuta soltanto in occasione del fronte di salita del clock:


 
### 3.4 Flip Flop D Edge Triggered - Prof. Sami



Le dispense di Sami propongono un approccio differente da quelle del paragrafo precedente. Viene utilizzato un blocco di controllo direttamente connesso a un semplice Latch SR e si considera la derivata del segnale di clock, generando un impulso in corrispondenza del fronte di salita o di discesa.



Il latch SR verrà realizzato con porte NOR per il fronte di salita. Per simulare la transizione di stato sul fronte di discesa bisogna fare ulteriori accorgimenti : le due porte AND del blocco di sinistra devono essere sostituite con delle porte OR, mentre il Latch SR va realizzato con le porte NAND.
 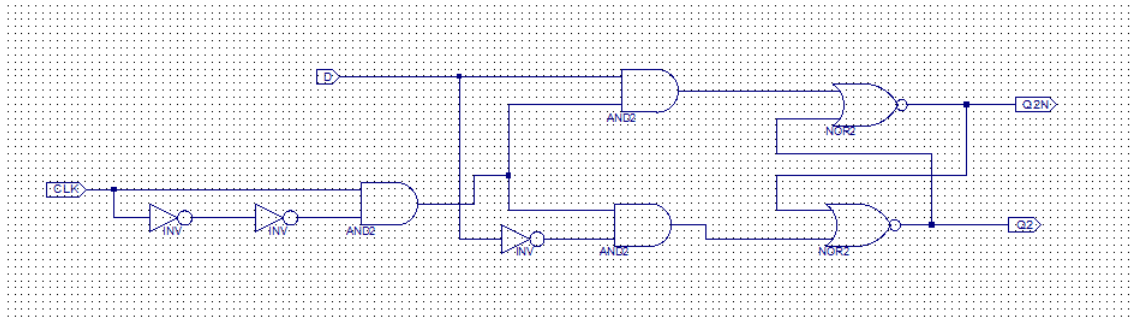
### 3.4.1 Schematici

Il primo schematico è relativo al flip flop D Edge triggered sul fronte di salita, mentre il secondo commuta sul fronte di discesa.



### 3.4.2 Codice

Il codice HDL functional model è autogenerato da Xilinx ISE e implementa la soluzione utilizzando un approccio di tipo strutturale.

#### 3.4.2.1 Flip Flop D Edge Triggered sul fronte di salita

```

1
2 library ieee;
3 use ieee.std_logic_1164.ALL;
4 use ieee.numeric_std.ALL;
5 library UNISIM;
6 use UNISIM.Vcomponents.ALL;
7
8 entity SamiFronteSalita is
9     port ( CLK : in    std_logic;
10           D   : in    std_logic;
11           Q2  : out   std_logic;
```

```

12         Q2N : out    std_logic);
13 end SamiFronteSalita;
14
15 architecture BEHAVIORAL of SamiFronteSalita is
16     attribute BOX_TYPE    : string ;
17     signal Q               : std_logic;
18     signal Q1              : std_logic;
19     signal XLXN_5          : std_logic;
20     signal XLXN_42         : std_logic;
21     signal XLXN_68         : std_logic;
22     signal XLXN_69         : std_logic;
23     signal Q2_DUMMY        : std_logic;
24     signal Q2N_DUMMY       : std_logic;
25
26     component AND2
27     port ( I0 : in        std_logic;
28           I1 : in        std_logic;
29           O  : out       std_logic);
30 end component;
31
32 attribute BOX_TYPE of AND2 : component is "BLACK_BOX";
33     component NOR2
34     port ( I0 : in        std_logic;
35           I1 : in        std_logic;
36           O  : out       std_logic);
37 end component;
38 attribute BOX_TYPE of NOR2 : component is "BLACK_BOX";
39
40     component INV
41     port ( I : in        std_logic;
42           O : out       std_logic);
43 end component;
44
45 attribute BOX_TYPE of INV : component is "BLACK_BOX";
46 begin
47
48     Q2 <= Q2_DUMMY;
49     Q2N <= Q2N_DUMMY;
50
51     a1 : AND2
52     port map (I0=>XLXN_69,
53              I1=>CLK,
54              O=>XLXN_42);
55     a2 : AND2
56     port map (I0=>XLXN_5,
57              I1=>XLXN_42,
58              O=>Q1);
59     a3 : AND2
60     port map (I0=>XLXN_42,

```



```

61         I1=>D,
62         O=>Q);
63     g2 : NOR2
64     port map (I0=>Q1,
65               I1=>Q2N_DUMMY,
66               O=>Q2_DUMMY);
67     g3 : NOR2
68     port map (I0=>Q2_DUMMY,
69               I1=>Q,
70               O=>Q2N_DUMMY);
71     INV1 : INV
72     port map (I=>CLK,
73               O=>XLXN_68);
74     INV2 : INV
75     port map (I=>XLXN_68,
76               O=>XLXN_69);
77     INV3 : INV
78     port map (I=>D,
79               O=>XLXN_5);
80
81
82 end BEHAVIORAL;

```

Codice Componente 3.4: Definizione del Flip Flop D Edge Triggered sul fronte di salita Sami

### 3.4.2.2 Flip Flop D Edge Triggered sul fronte di discesa

```

1  library ieee;
2  use ieee.std_logic_1164.ALL;
3  use ieee.numeric_std.ALL;
4  library UNISIM;
5  use UNISIM.Vcomponents.ALL;
6
7  entity SamiFronteDiscesa is
8      port ( CLK : in    std_logic;
9            D   : in    std_logic;
10           Q2  : out   std_logic;
11           Q2N : out   std_logic);
12 end SamiFronteDiscesa;
13
14 architecture BEHAVIORAL of SamiFronteDiscesa is
15     attribute BOX_TYPE : string ;
16     signal Q           : std_logic;
17     signal Q1          : std_logic;
18     signal XLXN_10     : std_logic;
19     signal XLXN_23     : std_logic;
20     signal XLXN_26     : std_logic;
21     signal Q2_DUMMY    : std_logic;

```

```

22  signal Q2N_DUMMY : std_logic;
23  component NAND2
24      port ( I0 : in      std_logic;
25             I1 : in      std_logic;
26             O  : out     std_logic);
27  end component;
28
29  attribute BOX_TYPE of NAND2 : component is "BLACK_BOX";
30  component NOR2      port ( I0 : in      std_logic;
31                             I1 : in      std_logic;
32                             O  : out     std_logic);
33  end component;
34
35  attribute BOX_TYPE of NOR2 : component is "BLACK_BOX";
36  component OR2
37      port ( I0 : in      std_logic;
38             I1 : in      std_logic;
39             O  : out     std_logic);
40  end component;
41
42  attribute BOX_TYPE of OR2 : component is "BLACK_BOX";
43
44  component INV
45      port ( I : in      std_logic;
46             O : out     std_logic);
47  end component;
48
49  attribute BOX_TYPE of INV : component is "BLACK_BOX";
50
51  begin
52
53      Q2 <= Q2_DUMMY;
54      Q2N <= Q2N_DUMMY;
55
56      a1 : NAND2
57      port map (I0=>Q1,
58                I1=>Q2N_DUMMY,
59                O=>Q2_DUMMY);
60      a2 : NAND2
61      port map (I0=>Q2_DUMMY,
62                I1=>Q,
63                O=>Q2N_DUMMY);
64      g1 : NOR2
65      port map (I0=>XLXN_26,
66                I1=>CLK,
67                O=>XLXN_23);
68      g2 : OR2
69      port map (I0=>XLXN_10,
70                I1=>XLXN_23,

```

```

71         O=>Q1);
72     g3 : OR2
73     port map (I0=>XLXN_23,
74               I1=>D,
75               O=>Q);
76     INV1 : INV
77     port map (I=>CLK,
78               O=>XLXN_26);
79     INV2 : INV
80     port map (I=>D,
81               O=>XLXN_10);
82
83 end BEHAVIORAL;

```

Codice Componente 3.5: Definizione del Flip Flop D Edge Triggered sul fronte di discesa Sami

### 3.5 Simulazione

La seguente simulazione behavioral mostra come cambia lo stato del flip flop, a seconda della variazione del dato D, in corrispondenza del fronte del clock. Un unico testbench è presentato per entrambe le soluzioni (rising e falling edge).

```

1
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.ALL;
4  USE ieee.numeric_std.ALL;
5  LIBRARY UNISIM;
6  USE UNISIM.vcomponents.ALL;
7  ENTITY SamiFronteDiscesa_SamiFronteDiscesa_sch_tb IS
8  END SamiFronteDiscesa_SamiFronteDiscesa_sch_tb;
9
10 ARCHITECTURE behavioral OF SamiFronteDiscesa_SamiFronteDiscesa_sch_tb IS
11
12     COMPONENT SamiFronteDiscesa
13     PORT(
14         D : IN STD_LOGIC;
15         Q2N : OUT STD_LOGIC;
16         Q2 : OUT STD_LOGIC;
17         CLK : IN STD_LOGIC);
18     END COMPONENT;
19
20     SIGNAL D :STD_LOGIC := '0';
21     SIGNAL Q2N :STD_LOGIC;
22     SIGNAL Q2 :STD_LOGIC;
23     SIGNAL CLK :STD_LOGIC;
24     constant CLK_period : time := 10 ns;
25
26 BEGIN

```


```

27  UUT: SamiFronteDiscesa PORT MAP (
28      D => D,
29      Q2N => Q2N,
30      Q2 => Q2,
31      CLK => CLK
32  );
33
34
35  CLK_process :process
36  BEGIN
37      CLK<= '0';
38      wait for CLK_period/2;
39      CLK <= '1';
40      wait for CLK_period/2;
41  end process;
42
43  tb : PROCESS
44  BEGIN
45  wait for 10 ns;
46
47  D<= '0', '1' after 28 ns,'0' after 42 ns, '1' after 53 ns,'0' after 66 ns;
48
49      WAIT;
50  END PROCESS;
51
52  END;


```

Codice Componente 3.6: Definizione del testbench per ffd sami etd

 
Simulazione behavioral del flip flop edge triggered su fronte di discesa:



 
Simulazione behavioral del flip flop edge triggered su fronte di salita:


 
### 3.6 Flip Flop D Master Slave - Prof. Antonino Mazzeo




La soluzione prevede di collegare in cascata due flip flop D: un master, attivo sul fronte di salita del clock, e uno slave, attivo sul fronte di discesa. Quando il clock si alza, il master campiona il dato D in ingresso e lo presenta in uscita dopo un certo ritardo; il flip flop slave riceve in ingresso il dato campionato dal master ma non campiona e presenta il dato fino a quando il segnale di clock non si abbassa.

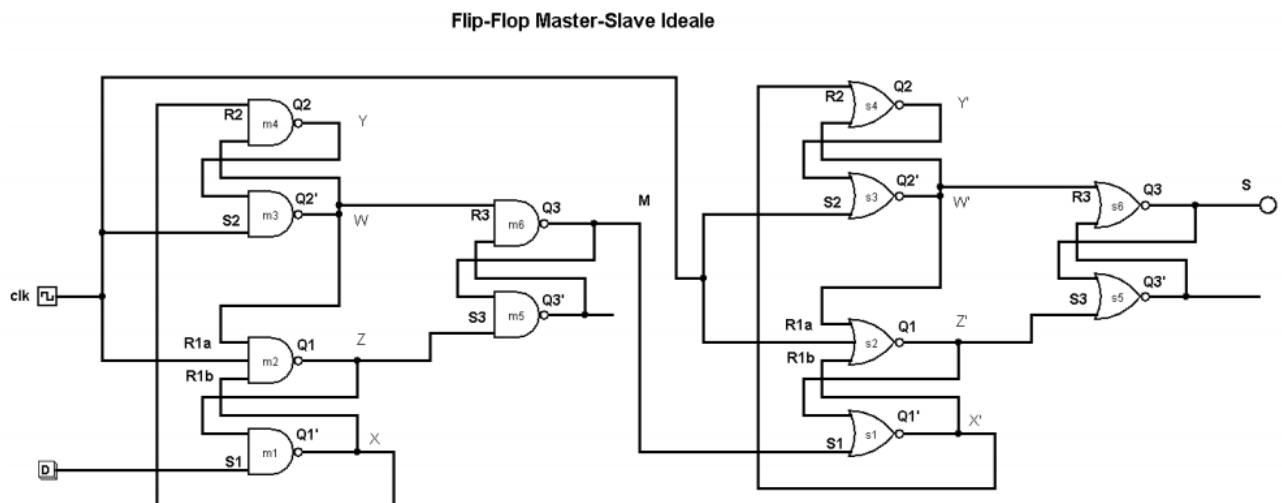

Di seguito è possibile osservare l'automa a stati finiti del flip flop master-slave ideale, i cui stati sono:


- $q_0$  e  $q_1$  in cui il flip flop presenta rispettivamente 0 e 1;
- $q_{00}$  e  $q_{11}$  in cui, all'alzarsi del segnale di abilitazione, campiona lo stesso dato che sta già presentando;

 - q01 e q10 in cui è stato campionato un valore diverso da quello che sta correntemente presentando.


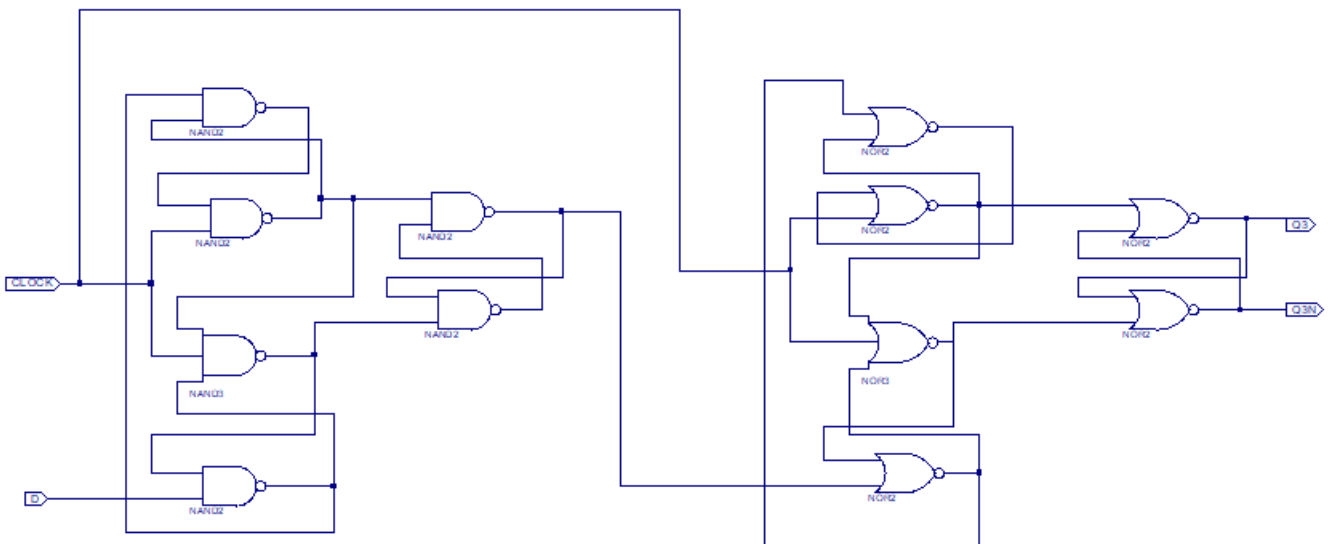
### 3.6.1 Schematici

Si è scelto di sviluppare il progetto direttamente tramite schematic in Xilinx ISE, usando il tool grafico e collegando manualmente le porte logiche.



Come si può osservare, la struttura deve essere realizzata con un flip flop edge triggered a porte NAND per il master e uno a porte NOR per lo slave, per poter campionare sul fronte di salita e presentare sul fronte di discesa del segnale di abilitazione.

### 3.6.2 Codice

Il codice HDL functional model è autogenerato da Xilinx ISE e implementa la soluzione utilizzando un approccio di tipo strutturale.

```
1 library ieee;
```

```

2 use ieee.std_logic_1164.ALL;
3 use ieee.numeric_std.ALL;
4 library UNISIM;
5 use UNISIM.Vcomponents.ALL;
6
7 entity MazzeoMS is
8     port ( CLOCK : in      std_logic;
9           D      : in      std_logic;
10          Q3      : out     std_logic;
11          Q3N     : out     std_logic);
12 end MazzeoMS;
13
14 architecture Structural of MazzeoMS is
15     attribute BOX_TYPE : string ;
16     signal M           : std_logic;
17     signal W           : std_logic;
18     signal W1          : std_logic;
19     signal X           : std_logic;
20     signal XLXN_86     : std_logic;
21     signal X1          : std_logic;
22     signal Y           : std_logic;
23     signal Y1          : std_logic;
24     signal Z           : std_logic;
25     signal Z1          : std_logic;
26     signal Q3_DUMMY    : std_logic;
27     signal Q3N_DUMMY   : std_logic;
28     component NAND2
29         port ( I0 : in      std_logic;
30               I1 : in      std_logic;
31               O  : out     std_logic);
32     end component;
33     attribute BOX_TYPE of NAND2 : component is "BLACK_BOX";
34     component NAND3
35         port ( I0 : in      std_logic;
36               I1 : in      std_logic;
37               I2 : in      std_logic;
38               O  : out     std_logic);
39     end component;
40     attribute BOX_TYPE of NAND3 : component is "BLACK_BOX";
41     component NOR2
42         port ( I0 : in      std_logic;
43               I1 : in      std_logic;
44               O  : out     std_logic);
45     end component;
46     attribute BOX_TYPE of NOR2 : component is "BLACK_BOX";
47     component NOR3
48         port ( I0 : in      std_logic;
49               I1 : in      std_logic;
50               I2 : in      std_logic);

```

```

51         O : out    std_logic);
52 end component;
53 attribute BOX_TYPE of NOR3 : component is "BLACK_BOX";
54 begin
55 Q3 <= Q3_DUMMY;
56 Q3N <= Q3N_DUMMY;
57
58 m1 : NAND2
59     port map (I0=>D,
60               I1=>Z,
61               O=>X);
62 m2 : NAND3
63     port map (I0=>X,
64               I1=>CLOCK,
65               I2=>W,
66               O=>Z);
67 m3 : NAND2
68     port map ( I0=>CLOCK,
69               I1=>Y,
70               O=>W);
71 m4 : NAND2
72     port map (I0=>W,
73               I1=>X,
74               O=>Y);
75 m5 : NAND2
76     port map (I0=>Z,
77               I1=>M,
78               O=>XLXN_86);
79 m6 : NAND2
80     port map (I0=>XLXN_86,
81               I1=>W,
82               O=>M);
83 s1 : NOR2
84     port map (I0=>M,
85               I1=>Z1,
86               O=>X1);
87 s2 : NOR3
88     port map (I0=>X1,
89               I1=>CLOCK,
90               I2=>W1,
91               O=>Z1);
92 s3 : NOR2
93     port map (I0=>CLOCK,
94               I1=>Y1,
95               O=>W1);
96 s4 : NOR2
97     port map (I0=>W1,
98               I1=>X1,
99               O=>Y1);

```



```

100     s5 : NOR2
101     port map (I0=>Z1,
102               I1=>Q3_DUMMY,
103               O=>Q3N_DUMMY);
104     s6 : NOR2
105     port map (I0=>Q3N_DUMMY,
106               I1=>W1,
107               O=>Q3_DUMMY);
108 end Structural;

```

Codice Componente 3.7: Definizione del componente Arbitro 2 su 3

### 3.7 Simulazione

Il testbench ci conferma quanto già discusso in via teorica. Il flip flop master slave campiona sul fronte di salita e presenta il valore campionato sul fronte di discesa del clock.

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3  USE ieee.numeric_std.ALL;
4  LIBRARY UNISIM;
5  USE UNISIM.Vcomponents.ALL;
6  ENTITY MazzeoMS_MazzeoMS_sch_tb IS END MazzeoMS_MazzeoMS_sch_tb;
7  ARCHITECTURE behavioral OF MazzeoMS_MazzeoMS_sch_tb IS
8
9  COMPONENT MazzeoMS
10     PORT(
11         CLOCK: IN STD_LOGIC;
12         Q3: OUT STD_LOGIC;
13         Q3N: OUT STD_LOGIC;
14         D: IN STD_LOGIC
15     );
16 END COMPONENT;
17
18 SIGNAL Q3: STD_LOGIC := '0';
19 SIGNAL Q3N: STD_LOGIC;
20 SIGNAL CLOCK: STD_LOGIC;
21 SIGNAL D: STD_LOGIC := '0';
22 constant CLK_period : time := 10 ns;
23
24 BEGIN
25     UUT: MazzeoMS PORT MAP( Q3 => Q3, Q3N => Q3N, CLOCK => CLOCK, D => D );
26
27 CLOCK_process : process
28     begin
29         CLOCK <= '0';
30         wait for CLK_period/2;
31         CLOCK <= '1';
32         wait for CLK_period/2;


```

```

32 end process;
33
34 stim_proc: process
35 begin
36 wait for 20 ns;
37 D<= '0', '1' after 20 ns, '0' after 50 ns, '1' after 60 ns, '0' after 80 ns;
38 wait;
39 end process;
40 END;

```

 La simulazione in ISim conferma le aspettative mostrando che al variare di D, l'uscita del flip flop commuta solamente sul fronte di discesa del clock.




### 3.8 Flip Flop D Master Slave - Prof. Sami

Il progetto illustrato nelle dispense ci mostra un tipo di implementazione differente da quello visto in precedenza. Innanzitutto esso utilizza due Latch SR (un Master e uno Slave), le cui uscite Q e Q negato del Master sono collegate rispettivamente agli ingressi di Set e Reset dello Slave. Il Latch SR segue la logica retroazionale vista precedentemente nel Flip Flop del Prof. Mazzeo e può essere implementato sia con porte NAND (attivo basso) sia con porte NOR (attivo alto). Nella sua versione attivo alto, che è quella scelta, lo stato di memoria del Latch SR si ottiene quando entrambi gli ingressi sono bassi. La funzione di Reset avviene quando R è alto ed S è basso, come illustrato nella seguente tabella di verità :

S	R
0	0
0	1
1	0
1	1


"00" Memorizzazione. "01" Reset. "10" Set. "11" non ammesso.

 Partendo da questo si può costruire un flip flop D Master Slave :


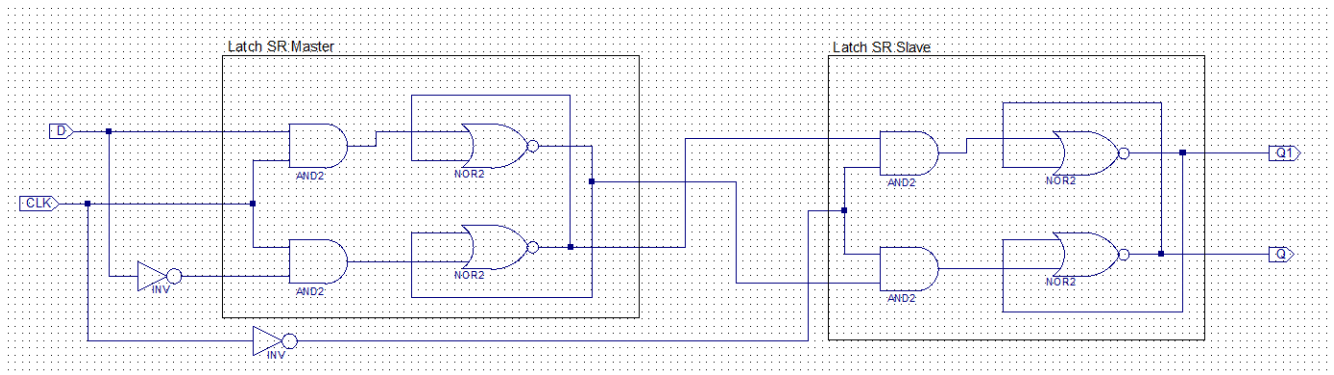
### 3.8.1 Schematici

Lo schematico in figura sottostante, realizzato col tool grafico di Xilinx, mostra i collegamenti tra i dispositivi e in particolare i latch che sono costruiti nella versione attivo alta (quindi con la parte di destra formata dal Latch SR asincrono e le due porte AND).



### 3.8.2 Codice

Il codice HDL functional model è autogenerato da Xilinx ISE e implementa la soluzione utilizzando un approccio di tipo strutturale.

```

1  library ieee;
2  use ieee.std_logic_1164.ALL;
3  use ieee.numeric_std.ALL;
4  library UNISIM;
5  use UNISIM.vcomponents.ALL;
6
7  entity SamiMasterSlave is
8      port ( CLK : in    std_logic;
9             D   : in    std_logic;
10            Q   : out   std_logic;
11            Q1  : out   std_logic);
12 end SamiMasterSlave;
13
14 architecture BEHAVIORAL of SamiMasterSlave is
15     attribute BOX_TYPE : string ;
16     signal XLXN_1      : std_logic;

```

```

17  signal XLXN_2    : std_logic;
18  signal XLXN_4    : std_logic;
19  signal XLXN_5    : std_logic;
20  signal XLXN_27   : std_logic;
21  signal XLXN_28   : std_logic;
22  signal XLXN_29   : std_logic;
23  signal XLXN_41   : std_logic;
24  signal Q1_DUMMY  : std_logic;
25  signal Q_DUMMY   : std_logic;
26
27  component AND2
28      port ( I0 : in    std_logic;
29             I1 : in    std_logic;
30             O  : out   std_logic);
31  end component;
32
33  attribute BOX_TYPE of AND2 : component is "BLACK_BOX";
34  component NOR2
35      port ( I0 : in    std_logic;
36             I1 : in    std_logic;
37             O  : out   std_logic);
38  end component;
39  attribute BOX_TYPE of NOR2 : component is "BLACK_BOX";
40
41  component INV
42      port ( I : in    std_logic;
43             O : out   std_logic);
44  end component;
45  attribute BOX_TYPE of INV : component is "BLACK_BOX";
46  begin
47      Q <= Q_DUMMY;
48      Q1 <= Q1_DUMMY;
49
50      a1 : AND2
51          port map (I0=>XLXN_27,
52                   I1=>CLK,
53                   O=>XLXN_4);
54
55      a2 : AND2
56          port map (I0=>CLK,
57                   I1=>D,
58                   O=>XLXN_5);
59
60      a3 : AND2
61          port map (I0=>XLXN_1,
62                   I1=>XLXN_41,
63                   O=>XLXN_28);
64
65      a4 : AND2

```

```

66     port map (I0=>XLXN_41,
67               I1=>XLXN_2,
68               O=>XLXN_29);
69
70     g1 : NOR2
71     port map (I0=>XLXN_4,
72               I1=>XLXN_1,
73               O=>XLXN_2);
74
75     g2 : NOR2
76     port map (I0=>XLXN_2,
77               I1=>XLXN_5,
78               O=>XLXN_1);
79
80     g3 : NOR2
81     port map (I0=>XLXN_28,
82               I1=>Q1_DUMMY,
83               O=>Q_DUMMY);
84
85     g4 : NOR2
86     port map (I0=>Q_DUMMY,
87               I1=>XLXN_29,
88               O=>Q1_DUMMY);
89
90     not1 : INV
91     port map (I=>CLK,
92               O=>XLXN_41);
93
94     not2 : INV
95     port map (I=>D,
96               O=>XLXN_27);
97
98 end BEHAVIORAL;

```

Codice Componente 3.8: Definizione del componente Arbitro 2 su 3

### 3.9 Simulazione

Il codice del testbench è riportato di seguito.

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3  USE ieee.numeric_std.ALL;
4  LIBRARY UNISIM;
5  USE UNISIM.Vcomponents.ALL;
6  ENTITY MasterSlave_MasterSlave_sch_tb IS
7  END MasterSlave_MasterSlave_sch_tb;
8  ARCHITECTURE behavioral OF MasterSlave_MasterSlave_sch_tb IS

```


```

9
10 COMPONENT MasterSlave
11 PORT( CLK : IN  STD_LOGIC;
12       Q1 : OUT STD_LOGIC;
13       Q  : OUT STD_LOGIC;
14       D  : IN  STD_LOGIC);
15 END COMPONENT;
16
17 SIGNAL CLK : STD_LOGIC;
18 SIGNAL Q1 : STD_LOGIC;
19 SIGNAL Q  : STD_LOGIC;
20 SIGNAL D  : STD_LOGIC;
21
22 constant CLK_period : time := 10 ns;
23
24 BEGIN
25
26   UUT: MasterSlave PORT MAP(
27     CLK => CLK,
28     Q1 => Q1,
29     Q  => Q,
30     D  => D
31   );
32
33   CLK_process : process
34   begin
35     CLK <= '0';
36     wait for CLK_period/2;
37     CLK <= '1';
38     wait for CLK_period/2;
39   end process;
40
41   stim_proc: process
42   begin
43     D <= '0';
44     wait for 98 ns;
45     D <= '1';
46     wait;
47   end process;
48 END;

```

Codice Componente 3.9: Definizione del testbench per SamiMS

 I risultati del test sono quelli attesi. Il dato contenuto nel registro commuta al variare di D e soltanto sul fronte di discesa del clock:



# Capitolo 4


## Esercizio 4

### 4.1 Traccia

Progettare ed implementare in VHDL un sommatore a propagazione dei riporti per stringhe di 4 bit, ed utilizzarlo successivamente per realizzare un sommatore di stringhe di 8 bit. Sintetizzare sulla board il sommatore di stringhe di 8 bit, utilizzando gli switch e i bottoni per inserire le stringhe di input, due cifre del display a 7 segmenti per visualizzare l'output su 8 bit, e un led per segnalare la condizione di overflow. NOTA: i due addendi devono essere acquisiti in due tempi diversi, secondo una tecnica a scelta dello studente.
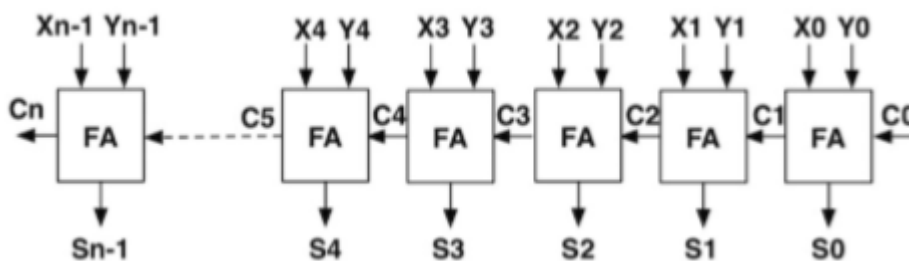
### 4.2 Soluzione


Il sommatore ad 8 bit viene realizzato per composizione di due sommatore a 4 bit. Il sommatore a 4 bit viene realizzato tramite cascata di full adder (4 in questo caso). Il singolo full adder presenta due ingressi per gli operandi da sommare e uno per il valore di riporto. Quest'ultimo nel primo full adder della cascata è normalmente 0. Le uscite sono la somma dei due operandi e il riporto (0,1) che viene collegato in ingresso al full adder immediatamente successivo.



Per realizzare il full adder si è fatto uso di due half adder, le cui uscite vengono messe in xor per ottenere il bit di somma.


Per quest'ultimo componente, si riporta la tabella di verità (input a sinistra e output a destra):

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

 

Di seguito si riporta la tabella di verità del full adder, realizzato come composizione di due half adder. X,Y e Z sono gli ingressi; S è il bit di somma e C quello di riporto.

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	1	1	1

 


### 4.2.1 Schematici


Gli schematici sono mostrati a partire da quello del full adder a 8 bit.




(Ripple Carry Adder 8 bit)

 

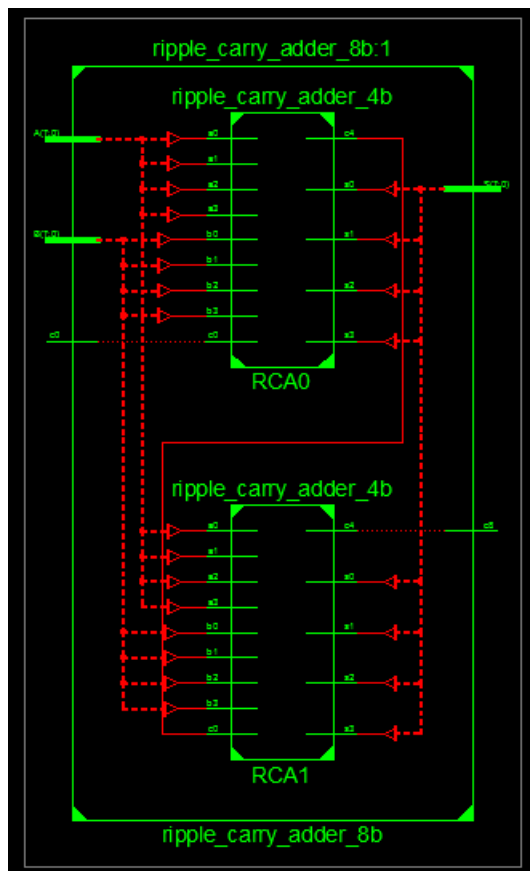
(Ripple Carry Adder 8 bit - Composizione)



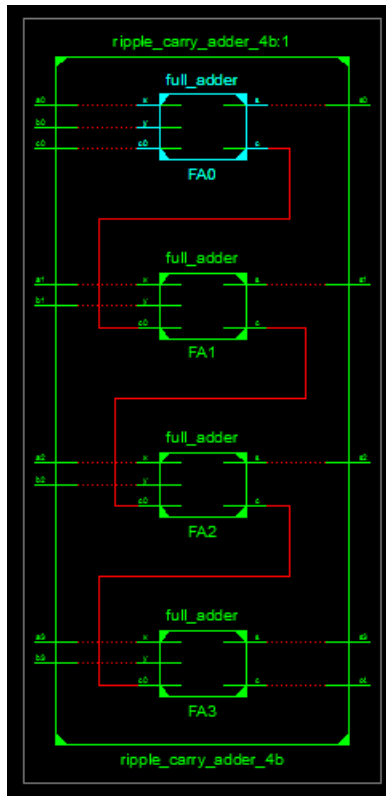(Ripple Carry Adder 4 bit - Composizione)



(Full Adder - Composizione)

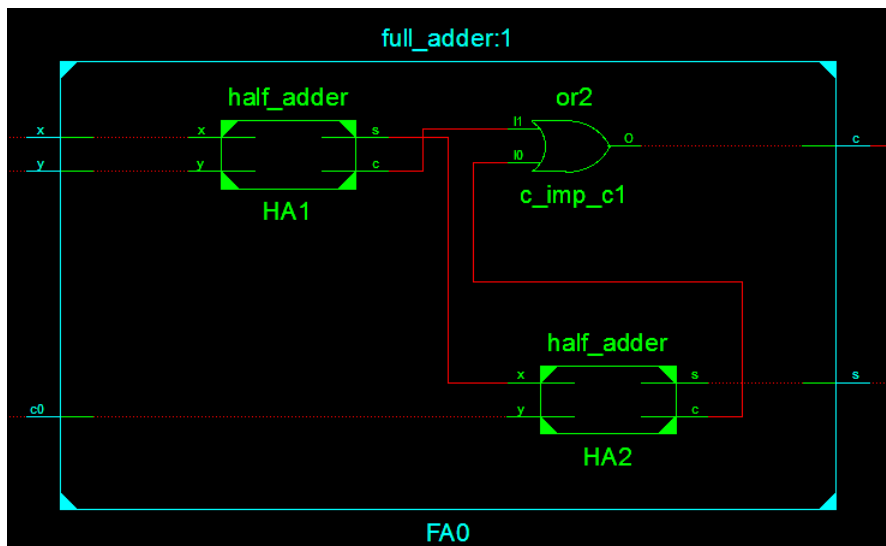

## 4.2.2 Codice

### 4.2.2.1 Ripple Carry Adder 8 bit

Tramite descrizione strutturale si usano i due sommatore a propagazione di riporti di 4 bit per crearne uno da 8 bit. Tale componente può essere usato per comporre eventualmente sommatore più grandi (16, 32, 64 bit).

L'ingresso c0 del sommatore a 8 bit corrisponderà al riporto del primo da 4 bit ed è '0' in questo caso.

```

1  entity ripple_carry_adder_8b is
2
3  PORT (
4      A : in  std_logic_vector (7 downto 0);
5      B : in  std_logic_vector(7 downto 0);
6      c0 : in std_logic;
7      c8 : out std_logic;
8      S : out std_logic_vector (7 downto 0)
9      );
10
11 end ripple_carry_adder_8b;
12
13 architecture Structural of ripple_carry_adder_8b is
14
15 Component ripple_carry_adder_4b
16     PORT (
17         a0, a1, a2, a3 : in  std_logic;
18         b0, b1, b2, b3 : in  std_logic;
19         c0 : in std_logic;
20         c4 : out std_logic;
21         s0, s1, s2, s3: out std_logic );
22 end Component;
23
24 signal c : std_logic;
25
26 begin
27 RCA0 : ripple_carry_adder_4b port map (
28     a0 => A(0),
29     a1 => A(1),
30     a2 => A(2),
31     a3 => A(3),
32     b0 => B(0),
33     b1 => B(1),
34     b2 => B(2),
35     b3 => B(3),
36     c0 => c0,
37     s0 => S(0),
38     s1 => S(1),
39     s2 => S(2),
40     s3 => S(3),
41     c4 => c
42 );
43 RCA1 : ripple_carry_adder_4b port map (
44     a0 => A(4),
45     a1 => A(5),
46     a2 => A(6),

```

```

47     a3 => A(7),
48     b0 => B(4),
49     b1 => B(5),
50     b2 => B(6),
51     b3 => B(7),
52     c0 => c,
53     s0 => S(4),
54     s1 => S(5),
55     s2 => S(6),
56     s3 => S(7),
57     c4 => c8
58 );
59 end Structural;

```

Codice Componente 4.1: Definizione del componente Bit String Comparator Generic

#### 4.2.2.2 Ripple Carry Adder 4 bit

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity ripple_carry_adder_4b is
5  PORT (
6      a0, a1, a2, a3 : in  std_logic;
7      b0, b1, b2, b3 : in  std_logic;
8      c0 : in std_logic;
9      c4 : out std_logic;
10     s0, s1, s2, s3: out std_logic
11 );
12
13 end ripple_carry_adder_4b;
14
15 architecture Structural of ripple_carry_adder_4b is
16
17 Component full_adder
18     PORT (
19         x : in  std_logic;
20         y : in std_logic;
21         c0 : in std_logic;
22         s : out std_logic;
23         c : out std_logic );
24 end Component;
25
26 signal c1, c2, c3 : std_logic;
27
28 begin
29 FA0 : full_adder port map (
30     x => a0,

```

```

31     y => b0,
32     c0 => c0,
33     s => s0,
34     c => c1
35 );
36
37 FA1 : full_adder port map (
38     x => a1,
39     y => b1,
40     c0 => c1,
41     s => s1,
42     c => c2
43 );
44
45 FA2 : full_adder port map (
46     x => a2,
47     y => b2,
48     c0 => c2,
49     s => s2,
50     c => c3
51 );
52 FA3 : full_adder port map (
53     x => a3,
54     y => b3,
55     c0 => c3,
56     s => s3,
57     c => c4
58 );
59
60 end Structural;

```

Codice Componente 4.2: Definizione del componente Bit String Comparator Generic

#### 4.2.2.3 Full Adder

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity full_adder is
5      PORT (
6          x : in  std_logic;
7          y : in  std_logic;
8          c0 : in  std_logic;
9          s : out std_logic;
10         c : out std_logic );
11
12 end full_adder;
13

```

```

14 architecture structural of full_adder is
15
16 Component half_adder
17     PORT ( x : in std_logic;
18           y : in std_logic;
19           s : out std_logic;
20           c : out std_logic);
21 end Component;
22
23 signal s1, c1, c2 : std_logic;
24
25 begin
26
27 HA1 : half_adder port map (
28     x => x,
29     y => y,
30     s => s1,
31     c => c1);
32 HA2 : half_adder port map(
33     x => s1,
34     y => c1,
35     s => s,
36     c => c2);
37
38 c <= c2 or c1;
39
40
41 end structural;

```

Codice Componente 4.3: Definizione del componente Bit String Comparator Generic

#### 4.2.2.4 Half Adder

```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity half_adder is
5     PORT ( x : in std_logic;
6           y : in std_logic;
7           s : out std_logic;
8           c : out std_logic);
9 end half_adder;
10
11 architecture DataFlow of half_adder is
12
13 begin
14
15 s <= x xor y;

```

```

16 c <= x and y;
17
18 end DataFlow;

```

Codice Componente 4.4: Definizione del componente Bit String Comparator Generic

### 4.3 Simulazione

Sono stati analizzati alcuni casi di particolare interesse con riporto 0 e 1 :

Riporto 0

A	B	C0	OUT	C_OUT
01010110	00011000	0	01101110	0
00000000	00000000	0	00000000	0
11111110	00000001	0	11111111	0
11111111	00000001	0	00000000	1
10000000	10000000	0	00000000	1

Riporto 1

A	B	C0	OUT	C_OUT
01010110	00011000	1	01101111	0
00000000	00000000	1	00000001	0
11111110	00000001	1	00000000	1
11111111	00000001	1	00000001	1
10000000	10000000	1	00000001	1

```

1
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.ALL;
4
5 -- Uncomment the following library declaration if using
6 -- arithmetic functions with Signed or Unsigned values
7 --USE ieee.numeric_std.ALL;
8
9 ENTITY tests IS
10 END tests;
11
12 ARCHITECTURE behavior OF tests IS
13
14     COMPONENT ripple_carry_adder_8b
15     PORT(
16         A : IN  std_logic_vector(7 downto 0);
17         B : IN  std_logic_vector(7 downto 0);
18         c0 : IN  std_logic;
19         c8 : OUT std_logic;
20         S : OUT std_logic_vector(7 downto 0)

```

```
21     );
22     END COMPONENT;
23
24
25     --Inputs
26     signal A : std_logic_vector(7 downto 0) := (others => '0');
27     signal B : std_logic_vector(7 downto 0) := (others => '0');
28     signal c0 : std_logic := '0';
29
30     --Outputs
31     signal c8 : std_logic;
32     signal S : std_logic_vector(7 downto 0);
33
34
35
36 BEGIN
37
38     uut: ripple_carry_adder_8b PORT MAP (
39         A => A,
40         B => B,
41         c0 => c0,
42         c8 => c8,
43         S => S
44     );
45
46
47     -- Stimulus process
48     stim_proc: process
49     begin
50         wait for 100 ns;
51
52         A <= "01010110";
53         B <= "00011000";
54         c0 <= '0';
55         wait for 100 ns;
56
57         A <= "00000000";
58         B <= "00000000";
59         c0 <= '0';
60         wait for 100 ns;
61
62         A <= "11111110";
63         B <= "00000001";
64         c0 <= '0';
65         wait for 100 ns;
66
67         A <= "11111111";
68         B <= "00000001";
69         c0 <= '0';
```



```

70     wait for 100 ns;
71
72     A <= "10000000";
73     B <= "10000000";
74     c0 <= '0';
75     wait for 100 ns;
76
77     A <= "01010110";
78     B <= "00011000";
79     c0 <= '1';
80     wait for 100 ns;
81
82     A <= "00000000";
83     B <= "00000000";
84     c0 <= '1';
85     wait for 100 ns;
86
87     A <= "11111110";
88     B <= "00000001";
89     c0 <= '1';
90     wait for 100 ns;
91
92     A <= "11111111";
93     B <= "00000001";
94     c0 <= '1';
95     wait for 100 ns;
96
97     A <= "10000000";
98     B <= "10000000";
99     c0 <= '1';
100
101
102     wait;
103 end process;
104
105 END;

```

Codice Componente 4.5: Testbench ripple carry adder

Risultati del test nel caso riporto 0 :

Name	Value	0 ns	100 ns	200 ns	300 ns	400 ns	500 ns
a[7:0]	01010110	00000000	01010110	00000000	11111110	11111111	10000000
b[7:0]	00011000	00000000	00011000	00000000	00000001		10000000
c0	1						
c8	0						
s[7:0]	01101111	00000000	01101110	00000000	11111111	00000000	00000000


Risultati del test nel caso riporto 1 :

500 ns	700 ns	800 ns	900 ns
01010110	00000000	11111110	11111111
00011000	00000000	00000001	
01101111	00000001	00000000	00000001
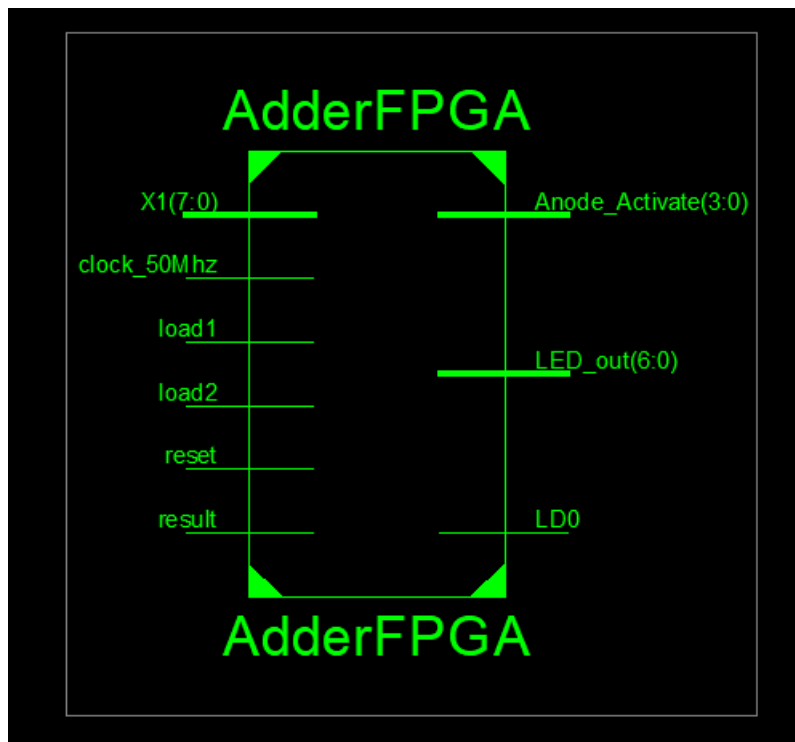
## 4.4 Sintesi su board FPGA

La sintesi del ripple carry adder a 8 bit su FPGA Nexys2 ha richiesto la realizzazione di componenti aggiuntivi.

Due bottoni (load 1 e load2) vengono utilizzati per l'acquisizione del valore dei due operandi, attraverso gli switch. Viene effettuata la somma e con la pressione di un terzo pulsante (result) viene mostrata su display a 7 segmenti. Il quarto ed ultimo pulsante viene invece usato come reset. La condizione di overflow è mostrata attraverso l'accensione del led LD0.



Il display a 7 segmenti utilizzato è quello mostrato nei capitoli precedenti. Di seguito sono presenti i file vhd e ucf relativi alla sintesi del componente su FPGA.

### 4.4.1 File UCF

```

2 NET "LED_out<6>" LOC = "L18"; # Bank = 1, Pin name = IO_L10P_1, Type = I/O,
  Sch name = CA
3 NET "LED_out<5>" LOC = "F18"; # Bank = 1, Pin name = IO_L19P_1, Type = I/O,
  Sch name = CB
4 NET "LED_out<4>" LOC = "D17"; # Bank = 1, Pin name = IO_L23P_1/HDC, Type =
  DUAL, Sch name = CC
5 NET "LED_out<3>" LOC = "D16"; # Bank = 1, Pin name = IO_L23N_1/LDC0, Type =
  DUAL, Sch name = CD
6 NET "LED_out<2>" LOC = "G14"; # Bank = 1, Pin name = IO_L20P_1, Type = I/O,
  Sch name = CE
7 NET "LED_out<1>" LOC = "J17"; # Bank = 1, Pin name = IO_L13P_1/A6/RHCLK4/
  IRDY1, Type = RHCLK/DUAL, Sch name = CF
8 NET "LED_out<0>" LOC = "H14"; # Bank = 1, Pin name = IO_L17P_1, Type = I/O,
  Sch name = CG
9
10 NET "clock_50Mhz" LOC = "B8"; # Bank = 0, Pin name = IP_L13P_0/GCLK8, Type
  = GCLK, Sch name = GCLK0
11 NET "Anode_Activate<0>" LOC = "F17"; # Bank = 1, Pin name = IO_L19N_1, Type
  = I/O, Sch name = AN0
12 NET "Anode_Activate<1>" LOC = "H17"; # Bank = 1, Pin name = IO_L16N_1/A0,
  Type = DUAL, Sch name = AN1
13 NET "Anode_Activate<2>" LOC = "C18"; # Bank = 1, Pin name = IO_L24P_1/LDC1,
  Type = DUAL, Sch name = AN2
14 NET "Anode_Activate<3>" LOC = "F15"; # Bank = 1, Pin name = IO_L21P_1, Type
  = I/O, Sch name = AN3
15
16 NET "X1<0>" LOC = "G18"; # Sch name = SW0
17 NET "X1<1>" LOC = "H18"; # Sch name = SW1
18 NET "X1<2>" LOC = "K18"; # Sch name = SW2
19 NET "X1<3>" LOC = "K17"; # Sch name = SW3
20 NET "X1<4>" LOC = "L14";
21 NET "X1<5>" LOC = "L13";
22 NET "X1<6>" LOC = "N17";
23 NET "X1<7>" LOC = "R17";
24 NET "load1" LOC = "B18";
25 NET "load2" LOC = "D18";
26 NET "reset" LOC = "H13";
27 NET "result" LOC = "E18";
28 NET "LD0" LOC = "J14";

```

#### 4.4.2 Sintesi finale

Un process regola l'immissione dei dati di input e il reset. Vengono utilizzati due flag booleani OP\_1 ed OP\_2 per verificare che siano stati immessi entrambi i valori. Quando vengono inseriti entrambi gli operandi, la pressione del terzo pulsante (result) pone in ingresso al segnale value\_to\_display il valore della somma e permette di far accendere il led della scheda se si ha overflow. Tale condizione si verifica quando gli addendi sono positivi e si ottiene un risultato negativo o quando gli addendi sono negativi e si ottiene un risultato positivo.

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4 use IEEE.std_logic_signed.all;
5
6 entity AdderFPGA is
7
8   Port (    clock_50Mhz : in STD_LOGIC;
9           reset : in STD_LOGIC;
10          X1 : in STD_LOGIC_VECTOR (7 downto 0);
11          load1,load2,result : in STD_LOGIC;
12          Anode_Activate : out STD_LOGIC_VECTOR (3 downto 0);
13          LED_out : out STD_LOGIC_VECTOR (6 downto 0);
14          LD0 : out STD_LOGIC );
15
16 end AdderFPGA;
17
18 architecture Behavioural of AdderFPGA is
19
20   signal OP_1, OP_2 : boolean := false;
21   signal op1,op2,sum : std_logic_vector (7 downto 0) := (others => '0') ;
22   signal value_to_display : std_logic_vector (7 downto 0):= (others => '0');
23   signal L1: std_logic:='0';
24
25   component ripple_carry_adder_8b is PORT (
26     A,B : in  std_logic_vector (7 downto 0);
27     c0 : in std_logic;
28     c8: out std_logic;
29     S: out std_logic_vector (7 downto 0)
30   );
31 end component;
32
33 component SEV_SEG_DISP is
34   Port ( clock_50Mhz : in STD_LOGIC;
35         reset : in STD_LOGIC;
36         X: in STD_LOGIC_VECTOR (7 downto 0);
37         Anode_Activate : out STD_LOGIC_VECTOR (3 downto 0);
38         LED_out : out STD_LOGIC_VECTOR (6 downto 0)
39   );
40 end component;
41
42
43
44 begin
45
46   FA8 : ripple_carry_adder_8b port map(
47     A => op1,
48     B => op2,


```

```

49     c0 => '0',
50     S => sum
51 );
52
53 SSD : SEV_SEG_DISP port map(
54     clock_50Mhz => clock_50Mhz,
55     reset => reset,
56     Anode_Activate => Anode_Activate,
57     LED_out => LED_out,
58     X => value_to_display
59 );
60
61
62
63 process (clock_50Mhz, reset)
64 begin
65
66     if (reset = '1') then
67         -- Reset
68         op1 <= (others => '0');
69         op2 <= (others => '0');
70         OP_1 <= false;
71         OP_2 <= false;
72     elsif (rising_edge(clock_50Mhz)) then
73
74         -- Immissione dati input
75         if load1 = '1' then
76             op1 <= X1;
77             OP_1 <= true;
78             OP_2 <= false;
79             LD0<='0';
80         elsif load2 = '1' then
81             op2 <= X1;
82             OP_2 <= true;
83         end if;
84
85         if (OP_1=true and OP_2=true) then
86             -- Display del risultato
87             if (result = '1') then
88                 value_to_display <=sum;
89
90                 if ((op1(7)='0' and op2(7)='0' and sum(7)='1') or (op1(7)='1' and op2
91                     (7)='1' and sum(7)='0')) then
92                     LD0<='1';
93                 else
94                     LD0<='0';
95                 end if;
96             end if;

```
 
```
97     else
98         -- Display dell'operando
99         value_to_display <= X1;
100         LD0<='0';
101     end if;
102 end if;
103
104 end process;
105 end Behavioural;
```



# Capitolo 5


## Esercizio 5

### 5.1 Traccia



Progettare ed implementare in VHDL un registro a scorrimento circolare di 8 bit utilizzando i flip-flop D edge triggered implementati all'esercizio 3 (si scelga una delle realizzazioni). Sintetizzare sulla board il componente utilizzando gli switch per acquisire il dato iniziale, un bottone per acquisire il segnale di shift e i led per visualizzare il contenuto del registro in ogni istante.
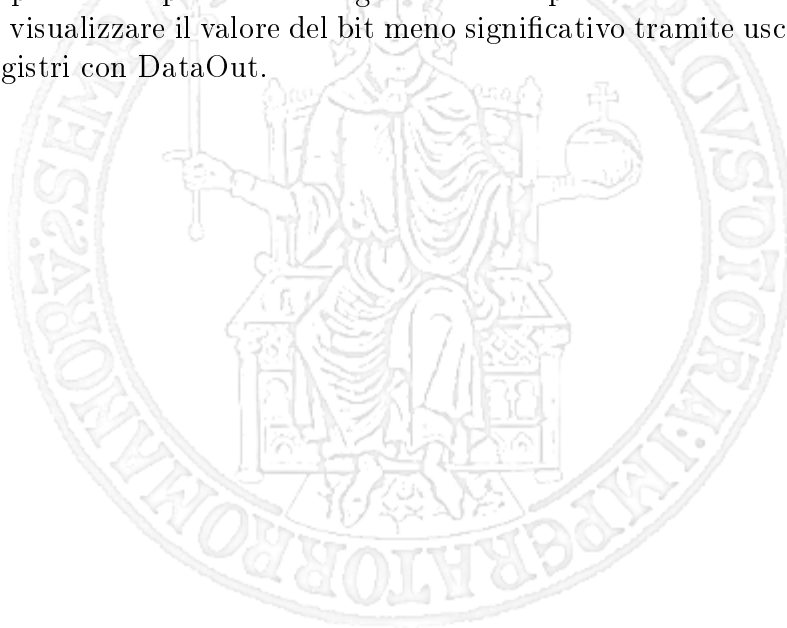
### 5.2 Soluzione

Lo shift register implementato prende in ingresso una stringa di 8 bit X, che può essere caricata nei flip flop (D edge triggered su fronte di discesa) in parallelo attraverso la pressione del pulsante load. Lo shift viene eseguito nel momento in cui il segnale di enable (pulsante enable) è pari ad 1. In questo caso, il valore contenuto nel flip flop i-esimo verrà propagato al flip flop (i+1)-esimo ogni qualvolta viene premuto il pulsante. Il segnale di reset pone a 0 il contenuto dei flip flop. In output è possibile visualizzare il valore del bit meno significativo tramite uscita Bitout e il valore corrente di tutti i registri con DataOut.



### 5.2.1 Schematici

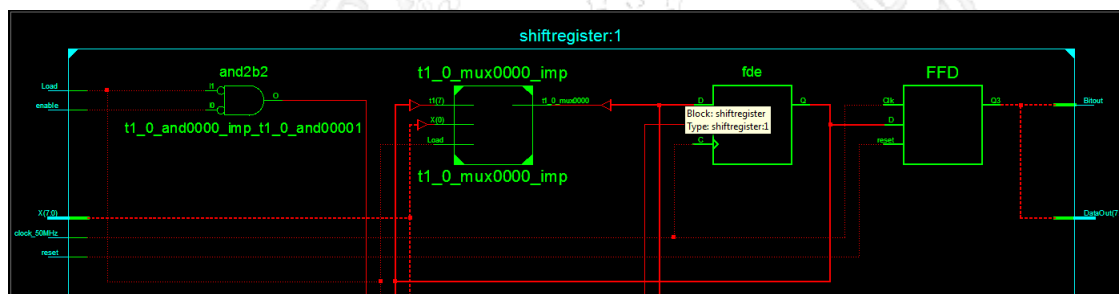 

### 5.2.2 Codice

#### 5.2.2.1 Registro a scorrimento circolare

Un process regola il caricamento dei dati in parallelo e l'abilitazione dell'operazione di shift, mentre i flip flop sono tra loro collegati per consentire la propagazione circolare del dato.

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
```



```

4
5 entity shiftregister is
6     Port (
7         X : in  STD_LOGIC_VECTOR (7 downto 0);
8         clock_50MHz, reset, Load, enable : in  STD_LOGIC;
9         Bitout : out STD_LOGIC:='0';
10        DataOut : out  STD_LOGIC_VECTOR (7 downto 0)
11    );
12 end shiftregister;
13
14 architecture Structural of shiftregister is
15
16 COMPONENT FFD
17     PORT(
18         D : IN std_logic;
19         Clk : IN std_logic;
20         reset : IN std_logic;
21         Q3 : OUT std_logic
22     );
23 END COMPONENT;
24
25 signal t1, t2 : std_logic_vector(7 downto 0):=(others=>'0');
26
27 begin
28
29
30
31 FFD0: FFD PORT MAP (
32     D => t1(0),
33     Q3 => t2(0),
34     Clk => clock_50MHz,
35     reset => reset
36 );
37
38 FFD1: FFD PORT MAP (
39     D => t1(1),
40     Q3 => t2(1),
41     Clk => clock_50MHz,
42     reset => reset
43 );
44
45 FFD2: FFD PORT MAP (
46     D => t1(2),
47     Q3 => t2(2),
48     Clk => clock_50MHz,
49     reset => reset
50 );
51
52

```

```
53
54 FFD3: FFD PORT MAP (
55     D => t1(3),
56     Q3 => t2(3),
57     Clk => clock_50MHz,
58     reset => reset
59 );
60
61
62 FFD4: FFD PORT MAP (
63     D => t1(4),
64     Q3 => t2(4),
65     Clk => clock_50MHz,
66     reset => reset
67 );
68
69
70 FFD5: FFD PORT MAP (
71     D => t1(5),
72     Q3 => t2(5),
73     Clk => clock_50MHz,
74     reset => reset
75 );
76
77
78 FFD6: FFD PORT MAP (
79     D => t1(6),
80     Q3 => t2(6),
81     Clk => clock_50MHz,
82     reset => reset
83 );
84
85 FFD7: FFD PORT MAP (
86     D => t1(7),
87     Q3 => t2(7),
88     Clk => clock_50MHz,
89     reset => reset
90 );
91
92
93
94 DataOut <= t2;
95 BitOut <= t2(7);
96
97 p: process(clock_50MHz)
98
99 begin
100
101
```

```

102 if(rising_edge(clock_50MHz)) then
103
104     if (Load='1') then
105         t1<=X;
106
107     elsif (enable='1') then
108
109         t1(7 downto 1)<=t1(6 downto 0);
110         t1(0)<=t1(7);
111     end if;
112
113 end if;
114 end process;
115
116 end Structural;

```

Codice Componente 5.1: Definizione del componente Registro a scorrimento circolare

### 5.2.2.2 FFD sul fronte di discesa con reset

Per l'implementazione del registro circolare sono stati utilizzati i seguenti flip flop edge triggered attivi su fronte di discesa (con aggiunta del reset):

```

1
2 library ieee;
3 use ieee.std_logic_1164.ALL;
4 use ieee.numeric_std.ALL;
5 library UNISIM;
6 use UNISIM.Vcomponents.ALL;
7
8 entity FFD is
9     port ( CLK      : in    std_logic:='0';
10           D        : in    std_logic:='0';
11           reset    : in    std_logic:='0';
12           Q3       : out   std_logic:='0'
13         );
14 end FFD;
15
16 architecture BEHAVIORAL of FFD is
17     attribute BOX_TYPE : string ;
18     signal A12         : std_logic:='0';
19     signal inverted    : std_logic:='0';
20     signal Q1          : std_logic:='0';
21     signal Q1N         : std_logic:='0';
22     signal Q2          : std_logic:='0';
23     signal Q2N         : std_logic:='0';
24     signal Q3_DUMMY    : std_logic:='0';
25     signal Q3N_DUMMY   : std_logic:='0';
26     component AND2

```

```

27     port ( I0 : in      std_logic;
28           I1 : in      std_logic;
29           O  : out     std_logic);
30 end component;
31 attribute BOX_TYPE of AND2 : component is "BLACK_BOX";
32
33 component NOR2
34     port ( I0 : in      std_logic;
35           I1 : in      std_logic;
36           O  : out     std_logic);
37 end component;
38 attribute BOX_TYPE of NOR2 : component is "BLACK_BOX";
39
40 component NOR3
41     port ( I0 : in      std_logic;
42           I1 : in      std_logic;
43           I2 : in      std_logic;
44           O  : out     std_logic);
45 end component;
46 attribute BOX_TYPE of NOR3 : component is "BLACK_BOX";
47
48 component INV
49     port ( I : in      std_logic;
50           O : out     std_logic);
51 end component;
52 attribute BOX_TYPE of INV : component is "BLACK_BOX";
53
54 begin
55 Q3 <= Q3_DUMMY;
56
57
58 a1 : AND2
59     port map (I0=>inverted,
60              I1=>D,
61              O=>A12);
62
63 g1 : NOR2
64     port map (I0=>A12,
65              I1=>Q1,
66              O=>Q1N);
67
68 g2 : NOR3
69     port map (I0=>Q1N,
70              I1=>CLK,
71              I2=>Q2N,
72              O=>Q1);
73
74 g3 : NOR2
75     port map (I0=>CLK,

```

```

76         I1=>Q2,
77         O=>Q2N);
78
79     g4 : NOR2
80         port map (I0=>Q2N,
81                 I1=>Q1N,
82                 O=>Q2);
83
84     g5 : NOR2
85         port map (I0=>Q1,
86                 I1=>Q3_DUMMY,
87                 O=>Q3N_DUMMY);
88
89     g6 : NOR2
90         port map (I0=>Q3N_DUMMY,
91                 I1=>Q2N,
92                 O=>Q3_DUMMY);
93
94     INV1 : INV
95         port map (I=>reset,
96                 O=>inverted);
97
98 end BEHAVIORAL;

```

Codice Componente 5.2: Definizione del componente FFD con reset

### 5.3 Simulazione

Per verificare il corretto funzionamento del registro circolare, sono stati eseguiti questi test :

- 1 - Inizializzazione dei registri a 0. Inserimento dei valori di X pari a 01001111, load ed enable pari ad '1';
- 2 - Test di funzionamento del segnale di reset;
- 3 - Inserimento di nuovi valori dopo il reset.

```

1
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.ALL;
4
5  ENTITY testb IS
6  END testb;
7
8  ARCHITECTURE behavior OF testb IS
9
10     -- Component Declaration for the Unit Under Test (UUT)
11
12     COMPONENT shiftregister
13     PORT (
14         X : IN  std_logic_vector(7 downto 0);

```

```

15     clock_50MHz : IN  std_logic;
16     reset : IN  std_logic;
17     Load,enable : IN  std_logic;
18     Bitout : OUT  std_logic;
19     DataOut : OUT  std_logic_vector(7 downto 0)
20 );
21 END COMPONENT;
22
23
24 --Inputs
25 signal X : std_logic_vector(7 downto 0) := (others => '0');
26 signal clock_50MHz : std_logic := '0';
27 signal reset : std_logic := '0';
28 signal Load,enable : std_logic := '0';
29
30 --Outputs
31 signal Bitout : std_logic:= '0';
32 signal DataOut : std_logic_vector(7 downto 0):= (others => '0');
33
34 -- Clock period definitions
35 constant clock_50MHz_period : time := 10 ns;
36
37 BEGIN
38
39 -- Instantiate the Unit Under Test (UUT)
40 uut: shiftregister PORT MAP (
41     X => X,
42     clock_50MHz => clock_50MHz,
43     reset => reset,
44     Load => Load,
45     enable=>enable,
46     Bitout => Bitout,
47     DataOut => DataOut
48 );
49
50 -- Clock process definitions
51 clock_50MHz_process :process
52 begin
53     clock_50MHz <= '0';
54     wait for clock_50MHz_period/2;
55     clock_50MHz <= '1';
56     wait for clock_50MHz_period/2;
57 end process;
58
59
60 -- Stimulus process
61 stim_proc: process
62 begin
63     -- hold reset state for 100 ns.

```

```


64     wait for 50 ns;
65
66     -- TEST 1
67     X<="01001111";
68     Load<='1';
69     wait for 10 ns;
70     Load <= '0';
71     wait for 20 ns;
72     enable <= '1';
73     wait for 300 ns;
74
75     -- TEST 2
76     reset <= '1';
77     wait for 50 ns;
78     reset <= '0';
79     enable <= '0';
80     wait for 150 ns;
81
82     -- TEST 3
83     X<="01000000";
84     Load<='1';
85     wait for 10 ns;
86     Load <= '0';
87     wait for 20 ns;
88     enable <= '1';
89
90     wait;
91 end process;
92
93 END;

```

Codice Componente 5.3: Definizione del testbench per Registro a scorrimento circolare

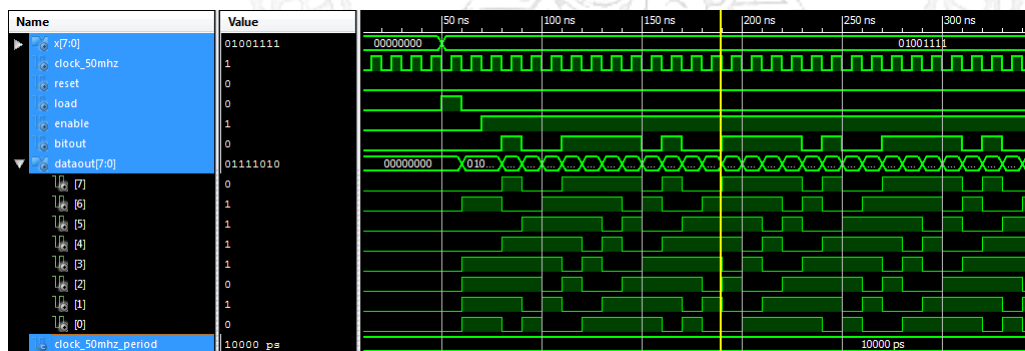
### 5.3.0.1 Test 1

Vengono caricati i bit in parallelo su tutti i flip flop. I bit vengono propagati per tutta la durata della simulazione in corrispondenza del fronte di discesa del clock.



 
### 5.3.0.2 Test 2

Osserviamo che il reset funziona correttamente. L'attivazione del segnale di reset pone direttamente a 0 il contenuto dei registri. Enable viene posto a 0 e lo shift register termina lo scorrimento.


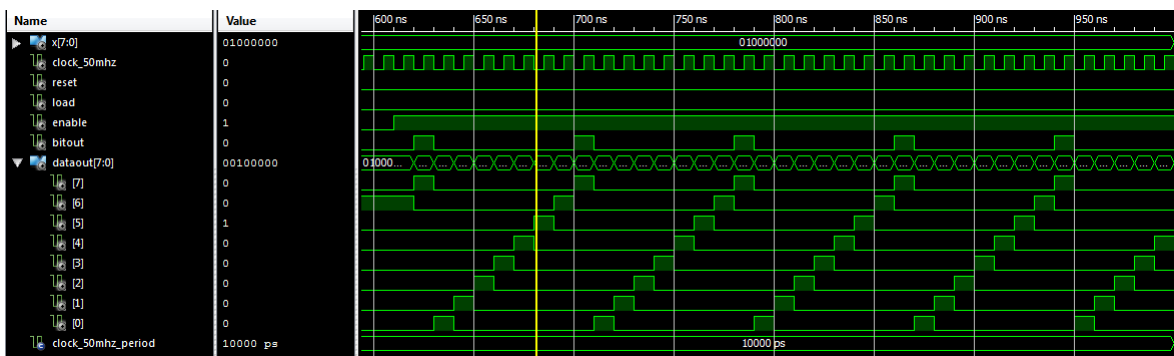
### 5.3.0.3 Test 3


Dopo il segnale di reset viene caricato un nuovo dato (01000000), che viene propagato fra tutti i flip flop per tutta la durata della simulazione.


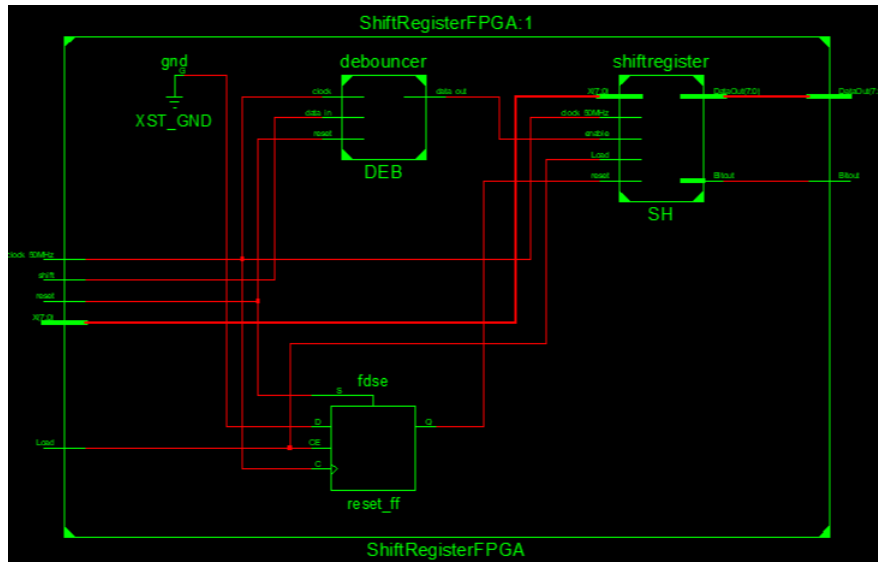
## 5.4 Sintesi su board FPGA

Adattare l'implementazione per il funzionamento su FPGA è semplice in questo caso, poichè essendo il caricamento effettuato in parallelo è possibile collegare l'input X con gli switch e l'output con i led. Load, reset e shift corrispondono a 3 dei bottoni della board. Load carica in X i dati attualmente presenti sugli switch, reset pone a 0 il contenuto dei flip flop e shift esegue un'unica operazione di shift circolare visualizzabile in output tramite i led.





```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4
5 -- Uncomment the following library declaration if using
6 -- arithmetic functions with Signed or Unsigned values
7 --use IEEE.NUMERIC_STD.ALL;
8
9 -- Uncomment the following library declaration if instantiating
10 -- any Xilinx primitives in this code.
11 --library UNISIM;
12 --use UNISIM.VComponents.all;
13
14 entity ShiftRegisterFPGA is
15     Port (
16         X : in  STD_LOGIC_VECTOR (7 downto 0);
17         clock_50MHz, reset : in  STD_LOGIC;
18         Load,shift :in STD_LOGIC;
19         Bitout : out STD_LOGIC;
20         DataOut : out  STD_LOGIC_VECTOR (7 downto 0)
21     );
22 end ShiftRegisterFPGA;
23
24 architecture Structural of ShiftRegisterFPGA is
25
26
27 COMPONENT shiftregister
28     PORT (
29         X : in  STD_LOGIC_VECTOR (7 downto 0);
30         clock_50MHz, reset,Load,enable : in  STD_LOGIC;
31         Bitout : out STD_LOGIC:='0';
32         DataOut : out  STD_LOGIC_VECTOR (7 downto 0)

```

```
33
34 );
35 END COMPONENT;
36
37 COMPONENT debouncer
38   PORT(
39     clock, reset: in std_logic;
40     data_in: in std_logic;
41     data_out: out std_logic
42   );
43
44 END COMPONENT;
45
46
47 signal t1, t2 : std_logic_vector(7 downto 0);
48 signal reset_ff, c: std_logic := '0';
49
50
51 begin
52
53 DEB: debouncer PORT MAP (
54
55   clock=>clock_50MHz,
56   reset=>reset,
57   data_in=>shift,
58   data_out=>c
59
60
61 );
62
63
64
65 SH: shiftregister PORT MAP (
66   X=>X,
67   clock_50MHz=>clock_50MHz,
68   reset=>reset_ff,
69   enable=>c,
70   Load=>Load,
71   Bitout=>Bitout,
72   DataOut=>DataOut
73
74 );
75
76
77 p: process (clock_50MHz)
78
79 begin
80
81
```

```


82 if(rising_edge(clock_50MHz)) then
83     if (reset='1') then
84         reset_ff<='1';
85
86     elsif( Load='1') then
87         reset_ff<='0';
88
89
90     end if;
91
92 end if;
93 end process;
94
95 end Structural;

```

Codice Componente 5.4: Definizione del file UCF
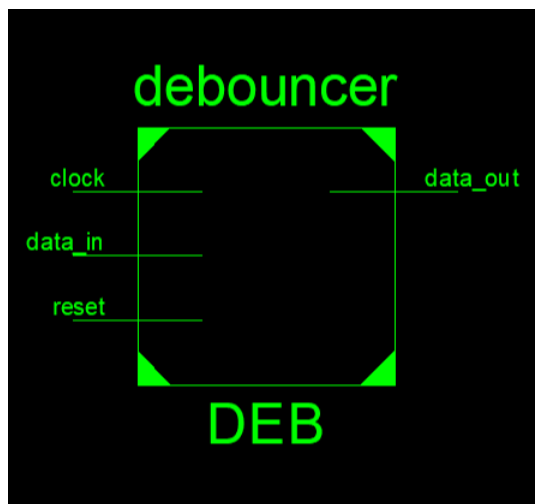
#### 5.4.0.1 Debouncer

Il componente debouncer permette di generare un unico impulso di durata pari al periodo del segnale di clock che esso prende in ingresso. Esso ci permette, alla pressione di un determinato bottone, di considerare quella pressione come un unico impulso in ingresso al nostro sistema (data l'elevata frequenza del clock). In questo caso è utilizzato per il bottone di shift, che corrisponde all' input data\_in.



```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4 use ieee.std_logic_unsigned.all;
5
6 entity debouncer is
7     port (
8         clock, reset: in std_logic;

```

```
9   data_in: in std_logic;
10  data_out: out std_logic
11  );
12
13  end debouncer;
14
15  architecture Behavioral of debouncer is
16  signal s1,s2,slow_clk_enable: std_logic := '0';
17  signal counter: integer:=1;
18
19  begin
20
21  proc1: process(clock,reset)
22  begin
23      if(reset='1') then
24          counter <= 1;
25          slow_clk_enable <= '0';
26      elsif(rising_edge(clock)) then
27          if(counter =1000000) then
28              counter <= 1;
29              slow_clk_enable <= '1';
30          else
31              slow_clk_enable <= '0';
32              counter <= counter + 1;
33          end if;
34      end if;
35
36  end process;
37
38
39  proc2: process (clock,reset)
40  begin
41      if (reset='1') then
42          s1<='0';
43          s2<='0';
44      elsif (rising_edge(clock)) then
45          if(slow_clk_enable='1') then
46              s1<= data_in;
47              s2<=s1;
48          end if;
49      end if;
50
51
52  end process;
53
54  data_out<= s1 and (not s2) and slow_clk_enable;
55
56  end Behavioral;
```

## Codice Componente 5.5: Definizione del componente FFD con reset

## 5.4.0.2 File UCF

```

1
2
3 NET "clock_50MHz" LOC = "B8"; # Bank = 0, Pin name = IP_L13P_0/GCLK8, Type
  = GCLK, Sch name = GCLK0
4
5 NET "X<0>" LOC = "G18"; # Sch name = SW0
6 NET "X<1>" LOC = "H18"; # Sch name = SW1
7 NET "X<2>" LOC = "K18"; # Sch name = SW2
8 NET "X<3>" LOC = "K17"; # Sch name = SW3
9 NET "X<4>" LOC = "L14";
10 NET "X<5>" LOC = "L13";
11 NET "X<6>" LOC = "N17";
12 NET "X<7>" LOC = "R17";
13
14
15 NET "Load" LOC = "H13";
16 NET "reset" LOC = "E18";
17 NET "shift" LOC = "D18";
18
19 NET "DataOut<0>" LOC = "J14";
20 NET "DataOut<1>" LOC = "J15";
21 NET "DataOut<2>" LOC = "K15";
22 NET "DataOut<3>" LOC = "K14";
23 NET "DataOut<4>" LOC = "E16";
24 NET "DataOut<5>" LOC = "P16";
25 NET "DataOut<6>" LOC = "E4";
26 NET "DataOut<7>" LOC = "P4";

```

## Codice Componente 5.6: Definizione del file UCF

# Capitolo 6

## Esercizio 6


### 6.1 Traccia

Progettare ed implementare in VHDL un contatore mod-16 nella modalità serie e parallelo. Sintetizzare sulla board il componente (nella sola modalità serie) utilizzando un bottone per acquisire il segnale di conteggio e 2 cifre del display per visualizzare il contenuto del registro.
 
### 6.2 Soluzione


La soluzione proposta mostra i contatori in parallelo e serie realizzati con flip flop di tipo T (fronte di discesa), dotati di ingresso T, CLK e Reset e di uscita Q.

Di seguito viene mostrato un esempio di contatore seriale.



Tale soluzione sfrutta le proprietà del flip flop T per costruire un contatore in serie. Nel nostro caso i flip flop utilizzati saranno 4 poichè è richiesto un contatore modulo 16. Come si può osservare, il clock viene dato in ingresso solamente al primo flip flop. Tutti gli altri avranno clock pari all'uscita del precedente e tutti avranno ingresso T pari al valore logico '1'.

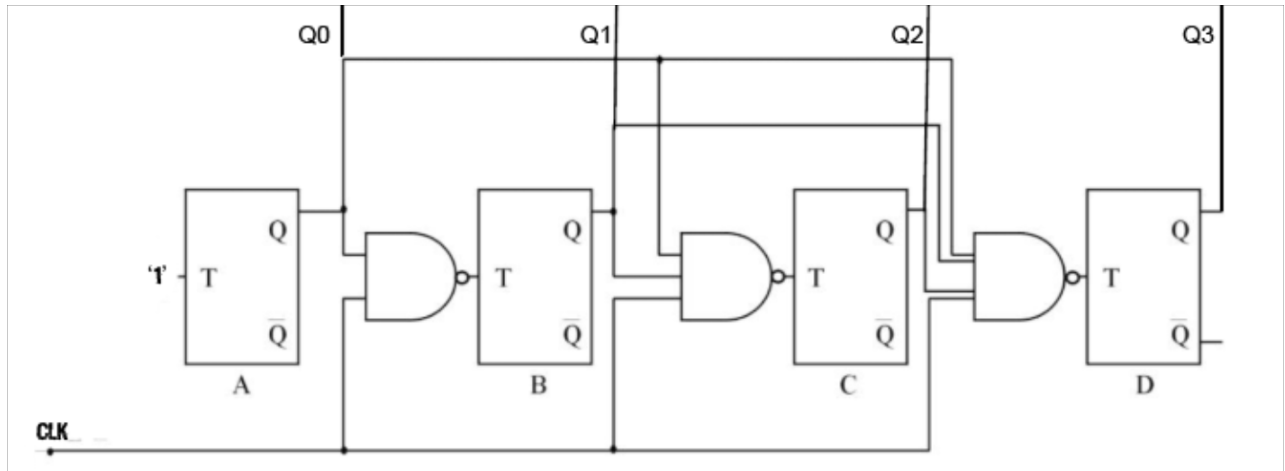
Per quanto riguarda il contatore parallelo invece abbiamo una situazione di questo tipo:



Lo stesso clock va in ingresso a tutti i flip flop della catena. Un flip flop commuta quando i precedenti hanno commutato ed il clock è alto.

## 6.2.1 Schematici

### 6.2.1.1 Flip Flop T

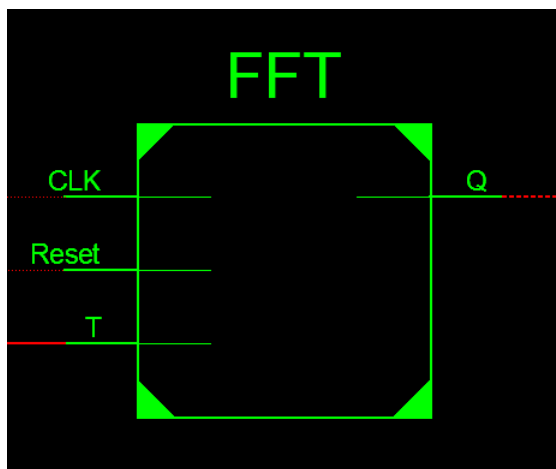


# contatore\_parallelo


The diagram shows a black rectangular block representing a parallel counter. It has two input lines on the left: 'clock\_50Mhz' at the top and 'RESET' below it. It has one output line on the right labeled 'Y(0:3)'. The four corners of the block are marked with small red triangles.


# contatore\_parallelo



 

### 6.2.1.3 Contatore Seriale Mod-16

 

 

## 6.2.2 Codice

Di seguito è riportato il codice dei flip flop utilizzati e dei contatori in parallelo e serie, questi ultimi realizzati con una descrizione di tipo structural.

### 6.2.2.1 Flip Flop T

I flip flop utilizzati per l'implementazione dei contatori sono flip flop di tipo T sensibili al fronte di discesa del clock. Ad ogni colpo di clock l'uscita è calcolata attraverso una XOR tra il segnale di ingresso T e il segnale temporaneo calcolato precedentemente, che viene posto a 0 in caso di reset.

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4
5  entity FFT is port (
6
7      T,Reset,CLK: in std_logic;
8      Q: out std_logic
9  );
10 end FFT;
11
12 architecture Behavioral of FFT is
13     signal temp: std_logic := '0';
14
15 begin
16     process (Reset,CLK)
17
18     begin
19         if Reset='1' then
20             temp <= '0';

```

```

21
22 elsif (falling_edge(CLK)) then
23     temp <= T xor temp;
24 end if;
25
26 end process;
27
28 Q <= temp;
29 end Behavioral;

```

Codice Componente 6.1: Definizione del flip flop T

### 6.2.2.2 Contatore Parallelo Mod-16

```

1
2
3 library IEEE;
4 use IEEE.STD_LOGIC_1164.ALL;
5     use ieee.std_logic_unsigned.all;
6     library UNISIM;
7 use UNISIM.Vcomponents.ALL;
8
9 entity contatore_parallelo is
10
11 port (
12     clock_50Mhz : in std_logic;
13     RESET : in std_logic;
14     Y : out std_logic_vector(0 to 3)
15 );
16
17 end contatore_parallelo;
18
19 architecture Structural of contatore_parallelo is
20
21
22
23 Component FFT
24     port ( CLK : in     std_logic;
25           T   : in     std_logic;
26           reset : in std_logic;
27           Q   : out    std_logic
28
29
30         );
31 end Component;
32
33 signal t:  std_logic_vector (6 downto 0) := (others => '0') ;
34

```

```
35
36 begin
37
38
39 FFT0 : FFT port map (
40     T => '1',
41     CLK => clock_50Mhz,
42     Q => t(0),
43     reset => reset
44 );
45
46 AND_2 : AND2
47     port map (I0=>t(0),
48               I1=>clock_50Mhz,
49               O=>t(1));
50
51
52 FFT1 : FFT port map (
53     T => t(1),
54     CLK => clock_50Mhz,
55     Q => t(2),
56
57     reset => reset
58 );
59
60 AND_3 : AND3
61     port map (I0=>t(0),
62               I1=>t(2),
63               I2 =>clock_50Mhz,
64               O=>t(3));
65
66
67
68 FFT2 : FFT port map (
69     T => t(3),
70     CLK => clock_50Mhz,
71     Q => t(4),
72     reset => reset
73 );
74
75 AND_4 : AND4
76     port map (I0=>t(0),
77               I1=>t(2),
78               I2 =>t(4),
79               I3 =>clock_50Mhz,
80               O=>t(5));
81
82 FFT3 : FFT port map (
83     T => t(5),
```

```

84     CLK => clock_50Mhz,
85     Q => t(6),
86     reset => reset
87 );
88
89 Y <= t(6) & t(4) & t(2) & t(0);
90
91 end Structural;

```

Codice Componente 6.2: Definizione del contatore parallelo

### 6.2.2.3 Contatore in serie Mod-16

```

1
2
3
4 library IEEE;
5 use IEEE.STD_LOGIC_1164.ALL;
6 use ieee.std_logic_unsigned.all;
7 library UNISIM;
8 use UNISIM.Vcomponents.ALL;
9
10 entity contatore_serie is
11
12 port (
13     clock_50Mhz : in std_logic;
14     RESET : in std_logic;
15     Y : out std_logic_vector(3 downto 0)
16 );
17
18 end contatore_serie;
19
20 architecture Structural of contatore_serie is
21
22 Component FFT
23     port ( CLK : in std_logic;
24           T : in std_logic;
25           reset : in std_logic;
26           Q : out std_logic
27           );
28 end Component;
29
30 signal t: std_logic_vector (3 downto 0) := (others => '0') ;
31
32
33 begin
34
35

```

```

36 FFT0 : FFT port map (
37     T => '1',
38     CLK => clock_50Mhz,
39     Q => t(0),
40     reset => reset
41 );
42
43 FFT1 : FFT port map (
44     T => '1',
45     CLK => t(0),
46     Q => t(1),
47     reset => reset
48 );
49
50 FFT2 : FFT port map (
51     T => '1',
52     CLK => t(1),
53     Q => t(2),
54
55     reset => reset
56 );
57
58 FFT3 : FFT port map (
59     T => '1',
60     CLK => t(2),
61     Q => t(3),
62     reset => reset
63 );
64
65 Y <= t;
66
67 end Structural;

```

Codice Componente 6.3: Definizione del contatore in serie

## 6.3 Simulazione

È stato eseguito lo stesso testbench per entrambi i contatori. Si riporta di seguito quello relativo al contatore parallelo. Il conteggio viene fatto partire per 100 ns e poi viene testato il reset.

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3
4
5  ENTITY test IS
6  END test;
7
8  ARCHITECTURE behavior OF test IS

```

```


9
10
11 COMPONENT contatore_parallelo
12 PORT(
13     clock_50Mhz : IN  std_logic;
14     RESET : IN  std_logic;
15     Y : OUT  std_logic_vector(0 to 3)
16 );
17 END COMPONENT;
18
19
20 --Inputs
21 signal clock_50Mhz : std_logic := '0';
22 signal RESET : std_logic := '0';
23
24 --Outputs
25 signal Y : std_logic_vector(0 to 3);
26
27 -- Clock period definitions
28 constant clock_50Mhz_period : time := 10 ns;
29
30 BEGIN
31
32 uut: contatore_parallelo PORT MAP (
33     clock_50Mhz => clock_50Mhz,
34     RESET => RESET,
35     Y => Y
36 );
37
38 -- Clock process definitions
39 clock_50Mhz_process : process
40 begin
41     clock_50Mhz <= '0';
42     wait for clock_50Mhz_period/2;
43     clock_50Mhz <= '1';
44     wait for clock_50Mhz_period/2;
45 end process;
46
47
48 stim_proc: process
49 begin
50
51     wait for 100 ns;
52     reset <= '1';
53     wait for 100 ns;
54     reset <= '0';
55
56     wait;
57 end process;

```


58  
59 `END;`

Codice Componente 6.4: Definizione del testbench contatore parallelo

### 6.3.0.1 Test Contatore Parallelo

 

### 6.3.0.2 Test Contatore Serie

 


## 6.4 Sintesi su board FPGA

Per la sintesi su FPGA del contatore in serie, sono stati importati diversi componenti, tra cui: display a 7 segmenti, debouncer e componente bin2bcd.
 
### 6.4.1 Bin2bcd

Il componente bint2bcd permette di ottenere, a partire da un input binario, un output che può essere mostrato sul display a 7 segmenti in digitale.



```
1
2 library ieee;
3 use ieee.std_logic_1164.all;
4 use ieee.numeric_std.all;
5 use IEEE.std_logic_unsigned.all;
```



```



6
7 entity bin2bcd is
8     port ( input:      in   std_logic_vector (15 downto 0);
9           output: out std_logic_vector (15 downto 0)
10 );
11 end entity;
12
13 architecture behavioural of bin2bcd is
14     alias data: std_logic_vector (15 downto 0) is input;
15
16 begin
17     process (data)
18         variable bcd:  std_logic_vector (15 downto 0);
19         variable bint: std_logic_vector (13 downto 0);
20     begin
21         bcd := (others => '0');
22         bint := data (13 downto 0);
23
24         for i in 0 to 13 loop
25             bcd(15 downto 1) := bcd(14 downto 0);
26             bcd(0) := bint(13);
27             bint(13 downto 1) := bint(12 downto 0);
28             bint(0) := '0';
29
30             if i < 13 and bcd(3 downto 0) > "0100" then
31                 bcd(3 downto 0) := (bcd(3 downto 0)) + 3;
32             end if;
33             if i < 13 and bcd(7 downto 4) > "0100" then
34                 bcd(7 downto 4) := (bcd(7 downto 4)) + 3;
35             end if;
36             if i < 13 and bcd(11 downto 8) > "0100" then
37                 bcd(11 downto 8) := (bcd(11 downto 8)) + 3;
38             end if;
39             if i < 13 and bcd(15 downto 12) > "0100" then
40                 bcd(15 downto 12) := (bcd(15 downto 12)) + 3;
41             end if;
42         end loop;
43
44         output<= bcd;
45
46     end process ;
47 end architecture;

```

Codice Componente 6.5: Definizione bin2bcd
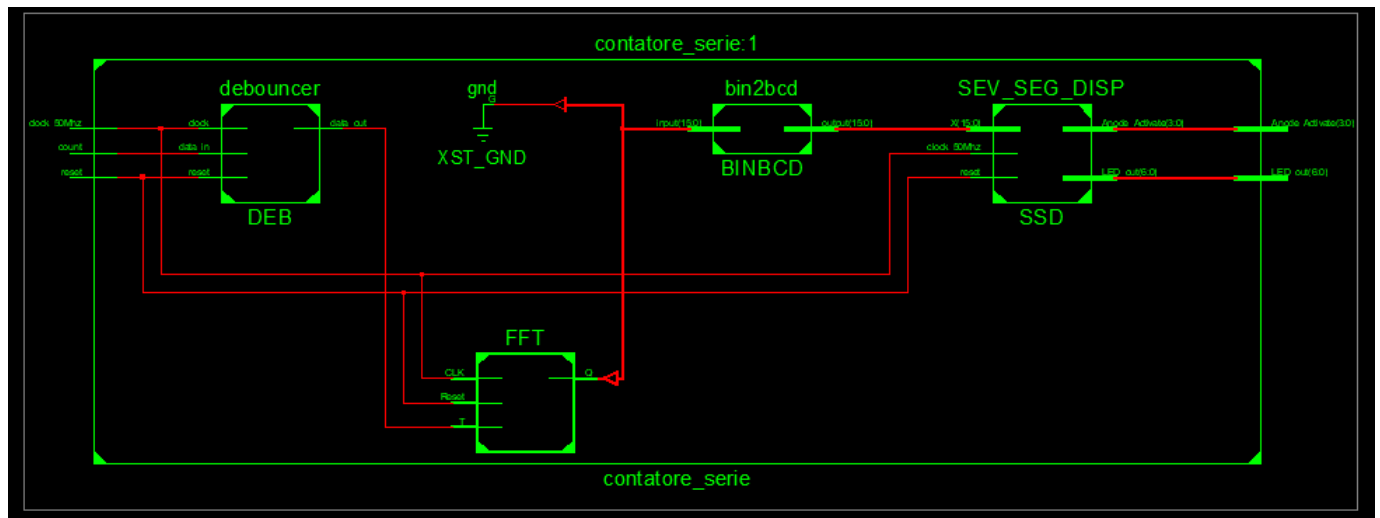 
## 6.4.2 Sintesi finale

Il contatore presenta in ingresso il clock, il reset e il segnale di conteggio; le uscite sono quelle del display a 7 segmenti.



```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4 use ieee.std_logic_unsigned.all;
5 library UNISIM;
6 use UNISIM.Vcomponents.ALL;
7
8 entity contatore_serie is
9
10 port (
11     clock_50Mhz : in std_logic;
12     reset : in std_logic;
13     count: in std_logic;
14     Anode_Activate : out STD_LOGIC_VECTOR (3 downto 0);
15     LED_out : out STD_LOGIC_VECTOR (6 downto 0)
16 );
17 end contatore_serie;
18

```

```

19 architecture Structural of contatore_serie is
20
21 Component FFT
22     port ( CLK : in    std_logic;
23           T   : in    std_logic;
24           reset : in std_logic;
25           Q   : out   std_logic
26 );
27 end Component;
28
29 Component debouncer
30     port ( clock, reset: in std_logic;
31           data_in: in std_logic;
32           data_out: out std_logic
33 );
34 end Component;
35
36 component bin2bcd is
37     port (
38         input: in  std_logic_vector (15 downto 0);
39         output: out std_logic_vector (15 downto 0)
40 );
41 end component;
42
43 component SEV_SEG_DISP is
44     Port ( clock_50Mhz : in STD_LOGIC;
45           reset : in STD_LOGIC;
46           X : in STD_LOGIC_VECTOR (15 downto 0);
47           Anode_Activate : out STD_LOGIC_VECTOR (3 downto 0);
48           LED_out : out STD_LOGIC_VECTOR (6 downto 0)
49 );
50 end component;
51
52 signal t: std_logic_vector (3 downto 0) := (others => '0');
53 signal value_to_display : std_logic_vector (15 downto 0);
54 signal value_converted : std_logic_vector (15 downto 0);
55 signal c: std_logic := '0';
56 constant ZERO : std_logic_vector(11 downto 0) := (others => '0');
57
58 begin
59
60 FFT0 : FFT port map (
61     T => c,
62     CLK => clock_50Mhz,
63     Q => t(0),
64     reset => reset
65 );
66
67 FFT1 : FFT port map (

```

```

68     T => '1',
69     CLK => t(0),
70     Q => t(1),
71     reset => reset
72 );
73
74 FFT2 : FFT port map (
75     T => '1',
76     CLK => t(1),
77     Q => t(2),
78     reset => reset
79 );
80
81 FFT3 : FFT port map (
82     T => '1',
83     CLK => t(2),
84     Q => t(3),
85     reset => reset
86 );
87
88 BINBCD : bin2bcd port map(
89     input => value_to_display,
90     output => value_converted);
91
92 SSD : SEV_SEG_DISP port map(
93     clock_50Mhz => clock_50Mhz,
94     reset => reset,
95     Anode_Activate => Anode_Activate,
96     LED_out => LED_out,
97     X => value_converted );
98
99 DEB: DEBOUNCER port map(
100     clock=>clock_50Mhz,
101     reset=>reset,
102     data_in=>count,
103     data_out=>c
104 );
105
106 value_to_display <= ZERO & t;
107 end Structural;

```

Codice Componente 6.6: Sintesi del contatore in serie

### 6.4.3 File UCF

```

1
2 NET "LED_out<6>" LOC = "L18"; # Bank = 1, Pin name = IO_L10P_1, Type = I/O,
  Sch name = CA


```

```

3 NET "LED_out<5>" LOC = "F18"; # Bank = 1, Pin name = IO_L19P_1, Type = I/O,
  Sch name = CB
4 NET "LED_out<4>" LOC = "D17"; # Bank = 1, Pin name = IO_L23P_1/HDC, Type =
  DUAL, Sch name = CC
5 NET "LED_out<3>" LOC = "D16"; # Bank = 1, Pin name = IO_L23N_1/LDC0, Type =
  DUAL, Sch name = CD
6 NET "LED_out<2>" LOC = "G14"; # Bank = 1, Pin name = IO_L20P_1, Type = I/O,
  Sch name = CE
7 NET "LED_out<1>" LOC = "J17"; # Bank = 1, Pin name = IO_L13P_1/A6/RHCLK4/
  IRDY1, Type = RHCLK/DUAL, Sch name = CF
8 NET "LED_out<0>" LOC = "H14"; # Bank = 1, Pin name = IO_L17P_1, Type = I/O,
  Sch name = CG
9
10 NET "clock_50Mhz" LOC = "B8"; # Bank = 0, Pin name = IP_L13P_0/GCLK8, Type
  = GCLK, Sch name = GCLK0
11 NET "Anode_Activate<0>" LOC = "F17"; # Bank = 1, Pin name = IO_L19N_1, Type
  = I/O, Sch name = AN0
12 NET "Anode_Activate<1>" LOC = "H17"; # Bank = 1, Pin name = IO_L16N_1/A0,
  Type = DUAL, Sch name = AN1
13 NET "Anode_Activate<2>" LOC = "C18"; # Bank = 1, Pin name = IO_L24P_1/LDC1,
  Type = DUAL, Sch name = AN2
14 NET "Anode_Activate<3>" LOC = "F15"; # Bank = 1, Pin name = IO_L21P_1, Type
  = I/O, Sch name = AN3
15
16
17 NET "count" LOC = "B18";
18 NET "reset" LOC = "D18";

```

Codice Componente 6.7: UCF contatore

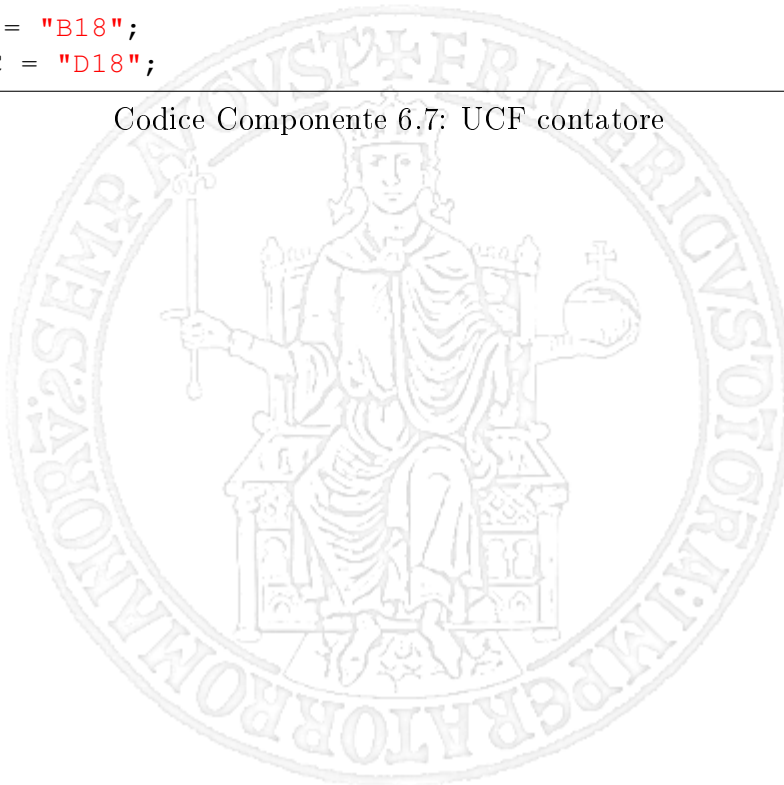

# Capitolo 7

## Esercizio 7

### 7.1 Traccia

Progettare ed implementare in VHDL un “arbitro 2 su 3”, ossia un componente che, presi due input binari in ingresso, fornisce in uscita un valore binario pari a quello che compare almeno 2 volte su 3 in ingresso. Sintetizzare sulla board il componente utilizzando gli switch per acquisire gli ingressi e un led per visualizzare il risultato.

### 7.2 Soluzione

Il funzionamento dell’arbitro 2 su 3 da implementare è descritto nella seguente tabella di verità

A0	A1	A2	U
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Il calcolo della funzione minimizzata tramite mappa di Karnaugh risulta essere :

$$U = A_2A_3 \vee A_1A_3 \vee A_1A_2$$

È stato utilizzato il tool sis per la verifica dell’espressione ottenuta:


```


UC Berkeley, SIS 1.2 (compiled May 21 2002 09:23:42)
sis> read_blif arbitro.blif
sis> write_blif
.model arbitro
.inputs A1 A2 A3
.outputs U
.names A1 A2 A3 U
111 1
011 1
101 1
110 1
.end
sis> write_eqn
INORDER = A1 A2 A3;
OUTORDER = U;
U = A1*A2*!A3 + A1*!A2*A3 + !A1*A2*A3 + A1*A2*A3;
sis> print_stats
arbitro pi= 3 po= 1 node= 1 latch= 0 lits(sop)= 12 lits(ff)= 9
sis> simplify
sis> write_eqn
INORDER = A1 A2 A3;
OUTORDER = U;
U = A2*A3 + A1*A3 + A1*A2;
sis> print_stats
arbitro pi= 3 po= 1 node= 1 latch= 0 lits(sop)= 6 lits(ff)= 5
sis>

```
 
### 7.2.1 Schematici

Lo schematico presenta 3 ingressi A1, A2 ed A3 ed un'unica uscita U, che è alta se vi sono almeno due bit pari a '1' in ingresso.



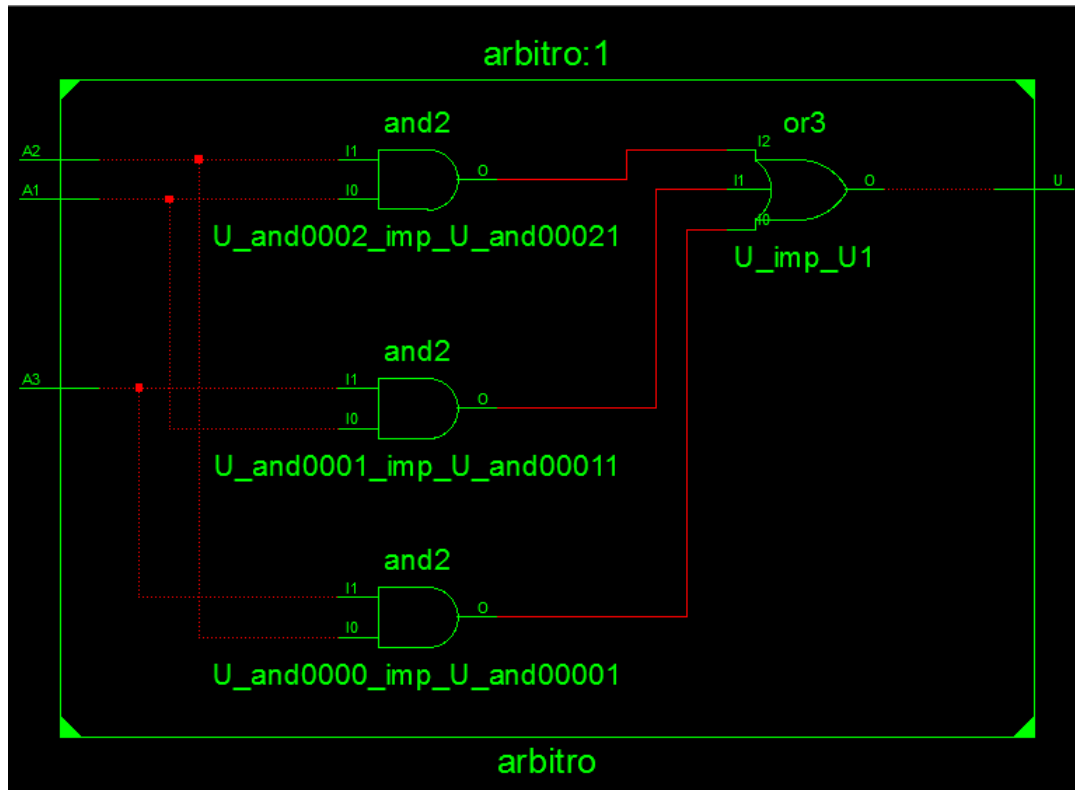

## 7.2.2 Codice

L'espressione minimizzata è stata tradotta con una descrizione dataflow.

### 7.2.2.1 Arbitro 2 su 3

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity arbitro is
5      Port ( A1 : in  STD_LOGIC;
6             A2 : in  STD_LOGIC;
7             A3 : in  STD_LOGIC;
8             U  : out STD_LOGIC
9          );
10 end arbitro;
11
12 architecture Dataflow of arbitro is
13
14 begin
15
16 U <= (A2 AND A3) OR (A1 AND A3) OR (A1 AND A2);
17
18 end Dataflow;

```

Codice Componente 7.1: Definizione del componente Arbitro 2 su 3



## 7.3 Simulazione

Nel caso in esame, essendo 8 le combinazioni totali in input da verificare possiamo fornire un testbench completo. I risultati attesi corrispondono a quelli della tabella di verità mostrata nel paragrafo precedente.

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3
4  ENTITY test IS
5  END test;
6
7  ARCHITECTURE behavior OF test IS
8
9      COMPONENT arbitro
10     PORT (
11         A1 : IN  std_logic;
12         A2 : IN  std_logic;
13         A3 : IN  std_logic;
14         U : OUT std_logic
15     );
16     END COMPONENT;
17
18
19     --Inputs
20     signal A1 : std_logic := '0';
21     signal A2 : std_logic := '0';
22     signal A3 : std_logic := '0';
23
24     --Outputs
25     signal U : std_logic;
26
27
28 BEGIN
29
30     uut: arbitro PORT MAP (
31         A1 => A1,
32         A2 => A2,
33         A3 => A3,
34         U => U
35     );
36
37
38     stim_proc: process
39     begin
40         -- hold reset state for 100 ns.
41         wait for 100 ns;
42         A1 <= '0';
43         A2 <= '0';

```


```

44   A3 <= '0';
45   wait for 100 ns;
46   A1 <= '0';
47   A2 <= '0';
48   A3 <= '1';
49   wait for 100 ns;
50   A1 <= '0';
51   A2 <= '1';
52   A3 <= '0';
53   wait for 100 ns;
54   A1 <= '0';
55   A2 <= '1';
56   A3 <= '1';
57   wait for 100 ns;
58   A1 <= '1';
59   A2 <= '0';
60   A3 <= '0';
61   wait for 100 ns;
62   A1 <= '1';
63   A2 <= '0';
64   A3 <= '1';
65   wait for 100 ns;
66   A1 <= '1';
67   A2 <= '1';
68   A3 <= '0';
69   wait for 100 ns;
70   A1 <= '1';
71   A2 <= '1';
72   A3 <= '1';
73
74   wait;
75   end process;
76
77   END;

```

Codice Componente 7.2: Definizione del testbench per Arbitro 2 su 3

 I risultati del test mostrano come varia U rispetto agli ingressi A1,A2,A3. Da una semplice analisi si evince che la macchina si comporta da arbitro 2 su 3.




## 7.4 Sintesi su board FPGA

Per sintetizzare la macchina su schedino NEXYS 2 è sufficiente mappare i segnali A1,A2,A3 con gli switch SW0,SW1,SW2 e l'uscita U col led LED0.

```
1 NET "A1"      LOC = "G18";    # Sch name = SW0
2 NET "A2"      LOC = "H18";    # Sch name = SW1
3 NET "A3"      LOC = "K18";    # Sch name = SW2
4
5 NET "U" LOC = "J14"; #Sch name LD0
```

 Codice Componente 7.3: Definizione del file UCF



# Capitolo 8

## Esercizio 8

### 8.1 Traccia

Progettare ed implementare un orologio che, a partire da un clock di riferimento che opera da base dei tempi di adeguata precisione, genera mediante uso di contatori il secondo, il minuto e l'ora. L'orologio deve essere sintetizzato su FPGA e la visualizzazione dell'ora deve sfruttare le 4 cifre del display e i led messi a disposizione dalla board di sviluppo, secondo la seguente modalità:



- i minuti (da 1 a 60) e le ore (da 1 a 24) sono visualizzati in formato 8-4-2-1 mediante le due cifre rispettivamente meno e più significative del display a 4 cifre a sette segmenti;
- i secondi (da 1 a 60) sono visualizzati utilizzando i quattro led di peso meno significativo dell'array di led presenti nella scheda

Il valore del tempo deve poter essere inizializzato acquisendo, in sequenza e tramite gli switch, i valori dell'ora, del minuti e dei secondi.

### 8.2 Soluzione e sintesi

L'orologio viene implementato con 3 contatori collegati in parallelo. Essi contano ore, minuti e secondi (rappresentati su 8 bit) e vengono inizializzati tramite il segnale logico di set. In particolare set stabilisce il valore di conteggio corrente del singolo contatore e, quando il segnale di enable sarà alto, partirà poi a contare fino al valore impostato tramite interfaccia generic. Al raggiungimento di questo valore, viene generato un segnale di fine conteggio e scatta il contatore successivo. Il segnale di fine conteggio (count\_end) uscente dal contatore viene posto in AND col clock di base per consentire la sincronizzazione tra i vari componenti.

### 8.2.1 Schematici

 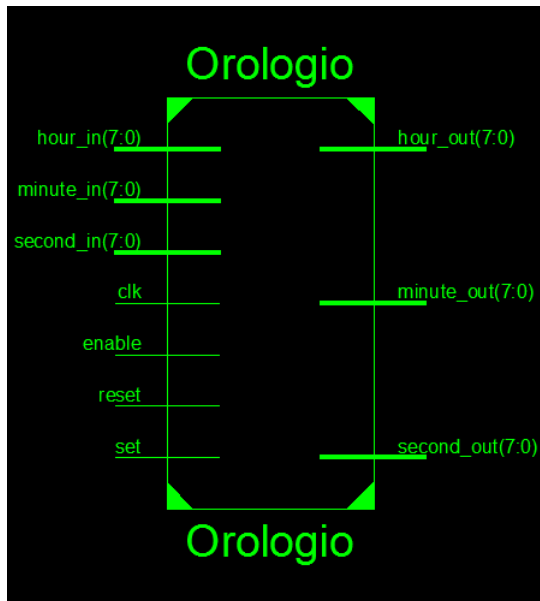

### 8.2.2 Codice

Il componente principale Orologio connette tra loro i tre contatori e imposta il valore limite di conteggio tramite la loro interfaccia generic. Come già detto essi sono tra loro connessi tramite porte logiche AND2 e AND3, che ne gestiscono la sincronizzazione.

#### 8.2.2.1 Orologio

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use ieee.numeric_std.all;
4  use IEEE.std_logic_unsigned.all;

```

```

6
7
8 entity Orologio is
9     Port ( hour_in, minute_in, second_in : in std_logic_vector (7 downto 0);
10           clk,enable,reset,set : in STD_LOGIC;
11           hour_out, minute_out, second_out : out std_logic_vector (7 downto 0)
12     );
13 end Orologio;
14
15 architecture Behavioral of Orologio is
16
17 Component contatore
18 Generic (N: integer);
19 port (
20
21     reset : in STD_LOGIC;
22     clk,enable,set : in STD_LOGIC;
23     datain: in STD_LOGIC_VECTOR(7 downto 0);
24     count : out STD_LOGIC_VECTOR(7 downto 0);
25     count_end : out STD_LOGIC
26
27 );
28 end component;
29
30 signal second :std_logic_vector (7 downto 0) := (others=>'0');
31 signal minute :std_logic_vector (7 downto 0) := (others=>'0');
32 signal hour :std_logic_vector (7 downto 0) := (others=>'0');
33 signal en1,en2,cc1,cc2,cc3: std_logic:='0';
34
35 begin
36
37
38 CH:contatore generic map(24) port map(
39     reset=>reset,
40     clk=>clk,
41     enable=>en2,
42     set=>set,
43     datain=>hour_in,
44     count=>hour,
45     count_end=>cc3
46
47 );
48
49
50 CM:contatore generic map(60) port map(
51     reset=>reset,
52     clk=>clk,
53     enable=>en1,
54     set=>set,

```

```

55     datain=>minute_in,
56     count=>minute,
57     count_end=>cc2
58
59 );
60
61
62
63 CS:contatore generic map(60) port map(
64     reset=>reset,
65     clk=>clk,
66     enable=>enable,
67     set=>set,
68     datain=>second_in,
69     count=>second,
70     count_end=>ccl
71
72 );
73
74
75 en1<=ccl and clk;
76 en2<=ccl and cc2 and clk;
77 second_out <= second;
78 minute_out <= minute;
79 hour_out <= hour;
80
81
82 end Behavioral;

```

Codice Componente 8.1: Definizione del componente Orologio

### 8.2.2.2 Contatore

Il contatore prende in ingresso diversi segnali, tra cui enable per iniziare il conteggio e set per impostarne il valore di partenza preso in ingresso da datain. L'interfaccia generic ci consente di stabilire un limite di conteggio, dopodichè il contatore riparte da 0. Il segnale di reset pone a 0 il conteggio e il valore di count\_end.

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4 use IEEE.NUMERIC_STD.ALL;
5 use IEEE.std_logic_arith.all;
6 use IEEE.MATH_REAL.all;
7
8
9 entity contatore is
10 Generic (N: integer);
11 Port (

```

```

12     reset : in STD_LOGIC;
13     clk,enable,set : in STD_LOGIC;
14     datain: in STD_LOGIC_VECTOR(7 downto 0);
15     count : out STD_LOGIC_VECTOR(7 downto 0);
16     count_end : out STD_LOGIC
17 );
18 end contatore;
19
20 architecture Behavioral of contatore is
21
22 begin
23
24 process (clk,reset,enable)
25 variable cnt: integer range 0 to N-1:=0;
26
27 begin
28
29 if (reset='1') then
30     cnt:=0;
31     count_end<='0';
32
33 elsif (set='1') then
34     cnt:= TO_INTEGER(unsigned(datain));
35
36 elsif falling_edge(clk) then
37
38     if(enable='1')then
39         if (cnt=N-1) then
40             cnt:=0;
41             count_end<='1';
42         else
43             cnt:= cnt+1;
44             count_end<='0';
45         end if;
46
47     end if;
48
49 end if;
50
51 count<=CONV_STD_LOGIC_VECTOR (cnt,8);
52
53 end process;
54
55 end Behavioral;

```

Codice Componente 8.2: Definizione del componente counter



### 8.2.2.3 Orologio FPGA

I componenti usati per la sintetizzazione sono : Display a 7 segmenti, convertitore bin to bcd, il counter visto precedentemente e il divisore di clock. I segnali vengono inseriti tramite gli switch (codificati su 8 bit) e acquisiti tramite i bottoni della board. La pressione finale del pulsante pone il segnale di enable a 1 e dà inizio al conteggio, partendo dai valori che sono stati immessi.

Il divisore di clock, il cui codice è mostrato in questa sezione, prende in ingresso il clock a 50 Mhz della board e restituisce in uscita un clock le cui finestre temporali sono pari a 1 secondo. Tale delay viene creato tramite un segnale temporaneo che, quando il contatore arriva a 25'000'000, viene negato. Tale valore limite di conteggio viene calcolato attraverso il fattore di scala :

$$Scale = \frac{f_{in}}{f_{out}}$$

La macchina a stati implementata nel process è composta da 4 stati (A, B, C, D). I primi 3 permettono di inserire rispettivamente ore, minuti e secondi usando gli switch della board e premendo l'apposito bottone di load (BTN\_NEXT). Successivamente lo stato D pone ad '1' il segnale Enable\_out del componente counter che dà inizio al conteggio. Sono stati usati due bin2bcd che prendono in ingresso i valori di output del componente counter (ore e minuti) e li convertono. Questi valori sono poi posti in ingresso al display a 7 segmenti. I secondi vengono semplicemente mostrati sui led. Il segnale di reset pone a 0 Enable\_out, ore, minuti e secondi e riporta la macchina nello stato A.

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4
5 entity orologioFPGA is
6     Port ( BTN_NEXT : in STD_LOGIC;
7           BTN_RESET : in STD_LOGIC;
8           clock_50Mhz : in STD_LOGIC;
9           X : in STD_LOGIC_VECTOR(7 downto 0);
10          Anode_Activate : out STD_LOGIC_VECTOR (3 downto 0); -- 4 Anode signals
11          LED_out : out STD_LOGIC_VECTOR (6 downto 0);
12          LDS : out STD_LOGIC_VECTOR (3 downto 0)
13
14 );
15 end orologioFPGA;
16
17 architecture Behavioral of orologioFPGA is
18
19 type State_type is (A, B, C, D); -- Define the states
20 signal State : State_Type := A;
21
22
23 signal hour_t, minute_t, second_t : STD_LOGIC_VECTOR(7 downto 0) := (others
    => '0');
24 signal enable_out_t : STD_LOGIC := '0';
25 signal set_t : STD_LOGIC := '1';

```

```

26 signal clock_div, c1 : STD_LOGIC := '0';
27
28 signal h,m,s : std_logic_vector (7 downto 0) := (others =>'0');
29
30 signal hour_conv,min_conv : STD_LOGIC_VECTOR(11 downto 0) := (others
    =>'0');
31
32 component Orologio is
33     Port ( hour_in, minute_in,second_in : in std_logic_vector (7 downto 0);
34           clk, enable,reset,set : in STD_LOGIC;
35           hour_out, minute_out, second_out: out std_logic_vector (7 downto 0)
36     );
37 end component;
38
39
40 Component debouncer
41     port (
42         clock, reset: in std_logic;
43         data_in: in std_logic;
44         data_out: out std_logic
45     );
46
47 end Component;
48
49 Component Clock_Divider
50 port (
51     clk,reset: in std_logic;
52     clock_out: out std_logic
53 );
54 end Component;
55
56 component bin2bcd is
57     port (
58         bin: in std_logic_vector (7 downto 0);
59         bcd: out std_logic_vector (11 downto 0)
60     );
61 end component;
62
63 component SEV_SEG_DISP is
64     Port ( clock_50Mhz : in STD_LOGIC;
65           reset : in STD_LOGIC; -- reset
66           Anode_Activate : out STD_LOGIC_VECTOR (3 downto 0); -- 4 Anode
               signals
67           LED_out : out STD_LOGIC_VECTOR (6 downto 0);
68           X : in STD_LOGIC_VECTOR (15 downto 0)
69     );
70
71 end component;
72

```

```
73
74
75 begin
76
77
78 CT : Orologio port map(
79     hour_in => hour_t,
80     minute_in => minute_t,
81     second_in => second_t,
82     enable => enable_out_t,
83     set=> set_t,
84     clk => clock_div,
85     reset => BTN_RESET,
86
87     hour_out => h,
88     minute_out => m,
89     second_out => s
90 );
91
92 CD : Clock_Divider port map (
93     clk => clock_50Mhz,
94     clock_out => clock_div,
95     reset => BTN_RESET
96 );
97
98
99
100 DEB: debouncer port map(
101     clock=> clock_50MHz,
102     reset=> BTN_RESET,
103     data_in=>BTN_NEXT,
104     data_out=>c1
105 );
106
107
108
109 B2BCD : bin2bcd port map (
110     bin => h,
111     bcd => hour_conv
112 );
113
114
115 B2BCD2 : bin2bcd port map (
116     bin => m,
117     bcd => min_conv
118 );
119
120 SEG : SEV_SEG_DISP port map (
121     clock_50Mhz => clock_50Mhz,
```

```

122  reset => BTN_RESET,
123  Anode_Activate => Anode_Activate,
124  LED_out => LED_out,
125
126  X(15) => hour_conv(7),
127  X(14) => hour_conv(6),
128  X(13) => hour_conv(5),
129  X(12) => hour_conv(4),
130  X(11) => hour_conv(3),
131  X(10) => hour_conv(2),
132  X(9) => hour_conv(1),
133  X(8) => hour_conv(0),
134
135  X(7) => min_conv(7),
136  X(6) => min_conv(6),
137  X(5) => min_conv(5),
138  X(4) => min_conv(4),
139  X(3) => min_conv(3),
140  X(2) => min_conv(2),
141  X(1) => min_conv(1),
142  X(0) => min_conv(0)
143
144 );
145
146 process (clock_div, BTN_RESET)
147 begin
148
149
150
151  if (BTN_RESET='1') then
152      hour_t <= (others => '0');
153      minute_t <= (others => '0');
154      second_t <= (others => '0');
155      enable_out_t <= '0';
156      set_t <= '1';
157      State <= A;
158  elsif (rising_edge(clock_50MHz)) then
159      case State is
160      when A =>
161          if (c1='1') then
162              if (X > "00010111") then
163                  State <= A;
164              else
165                  hour_t <= X;
166                  State <= B;
167              end if;
168
169          end if;
170      when B =>

```

```

171
172     if (c1='1') then
173
174     if (X > "00111011") then
175         State<=B;
176     else
177         minute_t <= X;
178         State<=C;
179     end if;
180
181
182     end if;
183 when C=>
184     if (c1='1') then
185
186     if (X > "00111011") then
187         State<=C;
188     else
189         second_t <= X;
190         State<=D;
191     end if;
192
193
194     end if;
195 when D=>
196     if (c1='1') then
197         set_t<='0';
198         enable_out_t <= '1';
199     end if;
200
201     end case;
202 end if;
203 LDS <= s(3 downto 0);
204
205 end process;
206
207
208
209
210 end Behavioral;

```

Codice Componente 8.3: Definizione della sintesi dell'orologio su FPGA

#### 8.2.2.4 Clock Divider

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;

```

```

4 use IEEE.numeric_std.ALL;
5
6 entity Clock_Divider is
7 port (
8     clk,reset: in std_logic;
9     clock_out: out std_logic);
10 end Clock_Divider;
11
12 architecture bhv of Clock_Divider is
13
14     signal count: integer:=1;
15     signal tmp : std_logic := '0';
16
17 begin
18
19     process(clk,reset)
20     begin
21         if(reset='1') then
22             count<=1;
23             tmp<='0';
24         elsif(clk'event and clk='1') then
25             count <=count+1;
26             if (count = 25000000) then -- vedremo i valori in 1 secondo
27                 tmp <= NOT tmp;
28                 count <= 1;
29             end if;
30         end if;
31         clock_out <= tmp;
32     end process;
33
34 end bhv;

```

Codice Componente 8.4: Definizione del file Clock Divider

### 8.2.2.5 Test UCF

Vengono impostati gli switch, i 4 led per i secondi, il display a 7 segmenti e i bottoni.

```

1
2 NET "LED_out<6>" LOC = "L18"; # Bank = 1, Pin name = IO_L10P_1, Type = I/O,
   Sch name = CA
3 NET "LED_out<5>" LOC = "F18"; # Bank = 1, Pin name = IO_L19P_1, Type = I/O,
   Sch name = CB
4 NET "LED_out<4>" LOC = "D17"; # Bank = 1, Pin name = IO_L23P_1/HDC, Type =
   DUAL, Sch name = CC
5 NET "LED_out<3>" LOC = "D16"; # Bank = 1, Pin name = IO_L23N_1/LDC0, Type =
   DUAL, Sch name = CD
6 NET "LED_out<2>" LOC = "G14"; # Bank = 1, Pin name = IO_L20P_1, Type = I/O,
   Sch name = CE

```

```

7 NET "LED_out<1>" LOC = "J17"; # Bank = 1, Pin name = IO_L13P_1/A6/RHCLK4/
  IRDY1, Type = RHCLK/DUAL, Sch name = CF
8 NET "LED_out<0>" LOC = "H14"; # Bank = 1, Pin name = IO_L17P_1, Type = I/O,
  Sch name = CG
9
10 NET "clock_50Mhz" LOC = "B8"; # Bank = 0, Pin name = IP_L13P_0/GCLK8, Type
  = GCLK, Sch name = GCLK0
11 NET "Anode_Activate<0>" LOC = "F17"; # Bank = 1, Pin name = IO_L19N_1, Type
  = I/O, Sch name = AN0
12 NET "Anode_Activate<1>" LOC = "H17"; # Bank = 1, Pin name = IO_L16N_1/A0,
  Type = DUAL, Sch name = AN1
13 NET "Anode_Activate<2>" LOC = "C18"; # Bank = 1, Pin name = IO_L24P_1/LDC1,
  Type = DUAL, Sch name = AN2
14 NET "Anode_Activate<3>" LOC = "F15"; # Bank = 1, Pin name = IO_L21P_1, Type
  = I/O, Sch name = AN3
15 NET "X<0>" LOC = "G18"; # Sch name = SW0
16 NET "X<1>" LOC = "H18"; # Sch name = SW1
17 NET "X<2>" LOC = "K18"; # Sch name = SW2
18 NET "X<3>" LOC = "K17"; # Sch name = SW3
19 NET "X<4>" LOC = "L14";
20 NET "X<5>" LOC = "L13";
21 NET "X<6>" LOC = "N17";
22 NET "X<7>" LOC = "R17";
23
24
25 NET "BTN_NEXT" LOC = "B18";
26 NET "BTN_RESET" LOC = "D18";
27
28 NET "LDS<0>" LOC = "J14";
29 NET "LDS<1>" LOC = "J15";
30 NET "LDS<2>" LOC = "K15";
31 NET "LDS<3>" LOC = "K14";

```

Codice Componente 8.5: Definizione del file UCF

### 8.3 Simulazione

Per l'orologio verranno presentati i casi di test più significativi. Nel primo caso si verifica che allo scadere del minuto 23:59:00, il contatore riprende il conteggio dalle ore 00:00:00. Nel secondo caso si mostra che posto il segnale di enable a 0 durante il conteggio, esso si blocca. Nel terzo caso viene mostrato il funzionamento del reset quando il segnale di enable è alto.

Ore	Minuti	Secondo	Enable_out	Reset
00010111 (23)	00111011 (59)	00000001 (1)	1	0
00010111(23)	00111011 (59)	00000001 (1)	1 -> 0	0
00001010(10)	00101011(43)	00001011(11)	1	1->0

Risultato atteso
Allo scadere del minuto, il contatore riparte da 00:00:00
Posto enable a 0, il conteggio si blocca
Posto reset a 0, il conteggio riparte

Il seguente codice mostra il testbench utilizzato. Si sceglie di non mostrare il codice per tutti i casi analizzati, poichè molto simili tra loro (basta modificare le variabili in ingresso nel process).

```

1  LIBRARY ieee;
2
3  LIBRARY ieee;
4  USE ieee.std_logic_1164.ALL;
5
6  ENTITY testc IS
7  END testc;
8
9  ARCHITECTURE behavior OF testc IS
10
11     -- Component Declaration for the Unit Under Test (UUT)
12
13     COMPONENT counter
14     PORT (
15         hour_in  : IN  std_logic_vector(7 downto 0);
16         minute_in : IN  std_logic_vector(7 downto 0);
17         second_in : IN  std_logic_vector(7 downto 0);
18         clk       : IN  std_logic;
19         enable    : IN  std_logic;
20         reset     : IN  std_logic;
21         hour_out  : OUT std_logic_vector(7 downto 0);
22         minute_out : OUT std_logic_vector(7 downto 0);
23         second_out : OUT std_logic_vector(7 downto 0)
24     );
25     END COMPONENT;
26
27
28     --Inputs
29     signal hour_in  : std_logic_vector(7 downto 0) := (others => '0');
30     signal minute_in : std_logic_vector(7 downto 0) := (others => '0');
31     signal second_in : std_logic_vector(7 downto 0) := (others => '0');
32     signal clk       : std_logic := '0';
33     signal enable    : std_logic := '0';
34     signal reset     : std_logic := '0';
35
36     --Outputs
37     signal hour_out  : std_logic_vector(7 downto 0);
38     signal minute_out : std_logic_vector(7 downto 0);
39     signal second_out : std_logic_vector(7 downto 0);
40
41     -- Clock period definitions

```



```


42     constant clk_period : time := 10 ns;
43
44 BEGIN
45
46 -- Instantiate the Unit Under Test (UUT)
47 uut: counter PORT MAP (
48     hour_in => hour_in,
49     minute_in => minute_in,
50     second_in => second_in,
51     clk => clk,
52     enable => enable,
53     reset => reset,
54     hour_out => hour_out,
55     minute_out => minute_out,
56     second_out => second_out
57 );
58
59 -- Clock process definitions
60 clk_process :process
61 begin
62     clk <= '0';
63     wait for clk_period/2;
64     clk <= '1';
65     wait for clk_period/2;
66 end process;
67
68
69 -- Stimulus process
70 stim_proc: process
71 begin
72     -- hold reset state for 100 ns.
73     wait for 100 ns;
74
75
76     hour_in <= "00010111";
77     minute_in <= "00111011";
78     second_in <= "00000001";
79     wait for 100 ns;
80     enable <= '1';
81     wait for 300 ns;
82     enable <= '0';
83     wait;
84 end process;
85
86 END;

```

Codice Componente 8.6: Definizione del testbench per counter.vhd


Test 1

 Si attende 1 minuto per verificare che il conteggio riparta da 0. Appena i secondi arrivano a 59 i valori di ore, minuti e secondi tornano a 0 e il conteggio riparte. Il test è superato correttamente e l'orologio si resetta allo scadere della mezzanotte.



 
### Test 2

Si abbassa il valore di enable e si verifica che il conteggio si blocca al successivo colpo di clock (fronte di salita).


 
### Test 3

Il reset funziona correttamente, impostato a 1 il valore di reset e dopo 100ns a 0 (con enable alto) i valori vengono resettati e il conteggio riparte immediatamente dopo.



# Capitolo 9

## Esercizio 9

### 9.1 Traccia

Progettare ed implementare in VHDL una macchina aritmetica combinatoria a scelta fra le seguenti:


- adder carry look ahead, per effettuare la somma di 2 stringhe A e B da 8 bit ciascuna;
- carry save adder, per effettuare la somma di 3 stringhe A, B e C da 8 bit ciascuna;
- carry select adder, per effettuare la somma di 2 stringhe A e B da 16 bit ciascuna;
- moltiplicatore con somma per righe, per effettuare il prodotto di 2 stringhe A e B da 8 bit ciascuna;
- moltiplicatore con somma per diagonal, per effettuare il prodotto di 2 stringhe A e B da 8 bit ciascuna;
- moltiplicatore con somma per colonne, per effettuare il prodotto di 2 stringhe A e B da 6 bit ciascuna;
- moltiplicatore a celle MAC, per effettuare il prodotto di 2 stringhe A e B da 8 bit ciascuna.

In ogni caso, la macchina implementata deve essere sintetizzata su FPGA e deve poter essere testata mediante l'utilizzo dei dispositivi di input/output (switch, bottoni, led, display) presenti sulla board di sviluppo in dotazione al gruppo. La modalità di utilizzo degli stessi è a completa discrezione degli studenti.

 
### 9.2 Soluzione

Il carry save adder è una macchina aritmetica costituita da blocchi carry save, che sommano i bit relativi agli operandi, e full adder. I full adder a valle prendono in ingresso i riporti generati nel livello superiore della somma dei bit i-esimi. I blocchi CS non sono soggetti alla propagazione del riporto, mentre i blocchi FA sono connessi a formare un sommatore ripple-carry. In tal modo è possibile realizzare la somma di un numero elevato di operandi, riducendo il ritardo totale complessivo.

$$s_i = (x_i + y_i + z_i) + c_{i,0} + c_{i,1}$$




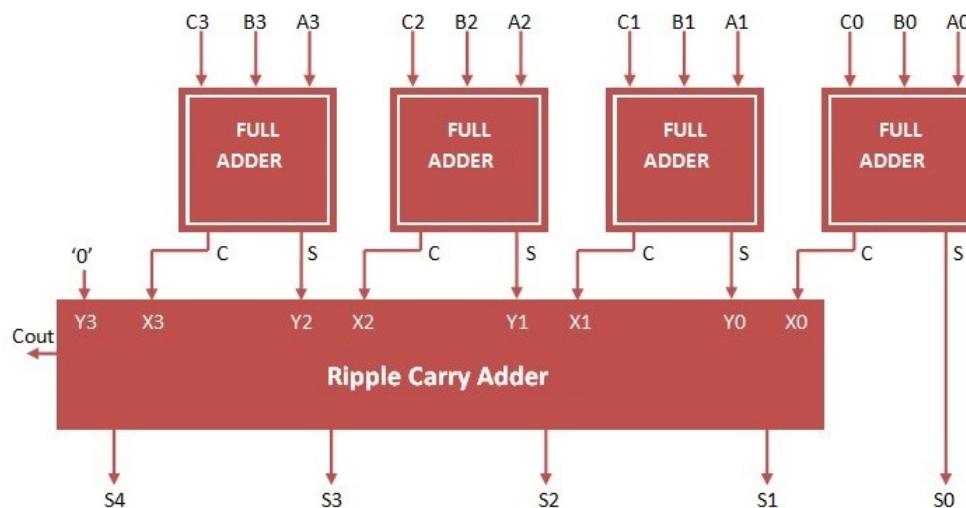
Per l'implementazione del carry save adder, è stato seguito il seguente modello:



Dopo aver sommato i bit relativi alle 3 stringhe (A,B e C), le somme e i carry ottenuti dai full adder vengono messo in ingresso ad un ripple carry adder, ad eccezione della prima somma S0 che rappresenta il primo bit del risultato finale.
  
### 9.2.1 Schematici

Il carry save adder è composto da 8 full adder, che costituiscono la carry save logic e permettono di sommare gli 8 bit dei 3 operandi considerati, e un ripple carry adder su 8 bit, che restituisce somma e riporto finali.



## 9.2.2 Codice

Il codice prodotto di seguito mostra l'implementazione strutturale del Carry Save Adder, importando nel progetto i full adder e il ripple carry adder a 8 bit sviluppato nel capitolo 4.

### 9.2.2.1 Carry Save Adder

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4
5 entity carry_save_adder is
6 Port ( A : in STD_LOGIC_VECTOR (7 downto 0);
7       B : in STD_LOGIC_VECTOR (7 downto 0);
8       C : in STD_LOGIC_VECTOR (7 downto 0);
9       S1 : OUT STD_LOGIC_VECTOR (8 downto 0);
10      Cout : OUT STD_LOGIC);
11 end carry_save_adder;
12
13 architecture Behavioral of carry_save_adder is
14
15 component ripple_carry_adder_8b
16 PORT (
17     A : in  std_logic_vector (7 downto 0);
18     B : in  std_logic_vector(7 downto 0);
19     c0 : in std_logic;
20     c8 : out std_logic;
21     S : out std_logic_vector (7 downto 0)
22 );
23
24 end component;
25
26
27 component full_adder is
28     PORT (
29         x : in  std_logic;
30         y : in std_logic;
31         c0 : in std_logic;
32         s : out std_logic;
33         c : out std_logic );
34
35 end component;
36
37
38
39 -- Intermediate signal
40 signal X,Y: STD_LOGIC_VECTOR(3 downto 0);
41 signal C1,C2,C3: STD_LOGIC;
42
43 signal carry : STD_LOGIC_VECTOR(7 downto 0);
44 signal sum : STD_LOGIC_VECTOR(7 downto 0);
45
46 begin
47
48 -- 8 full adder

```

```

49 FA0 : full_adder port map ( x => A(0), y => B(0), c0 => C(0), s => S1(0), c
    => carry(0) );
50 FA1 : full_adder port map ( x => A(1), y => B(1), c0 => C(1), s => sum(0), c
    => carry(1) );
51 FA2 : full_adder port map ( x => A(2), y => B(2), c0 => C(2), s => sum(1), c
    => carry(2) );
52 FA3 : full_adder port map ( x => A(3), y => B(3), c0 => C(3), s => sum(2), c
    => carry(3) );
53 FA4 : full_adder port map ( x => A(4), y => B(4), c0 => C(4), s => sum(3), c
    => carry(4) );
54 FA5 : full_adder port map ( x => A(5), y => B(5), c0 => C(5), s => sum(4), c
    => carry(5) );
55 FA6 : full_adder port map ( x => A(6), y => B(6), c0 => C(6), s => sum(5), c
    => carry(6) );
56 FA7 : full_adder port map ( x => A(7), y => B(7), c0 => C(7), s => sum(6), c
    => carry(7) );

57
58 -- 1 ripple carry adder a 8 bit
59 RCA0 : ripple_carry_adder_8b port map (
60     A(0) => sum(0),
61     A(1) => sum(1),
62     A(2) => sum(2),
63     A(3) => sum(3),
64     A(4) => sum(4),
65     A(5) => sum(5),
66     A(6) => sum(6),
67     A(7) => '0',
68     B => carry,
69     c0 => '0',
70     c8 => cout,
71     S(0) => S1(1),
72     S(1) => S1(2),
73     S(2) => S1(3),
74     S(3) => S1(4),
75     S(4) => S1(5),
76     S(5) => S1(6),
77     S(6) => S1(7),
78     S(7) => S1(8)
79 );
80
81
82 end Behavioral;

```

Codice Componente 9.1: Definizione del componente Carry Save Adder

### 9.3 Simulazione

Prima di sintetizzare il componente ne verifichiamo il corretto funzionamento attraverso dei test. A, B, C sono i 3 operandi in ingresso, SUM è la loro somma e Cout è l'eventuale valore di riporto. La seguente tabella mostra i casi di test analizzati e l'output atteso per ognuno di essi.

A	B	C	Cout	SUM
00000000	00000000	00000000	0	000000000
11111111	11111111	11111111	1	011111101
00000000	00000001	10101101	0	010101110
10101101	00000000	00000001	0	010101110
00101010	10000010	10101010	0	101010110

In decimale i test corrispondono a :

A	B	C	SUM
0	0	0	0
255	255	255	765
0	1	173	174
173	0	1	174
42	130	170	342

```

1
2
3  LIBRARY ieee;
4  USE ieee.std_logic_1164.ALL;
5
6  ENTITY testcsa IS
7  END testcsa;
8
9  ARCHITECTURE behavior OF testcsa IS
10
11     -- Component Declaration for the Unit Under Test (UUT)
12
13     COMPONENT carry_save_adder
14     PORT (
15         A : IN  std_logic_vector(7 downto 0);
16         B : IN  std_logic_vector(7 downto 0);
17         C : IN  std_logic_vector(7 downto 0);
18         S1 : OUT std_logic_vector(8 downto 0);
19         Cout : OUT std_logic
20     );
21     END COMPONENT;
22
23
24     --Inputs
25     signal A : std_logic_vector(7 downto 0) := (others => '0');
26     signal B : std_logic_vector(7 downto 0) := (others => '0');

```



```

27     signal C : std_logic_vector(7 downto 0) := (others => '0');
28
29 --Outputs
30     signal S1 : std_logic_vector(8 downto 0);
31     signal Cout : std_logic;
32     -- No clocks detected in port list. Replace <clock> below with
33     -- appropriate port name
34
35
36
37 BEGIN
38
39     -- Instantiate the Unit Under Test (UUT)
40     uut: carry_save_adder PORT MAP (
41         A => A,
42         B => B,
43         C => C,
44         S1 => S1,
45         Cout => Cout
46     );
47
48
49
50     -- Stimulus process
51     stim_proc: process
52     begin
53         -- hold reset state for 100 ns.
54
55         wait for 100 ns;
56         A <= "00000000";
57         B <= "00000000";
58         C <= "00000000";
59         wait for 100 ns;
60         A <= "11111111";
61         B <= "11111111";
62         C <= "11111111";
63         wait for 100 ns;
64         A <= "00000000";
65         B <= "00000001";
66         C <= "10101101";
67         wait for 100 ns;
68         A <= "10101101";
69         B <= "00000000";
70         C <= "00000001";
71         wait for 100 ns;
72         A <= "00101010";
73         B <= "10000010";
74         C <= "10101010";
75         wait for 100 ns;

```

```

76     wait;
77     end process;
78
79 END;
```

Codice Componente 9.2: Definizione del testbench per Carry Save Adder

I risultati dei test in ISim confermano i risultati attesi.

Name	Value	200 ns	300 ns	400 ns	500 ns	600 ns	700 ns
a[7:0]	00101010	00000000	11111111	00000000	10101101		00101010
b[7:0]	10000010	00000000	11111111	00000001	00000000		10000010
c[7:0]	10101010	00000000	11111111	10101101	00000001		10101010
s1[8:0]	101010110	000000000	011111101	010101110	010101110		101010110
cout	0						

## 9.4 Sintesi su board FPGA

La sintesi su board per il carry save adder è simile a quella implementata per il semplice full adder. Ci serviamo del solito componente display a 7 segmenti (per mostrare i dati) e del carry save precedentemente sviluppato. Il processo di controllo prevede che l'utente inserisca in ordine i valori da sommare (codificati su 8 bit) attraverso gli switch. Questi poi sono caricati con la pressione dei bottoni presenti sulla board. Ogni volta che un valore viene immesso, il sistema controlla se sono stati inseriti anche gli altri 2 e calcola il risultato, che viene mostrato premendo il bottone di result. Durante tutta l'operazione i valori degli operandi vengono mostrati in tempo reale sul display a 7 segmenti.

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4 use ieee.numeric_std.all;
5 use IEEE.std_logic_signed.all;
6
7
8 entity CarrySaveFPGA is
9
10     Port (    clock_50Mhz : in STD_LOGIC;
11              load1, load2, load3, result: in STD_LOGIC;
12              X : in STD_LOGIC_VECTOR (7 downto 0);
13              Anode_Activate : out STD_LOGIC_VECTOR (3 downto 0);
14              LED_out : out STD_LOGIC_VECTOR (6 downto 0)
15     );
16
17 end CarrySaveFPGA;
18
19 architecture Behavioural of CarrySaveFPGA is
20
21
22     signal OP_1, OP_2, OP_3: boolean := false;
23
```

```

24 signal op1, op2, op3 : std_logic_vector (7 downto 0) := (others => '0') ;
25 signal sum : std_logic_vector (8 downto 0) := (others => '0') ;
26 signal zero : std_logic_vector (7 downto 0) := (others => '0') ;
27
28 signal cout : std_logic;
29
30 signal value_to_display: std_logic_vector (8 downto 0);
31
32
33
34 component carry_save_adder is
35     Port (   A,B,C : in STD_LOGIC_VECTOR (7 downto 0);
36             S1 : OUT STD_LOGIC_VECTOR (8 downto 0);
37             Cout : OUT STD_LOGIC
38 );
39 end component;
40
41
42
43 component SEV_SEG_DISP is
44     Port (
45         X : in STD_LOGIC_VECTOR(8 downto 0);
46         clock_50Mhz : in STD_LOGIC;
47         reset : in STD_LOGIC;
48         Anode_Activate : out STD_LOGIC_VECTOR (3 downto 0);
49         LED_out : out STD_LOGIC_VECTOR (6 downto 0)
50 );
51
52 end component;
53
54
55 begin
56
57 CSA : carry_save_adder port map(
58     A => op1,
59     B => op2,
60     C => op3,
61     Cout => cout,
62     S1 => sum
63 );
64
65
66 SSD : SEV_SEG_DISP port map(
67     X => value_to_display,
68     clock_50Mhz => clock_50Mhz,
69     reset => '0',
70     Anode_Activate => Anode_Activate,
71     LED_out => LED_out
72 );

```

```

73 );
74
75
76
77 process (clock_50Mhz)
78
79 begin
80
81     if (rising_edge(clock_50Mhz)) then
82         if load1 = '1' then
83             -- Primo operando
84             op1 <= X;
85             OP_1 <= true;
86             OP_2 <= false;
87             OP_3 <= false;
88         elsif load2 = '1' then
89             -- Secondo operando
90             op2 <= X;
91             OP_2 <= true;
92             OP_3 <= false;
93         elsif load3 = '1' then
94             -- Terzo operando
95             op3 <= X;
96             OP_3 <= true;
97         end if;
98
99         if (OP_1 = true and OP_2 = true and OP_3 = true) then
100             if result = '1' then
101                 -- Se sono stati inseriti 3 operandi e se il bottone apposito viene
102                 -- premuto
103                 value_to_display <= sum;
104             end if;
105         else
106             -- mostra in tempo reale i valori degli operandi inseriti
107             value_to_display <= '0' & X;
108         end if;
109     end if;
110
111 end process;
112
113 end Behavioural;

```

Codice Componente 9.3: Sintesi carry save

### 9.4.1 File UCF

```

2 NET "LED_out<6>" LOC = "L18"; # Bank = 1, Pin name = IO_L10P_1, Type = I/O,
  Sch name = CA
3 NET "LED_out<5>" LOC = "F18"; # Bank = 1, Pin name = IO_L19P_1, Type = I/O,
  Sch name = CB
4 NET "LED_out<4>" LOC = "D17"; # Bank = 1, Pin name = IO_L23P_1/HDC, Type =
  DUAL, Sch name = CC
5 NET "LED_out<3>" LOC = "D16"; # Bank = 1, Pin name = IO_L23N_1/LDC0, Type =
  DUAL, Sch name = CD
6 NET "LED_out<2>" LOC = "G14"; # Bank = 1, Pin name = IO_L20P_1, Type = I/O,
  Sch name = CE
7 NET "LED_out<1>" LOC = "J17"; # Bank = 1, Pin name = IO_L13P_1/A6/RHCLK4/
  IRDY1, Type = RHCLK/DUAL, Sch name = CF
8 NET "LED_out<0>" LOC = "H14"; # Bank = 1, Pin name = IO_L17P_1, Type = I/O,
  Sch name = CG
9
10 NET "clock_50Mhz" LOC = "B8"; # Bank = 0, Pin name = IP_L13P_0/GCLK8, Type
  = GCLK, Sch name = GCLK0
11 NET "Anode_Activate<0>" LOC = "F17"; # Bank = 1, Pin name = IO_L19N_1, Type
  = I/O, Sch name = AN0
12 NET "Anode_Activate<1>" LOC = "H17"; # Bank = 1, Pin name = IO_L16N_1/A0,
  Type = DUAL, Sch name = AN1
13 NET "Anode_Activate<2>" LOC = "C18"; # Bank = 1, Pin name = IO_L24P_1/LDC1,
  Type = DUAL, Sch name = AN2
14 NET "Anode_Activate<3>" LOC = "F15"; # Bank = 1, Pin name = IO_L21P_1, Type
  = I/O, Sch name = AN3
15
16 NET "X<0>" LOC = "G18"; # Sch name = SW0
17 NET "X<1>" LOC = "H18"; # Sch name = SW1
18 NET "X<2>" LOC = "K18"; # Sch name = SW2
19 NET "X<3>" LOC = "K17"; # Sch name = SW3
20 NET "X<4>" LOC = "L14";
21 NET "X<5>" LOC = "L13";
22 NET "X<6>" LOC = "N17";
23 NET "X<7>" LOC = "R17";
24
25 NET "load1" LOC = "B18";
26 NET "load2" LOC = "D18";
27 NET "load3" LOC = "E18";
28 NET "result" LOC = "H13";

```

Codice Componente 9.4: F

# Capitolo 10

## Esercizio 10

### 10.1 Traccia

Progettare ed implementare in VHDL una macchina aritmetica sequenziale a scelta fra le seguenti:

- moltiplicatore di Robertson, per effettuare il prodotto di 2 stringhe A e B da 8 bit ciascuna;
- moltiplicatore di Booth, per effettuare il prodotto di 2 stringhe A e B da 8 bit ciascuna;
- divisore non-restoring, per effettuare la divisione intera fra due stringhe A e B di 4 bit ciascuna;
- divisore restoring, per effettuare la divisione intera fra due stringhe A e B di 4 bit ciascuna;

In ogni caso, la macchina implementata deve essere sintetizzata su FPGA e deve poter essere testata mediante l'utilizzo dei dispositivi di input/output (switch, bottoni, led, display) presenti sulla board di sviluppo in dotazione al gruppo. La modalità di utilizzo degli stessi è a completa discrezione degli studenti.

### 10.2 Soluzione

Il moltiplicatore di Robertson è un moltiplicatore sequenziale, che riceve in ingresso due operandi ad N bit codificati in complementi a due e restituisce un prodotto su 2N bit. Tale moltiplicatore sfrutta questa notazione:

$$X = -2^{n-1}x^{n-1} + \sum_{i=0}^{n-2} 2^i x_i$$

Per un numero positivo viene assegnato peso  $2^{n-1}$  al bit di segno  $x_{n-1}$ : poiché è nullo il suo contributo allo 0 sulla cifra più significativa. Per un numero negativo viene assegnato peso  $-2^{n-1}$  al bit di segno  $x_{n-1}$ : poiché esso vale 1 il suo contributo al numero è -1 sulla cifra più significativa. Tale metodo ci consente di utilizzare una tecnica unsigned facendo attenzione ad effettuare una sottrazione invece di una addizione quando si incontra un segno negativo. A tal scopo è stato implementato un componente che effettua sia l'addizione che la sottrazione di due operandi a seconda del valore di un bit (0,1) in ingresso.

Riassumiamo dunque i 4 casi possibili :

- $X > 0$  e  $Y > 0$  : caso standard, moltiplicazione tra unsigned fatta con addizione e shift.
  - $X > 0$  e  $Y < 0$  : quando si moltiplica  $Y$  per il  $j$ -esimo valore di  $X$  diverso da 0, il prodotto parziale è negativo e quindi il bit più significativo dell'accumulatore  $A$  diventa 1.
  - $X < 0$  e  $Y > 0$  : per l'ultimo prodotto va effettuato un'ulteriore operazione di correzione  $A - M$ .
  - $X < 0$  e  $Y < 0$  : anche in tal caso è necessario per l'ultimo prodotto l'operazione di correzione  $A - M$ . Il bit più significativo di  $A$  resta 0 e diventa 1 quando il  $j$ -esimo valore di  $X$  è 1.
- L'algoritmo è mostrato di seguito :

```

2CMultiplier:    (in:INBUS; OUT:OUTBUS)
                  register A[7:0],M[7:0],Q[7:0],COUNT[2:0],F;
                  bus INBUS[7:0],OUTBUS[7:0];

BEGIN:           A:=0,COUNT:=0,F:=0,
INPUT:           M:=INBUS;Q:=INBUS;

ADD:             A[7:0]:=A[7:0] + M [7:0] x Q[0],
                  F:=(M[7] and Q[0]) or F;
RSHIFT:         A[7]:= F,  A[6:0].Q:= A.Q[7:1],
INCREMENT:      COUNT:=COUNT+1

TEST:           if COUNT<7 then go to ADD;


SUBTRACT:        A[7:0]:=A[7:0]-M[7:0]xQ[0];    {l'ultima op è sempre SUB}
RSHIFT:         A[7]:= A[7],  A[6:0].Q:= A.Q[7:1];

OUTPUT:         OUTBUS:=Q; OUTBUS:=A;
END 2CMultiplier;

```

L'algoritmo inizia ponendo in  $M$  e  $Q$  i due operandi  $X$  e  $Y$  (inbus) e inizializzando il registro  $A$  (accumulatore), il contatore e il registro  $F$ .


L'addizione si esegue tra  $A$  ed  $M$  e si pone il risultato nel registro  $A$ . Successivamente viene effettuata l'operazione  $F = (M(7) \text{ and } Q(0)) \text{ or } F$ , che serve a gestire il caso 2 (moltiplicando negativo e moltiplicatore positivo). Il valore di  $F$  viene posto nel bit più significativo di  $A$  e il contenuto di quest'ultimo viene shiftato a destra in modo tale che il bit  $Q(1)$  si trovi in  $Q(0)$  per la prossima operazione. Il contatore delle operazioni viene incrementato e fin quando rimane minore di 7 le operazioni vanno avanti. Lo stato di correzione viene richiamato quando il contatore si ferma e viene fatta la correzione tramite sottrazione di  $A$  ed  $M$ .

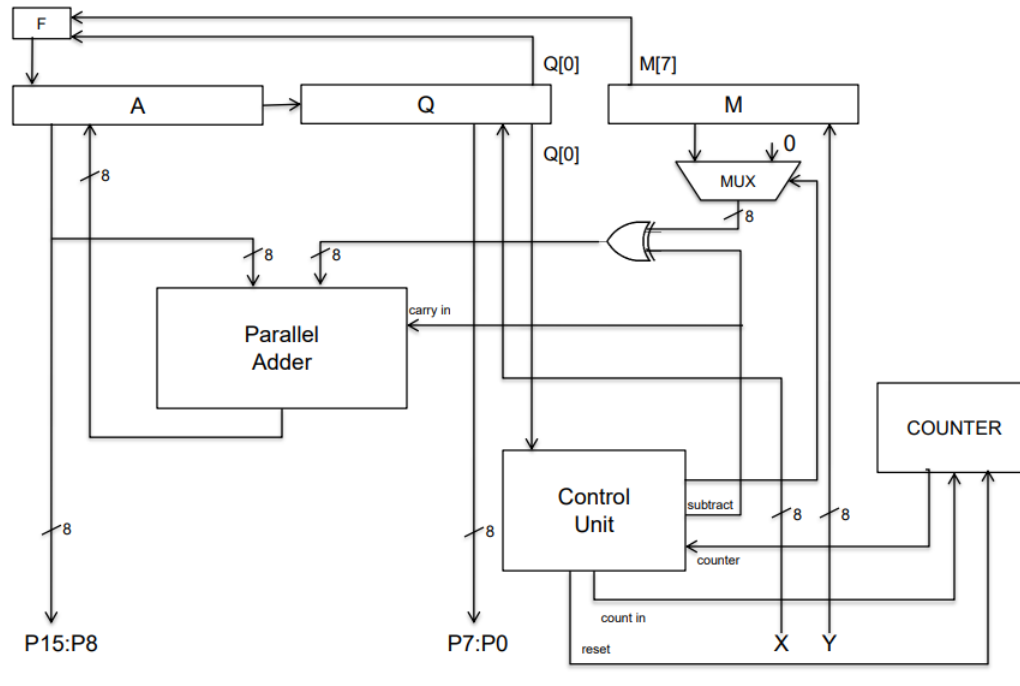

La control unit ha il compito di abilitare e disabilitare i componenti adibiti alle operazioni in base allo stato corrente. La parte di controllo dunque implementa una macchina a stati che gestisce il comportamento dei registri.
 
### 10.2.1 Schematici

Lo schematico mostra i due ingressi X e Y (moltiplicatore e moltiplicando) il clock, il reset e il segnale di start che abilita la periferica ad effettuare l'operazione. L'uscita di 16 bit è suddivisa in due segnali A1 e Q1 rappresentanti gli 8 bit rispettivamente più e meno significativi.





## 10.2.2 Codice

### 10.2.2.1 Moltiplicatore di Robertson

Tutti i componenti vengono collegati tra loro, come da figura, nel codice sottostante. Il flop flop D è il registro F mostrato in figura, nel segnale tD viene messa la and tra M(7) e Q(0). t\_sr\_a è il primo bit più significativo shiftato in A e prende il contenuto di F oppure A(7) nell'ultimo passaggio (per la correzione finale). t\_mux\_sel è il segnale del multiplexer che serve a prendere il contenuto del moltiplicando quando bisogna effettuare addizione o sottrazione e il bit Q(0) è pari ad 1. t\_shift abilita lo shift di A e Q a destra nei registri a scorrimento.

```

1
2
3
4 library IEEE;
5 use IEEE.STD_LOGIC_1164.ALL;
6 use ieee.numeric_std.all;
7 use IEEE.std_logic_unsigned.all;
8
9
10 entity Robertson is
11   Port (
12     clock : in  STD_LOGIC;
13     X,Y : in  STD_LOGIC_VECTOR (7 downto 0);
14     start,reset : in STD_LOGIC;
15     A1,Q1: out STD_LOGIC_VECTOR (7 downto 0)
16
17   );
18 end Robertson;
19
20 architecture Structural of Robertson is
21
22
23 component PC
24 Port (
25   clock : in STD_LOGIC;
26   start,reset : in STD_LOGIC;
27   count: in STD_LOGIC_VECTOR(2 downto 0);
28   Q0 : in STD_LOGIC;
29   mux_en,reg_en,shift_en,fshift_en : out STD_LOGIC;
30   sub : out STD_LOGIC;
31   A_en : out STD_LOGIC;
32   enablecount: out STD_LOGIC;
33   resetcount: out STD_LOGIC
34 );
35 end component;
36
37
38 Component FlipFlopD
39 port (

```

```
40     D: in STD_LOGIC;
41     clock: in STD_LOGIC;
42     enable, reset : in STD_LOGIC;
43     Q, Qn : out STD_LOGIC
44
45 );
46 end Component;
47
48
49 Component addsub
50 port (
51     X, Y : in STD_LOGIC_VECTOR (7 downto 0);
52     subtract : in STD_LOGIC;
53     cout : out STD_LOGIC;
54     s : out STD_LOGIC_VECTOR (7 downto 0);
55     ov : out STD_LOGIC
56
57 );
58 end Component;
59
60
61 Component shiftregister
62 port (
63
64     clock : in STD_LOGIC;
65     reset : in STD_LOGIC;
66     shift : in STD_LOGIC;
67     load : in STD_LOGIC;
68     serial_in : in STD_LOGIC;
69     parallel_in : in STD_LOGIC_VECTOR (7 downto 0);
70     serial_out : out STD_LOGIC;
71     parallel_out : out STD_LOGIC_VECTOR (7 downto 0)
72
73 );
74 end Component;
75
76
77 Component registro
78 port (
79
80     clock : in STD_LOGIC;
81     reset : in STD_LOGIC;
82     enable: in STD_LOGIC;
83     datain : in STD_LOGIC_VECTOR (7 downto 0);
84     dataout : out STD_LOGIC_VECTOR (7 downto 0)
85
86 );
87 end Component;
88
```

```

89
90 Component muxb
91 port (
92
93     a0,b0: in  std_logic_vector(7 downto 0);
94     s0 : in  std_logic;
95     y : out std_logic_vector(7 downto 0)
96
97 );
98 end Component;
99
100
101 Component counter
102 port (
103     clock : in STD_LOGIC;
104     enable : in STD_LOGIC;
105     reset: in STD_LOGIC;
106     count : out STD_LOGIC_VECTOR (2 downto 0)
107 );
108 end component;
109
110
111 signal tQ, t_a_in, uscita_a, tM, uscita_mux : std_logic_vector(7 downto 0)
112     :=(others=>'0');
113 signal mux_enable, reg_enable, t_shift_en, t_fshift_en, sub_enable,
114     t_Aenable :std_logic :='0';
115 signal resetcount,enablecount,t_mux_sel, tD, tF, tFn, tshift, t_load, t_sr_a
116     , t_sr_q :std_logic :='0';
117 signal cnt : std_logic_vector(2 downto 0):=(others=>'0');
118
119 begin
120
121 tshift <= t_shift_en or t_fshift_en;
122 t_load <= t_Aenable or sub_enable;
123 t_mux_sel <= mux_enable and (sub_enable or t_Aenable);
124
125 t_sr_a <= tF when t_shift_en = '1' else
126     '0' when (t_fshift_en='1' and tD='1') else
127     uscita_a(7) when t_fshift_en = '1' else
128     '0';
129
130 tD <= (tM(7) and tQ(0));
131
132 A1<= uscita_a;
133 Q1<= tQ;
134
135 cu: PC port map(clock,start,reset,cnt,tQ(0),mux_enable, reg_enable,

```

```

    t_shift_en, t_fshift_en, sub_enable, t_Aenable, enablecount, resetcount)
    ;
135
136 adder1: addsub port map(uscita_a,uscita_mux,sub_enable, open, t_a_in, open);
137
138 mux1: muxb port map ("00000000", tM, t_mux_sel, uscita_mux);
139
140 ff1 : FlipFlopD port map(tD, clock, tFn , reset, tF, tFn);
141
142 regM: registro port map(clock, reset, reg_enable, Y, tM);
143
144 regA: shiftregister port map(clock, reset, tshift, t_load,t_sr_a, t_a_in,
    t_sr_q, uscita_a);
145
146 regQ: shiftregister port map(clock, reset, tshift, reg_enable, t_sr_q, X,
    open, tQ);
147
148 contatore: counter port map (clock,enablecount,resetcount,cnt);
149
150 end Structural;

```

Codice Componente 10.1: Definizione del moltiplicatore di Robertson

### 10.2.2.2 PC

La parte di controllo implementa la macchina a stati di cui si è discusso in precedenza. Gli stati in tutto sono 6 : Idle, Add, Shift, Sub, Finale(ultimo shift) ed Output. Lo stato di Idle abilita i registri e resetta il contatore delle operazioni. Tutti gli altri componenti restano disabilitati fino a quando lo stato di start non è alto. Quando start è alto, se il primo bit di Q(0) è 1, si effettua una addizione; altrimenti si fa semplicemente lo shift. Nello stato di add si abilita il registro A (accumulatore) per memorizzare il risultato e si passa allo stato di shift per ottenere il nuovo Q(0). Lo stato di shift abilita i registri a scorrimento e il contatore aggiunge 1 al conteggio delle operazioni. Se il contatore è arrivato a 7 (maggiore di 110), lo stato successivo è substate che effettua la correzione e porta allo stato finale e di output, che mostra poi il risultato. Se invece il contatore non è ancora arrivato al limite massimo, si torna allo stato di add.

```

1
2  --
3  library IEEE;
4  use IEEE.STD_LOGIC_1164.ALL;
5
6  -- Uncomment the following library declaration if using
7  -- arithmetic functions with Signed or Unsigned values
8  --use IEEE.NUMERIC_STD.ALL;
9
10 -- Uncomment the following library declaration if instantiating
11 -- any Xilinx primitives in this code.

```

```

12 --library UNISIM;
13 --use UNISIM.VComponents.all;
14
15 entity PC is
16 port (
17     clock : in STD_LOGIC;
18     start,reset : in STD_LOGIC;
19     count: in STD_LOGIC_VECTOR(2 downto 0);
20     Q0 : in STD_LOGIC;
21     mux_en,reg_en,shift_en,fshift_en : out STD_LOGIC;
22     sub : out STD_LOGIC;
23     A_en : out STD_LOGIC;
24     enablecount: out STD_LOGIC;
25     resetcount: out STD_LOGIC
26 );
27 end PC;
28
29 architecture Behavioral of PC is
30
31
32 type STATE_type is (idle, add, shift, substate, finale, output);
33 signal State: STATE_type := idle;
34
35 begin
36
37 mux_en <= Q0;
38
39
40
41 process (clock,start,reset,Q0,State,count)
42 begin
43
44 if rising_edge(clock) then
45 case State is
46
47 when idle =>
48     resetcount <= '1';
49     reg_en <= '1';
50     shift_en <= '0';
51     fshift_en <= '0';
52     A_en <= '0';
53     sub <= '0';
54     enablecount <='0';
55
56     if (start = '1' and Q0 = '1') then
57         State <= add;
58     elsif (start = '1' and Q0 = '0') then
59         State <= shift;
60     else

```

```
61     State <= idle;
62 end if;
63
64 when add =>
65     reg_en <= '0';
66     shift_en <= '0';
67     fshift_en <= '0';
68     A_en <= '1';
69     resetcount <= '0';
70     sub <= '0';
71     enablecount <='0';
72
73     if reset = '1' then
74         State <= idle;
75     else
76         State <= shift;
77     end if;
78
79 when shift =>
80     reg_en <= '0';
81     shift_en <= '1';
82     fshift_en <= '0';
83     A_en <= '0';
84     resetcount <= '0';
85     sub <= '0';
86     enablecount <= '1';
87
88     if reset = '1' then
89         State <=idle;
90     elsif count = "110" then
91         State <= substate;
92     else
93         State <= add;
94     end if;
95
96 when substate =>
97     reg_en <= '0';
98     shift_en <= '0';
99     fshift_en <= '0';
100    A_en <= '0';
101    resetcount <= '0';
102
103    sub <= '1';
104    enablecount <= '0';
105
106    if reset = '1' then
107        State <=idle;
108    else
109        State <= finale;
```

```

110     end if;
111
112
113 when finale =>
114     shift_en <= '0';
115     fshift_en <= '1';
116     reg_en <= '0';
117     A_en <= '0';
118     resetcount <= '0';
119     sub <= '0';
120     enablecount <= '0';
121
122     if reset = '1' then
123         State <=idle;
124     else
125         State <= output;
126     end if;
127
128
129 when output =>
130     resetcount <= '0';
131     shift_en <= '0';
132     fshift_en <= '0';
133     reg_en <= '0';
134     A_en <= '0';
135     sub <= '0';
136     enablecount <= '0';
137
138     if (reset = '1' or start='0') then
139         State <=idle;
140     else
141         State <= output;
142     end if;
143
144
145 end case;
146
147
148 end if;
149 end process;
150
151
152 end Behavioral;

```

Codice Componente 10.2: Definizione della Parte di Controllo

### 10.2.2.3 Registro

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164. ALL;
4
5 entity registro is
6
7 Port (
8     clock : in STD_LOGIC;
9     reset  : in STD_LOGIC;
10    enable : in STD_LOGIC;
11    datain  : in STD_LOGIC_VECTOR (7 downto 0);
12    dataout : out STD_LOGIC_VECTOR (7 downto 0)
13 );
14 end registro;
15
16 architecture behavioral of registro is
17
18 begin
19
20 process (clock, reset, enable)
21
22 variable d: STD_LOGIC_VECTOR (7 downto 0):=(others => '0');
23
24 begin
25
26 if (reset = '1') then
27     d := (others => '0');
28
29 elsif (enable = '1' and rising_edge(clock)) then
30     d := datain;
31
32 else
33     d := d;
34 end if;
35
36 dataout <= d;
37
38 end process;
39
40 end behavioral;

```

Codice Componente 10.3: Definizione del registro

#### 10.2.2.4 Mux Bus

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164. ALL;

```




```

4
5
6 entity muxb is
7   PORT (
8     a0,b0: in  std_logic_vector(7 downto 0);
9     s0 : in  std_logic;
10    y : out std_logic_vector(7 downto 0)
11  );
12 end muxb;
13
14
15 architecture dataflow of muxb is
16
17 begin
18
19 y<= a0 when (s0 = '0') else
20    b0 when (s0 = '1') else
21    "00000000";
22
23 end dataflow;

```

Codice Componente 10.4: Definizione del mux bus

### 10.2.2.5 Adder - Subtractor

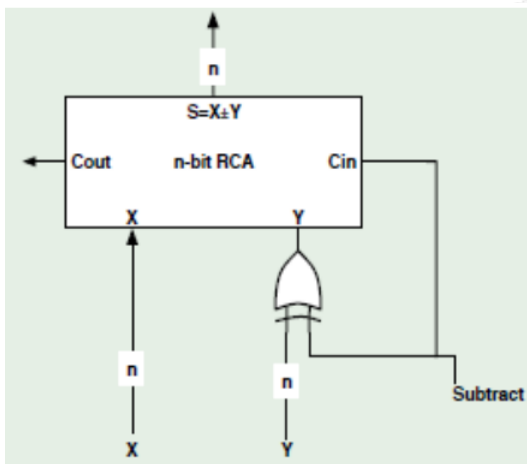

Il componente Adder-Subtractor, dati due operandi, ci permette di realizzare sia un' addizione che una sottrazione.

Quando il segnale subtract è '1' l'addizionatore prende in ingresso X e Y negato. Mettendo '1' in C0 al ripple carry adder (implementazione nei precedenti capitoli) si ottiene l'operazione X-Y.

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164. ALL;
4
5

```

```

6 entity addsub is
7 Port (
8     X,Y : in STD_LOGIC_VECTOR (7 downto 0);
9     subtract : in STD_LOGIC;
10    cout : out STD_LOGIC;
11    s : out STD_LOGIC_VECTOR (7 downto 0);
12    ov : out STD_LOGIC
13 );
14 end addsub;
15
16 architecture Structural of addsub is
17
18 component ripple_carry_adder_8b is
19 Port (
20
21     A,B : in std_logic_vector (7 downto 0);
22     c0 : in std_logic;
23     c8 : out std_logic;
24     S: out std_logic_vector (7 downto 0)
25 );
26 end component;
27
28
29 signal btemp,stemp : STD_LOGIC_VECTOR (7 downto 0);
30
31 begin
32
33
34 process (Y, subtract)
35 begin
36
37     for i in 0 to 7 loop
38         btemp(i) <= Y(i) xor subtract;
39     end loop;
40
41 end process;
42
43 adder: ripple_carry_adder_8b port map (X,btemp,subtract,cout,stemp);
44
45 ov <= '1' when (X(7)='0' and btemp(7)='0' and stemp(7)='1') or (X(7)='1' and
46         btemp(7)='1' and stemp(7)='0') else
47         '0';
48 s <= stemp;
49 end Structural;

```

Codice Componente 10.5: Definizione del Adder - Subtractor

## 10.3 Simulazione

Il testbench istanzia il componente moltiplicatore di Robertson e, dopo aver caricato i due operandi, l'operazione viene avviata mettendo ad 1 il segnale di start.

X	Y	Output atteso
00000011	00001000	00000000000011000
11111110	00001000	11111111111110000
00001000	11111110	1111111111110000
11111100	11111101	0000000000001100
11111111	11111111	0000000000000001
10000000	10000000	0100000000000000

I dati sono stati raccolti sostituendo di volta in volta i valori di X ed Y.

```

1
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.ALL;
4
5  ENTITY robertest IS
6  END robertest;
7
8  ARCHITECTURE behavior OF robertest IS
9
10     -- Component Declaration for the Unit Under Test (UUT)
11
12     COMPONENT Robertson
13     PORT (
14         clock : IN  std_logic;
15         X : IN  std_logic_vector(7 downto 0);
16         Y : IN  std_logic_vector(7 downto 0);
17         start : IN  std_logic;
18         reset : IN  std_logic;
19         A1 : OUT std_logic_vector(7 downto 0);
20         Q1 : OUT std_logic_vector(7 downto 0)
21     );
22     END COMPONENT;
23
24
25     --Inputs
26     signal clock : std_logic := '0';
27     signal X : std_logic_vector(7 downto 0) := (others => '0');
28     signal Y : std_logic_vector(7 downto 0) := (others => '0');
29     signal start : std_logic := '0';
30     signal reset : std_logic := '0';
31
32     --Outputs
33     signal A1 : std_logic_vector(7 downto 0);
34     signal Q1 : std_logic_vector(7 downto 0);


```

```
35
36  -- Clock period definitions
37  constant clock_period : time := 10 ns;
38
39 BEGIN
40
41  -- Instantiate the Unit Under Test (UUT)
42  uut: Robertson PORT MAP (
43      clock => clock,
44      X => X,
45      Y => Y,
46      start => start,
47      reset => reset,
48      A1 => A1,
49      Q1 => Q1
50  );
51
52  -- Clock process definitions
53  clock_process : process
54  begin
55      clock <= '0';
56      wait for clock_period/2;
57      clock <= '1';
58      wait for clock_period/2;
59  end process;
60
61
62  -- Stimulus process
63  stim_proc: process
64  begin
65
66
67      X <= "00000000";
68      Y <= "00000000";
69      wait for 100 ns;
70
71
72      X <= "00000001";
73      Y <= "00000001";
74
75      wait for 10 ns;
76      start <= '1';
77      --wait for 100ns;
78      --start <= '0';
79
80      wait;
81  end process;
82
83 END;
```


## Codice Componente 10.6: Definizione del testbench per Moltiplicatore di Robertson

Tutti i risultati dei test corrispondono a quelli attesi.


Test 1

 


Test 2

 


Test 3

 


Test 4

 

Test 5

 

Test 6

 

## 10.4 Sintesi su board FPGA

### 10.4.1 Sintesi Robertson

Al moltiplicatore di Robertson vengono aggiunti un componente display a 7 segmenti per mostrare operandi e risultato. È presente un process per regolare l'immissione degli input (switch e bottoni) e dare lo start al moltiplicatore per calcolare il risultato. Dopo la pressione del bottone result, al segnale value\_to\_display, direttamente collegato col display a 7 segmenti, vengono assegnati tramite l'operatore & i due segnali di uscita A e Q, che insieme rappresentano il risultato su 16 bit della moltiplicazione.

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4
5
6 entity RobertsonFPGA is
7 Port (
8     clock_50Mhz : in STD_LOGIC;
9     X : in STD_LOGIC_VECTOR (7 downto 0);
10    load1,load2,result,reset : in STD_LOGIC;
11    Anode_Activate : out STD_LOGIC_VECTOR (3 downto 0);
12    LED_out : out STD_LOGIC_VECTOR (6 downto 0)
13 );
14
15 end RobertsonFPGA;
16
17 architecture Behavioral of RobertsonFPGA is
18
19 signal OP_1,OP_2 : boolean := false;

```

```

20 signal op1,op2: std_logic_vector (7 downto 0) := (others => '0') ;
21
22 signal start: std_logic := '0';
23 constant zero: std_logic_vector (7 downto 0) := (others => '0') ;
24 signal A1,Q1 : std_logic_vector (7 downto 0) := (others => '0') ;
25
26 signal value_to_display : std_logic_vector (15 downto 0);
27
28
29 component Robertson is
30     Port (
31         clock : in  STD_LOGIC;
32         X,Y : in  STD_LOGIC_VECTOR (7 downto 0);
33         start,reset : in STD_LOGIC;
34         A1, Q1: out STD_LOGIC_VECTOR (7 downto 0)
35
36     );
37 end component;
38
39
40 component SEV_SEG_DISP is
41     Port ( clock_50Mhz : in STD_LOGIC;
42           X : in STD_LOGIC_VECTOR (15 downto 0);
43           reset : in STD_LOGIC;
44           Anode_Activate : out STD_LOGIC_VECTOR (3 downto 0);
45           LED_out : out STD_LOGIC_VECTOR (6 downto 0)
46     );
47
48 end component;
49
50
51 begin
52
53
54 ROB : Robertson port map (
55     clock => clock_50Mhz,
56     X => op1,
57     Y => op2,
58     start => start,
59     reset => reset,
60     A1 => A1,
61     Q1 => Q1
62 );
63
64
65
66 SSD : SEV_SEG_DISP port map(
67     clock_50Mhz => clock_50Mhz,
68     X => value_to_display,

```

```

69     reset => reset,
70     Anode_Activate => Anode_Activate,
71     LED_out => LED_out
72 );
73
74
75 p: process (clock_50Mhz, reset)
76
77 begin
78
79     if (reset= '1') then
80         OP_1 <= false;
81         OP_2 <= false;
82         op1<= (others=>'0');
83         op2<= (others=>'0');
84         start <= '0';
85     elsif (rising_edge(clock_50Mhz)) then
86         if load1 = '1' then
87             start <= '0';
88             op1 <= X;
89             OP_1 <= true;
90             OP_2 <= false;
91
92         elsif load2 = '1' then
93             op2 <= X;
94             OP_2 <= true;
95         end if;
96
97         if (OP_1 = true and OP_2 = true) then
98             if result = '1' then
99                 start <= '1';
100                 value_to_display <= A1 & Q1;
101             end if;
102         else
103             value_to_display <= zero & X;
104         end if;
105
106     end if;
107
108
109 end process;
110
111 end Behavioral;

```

Codice Componente 10.7: Sintesi Robertson

### 10.4.2 File UCF



```

1
2 NET "LED_out<6>" LOC = "L18"; # Bank = 1, Pin name = IO_L10P_1, Type = I/O,
  Sch name = CA
3 NET "LED_out<5>" LOC = "F18"; # Bank = 1, Pin name = IO_L19P_1, Type = I/O,
  Sch name = CB
4 NET "LED_out<4>" LOC = "D17"; # Bank = 1, Pin name = IO_L23P_1/HDC, Type =
  DUAL, Sch name = CC
5 NET "LED_out<3>" LOC = "D16"; # Bank = 1, Pin name = IO_L23N_1/LDC0, Type =
  DUAL, Sch name = CD
6 NET "LED_out<2>" LOC = "G14"; # Bank = 1, Pin name = IO_L20P_1, Type = I/O,
  Sch name = CE
7 NET "LED_out<1>" LOC = "J17"; # Bank = 1, Pin name = IO_L13P_1/A6/RHCLK4/
  IRDY1, Type = RHCLK/DUAL, Sch name = CF
8 NET "LED_out<0>" LOC = "H14"; # Bank = 1, Pin name = IO_L17P_1, Type = I/O,
  Sch name = CG
9
10 NET "clock_50Mhz" LOC = "B8"; # Bank = 0, Pin name = IP_L13P_0/GCLK8, Type
  = GCLK, Sch name = GCLK0
11 NET "Anode_Activate<0>" LOC = "F17"; # Bank = 1, Pin name = IO_L19N_1, Type
  = I/O, Sch name = AN0
12 NET "Anode_Activate<1>" LOC = "H17"; # Bank = 1, Pin name = IO_L16N_1/A0,
  Type = DUAL, Sch name = AN1
13 NET "Anode_Activate<2>" LOC = "C18"; # Bank = 1, Pin name = IO_L24P_1/LDC1,
  Type = DUAL, Sch name = AN2
14 NET "Anode_Activate<3>" LOC = "F15"; # Bank = 1, Pin name = IO_L21P_1, Type
  = I/O, Sch name = AN3
15
16
17 NET "X<0>" LOC = "G18"; # Sch name = SW0
18 NET "X<1>" LOC = "H18"; # Sch name = SW1
19 NET "X<2>" LOC = "K18"; # Sch name = SW2
20 NET "X<3>" LOC = "K17"; # Sch name = SW3
21 NET "X<4>" LOC = "L14";
22 NET "X<5>" LOC = "L13";
23 NET "X<6>" LOC = "N17";
24 NET "X<7>" LOC = "R17";
25
26
27 NET "load1" LOC = "B18";
28 NET "load2" LOC = "D18";
29 NET "result" LOC = "E18";
30 NET "reset" LOC = "H13";

```

Codice Componente 10.8: Definizione del file UCF

# Capitolo 11

## Esercizio 11

### 11.1 Traccia

Sfruttando l'implementazione fornita dalla Digilent di un dispositivo UART (RS232RefComp.vhd), progettare ed implementare in VHDL i seguenti componenti:


- a) UART\_TAPPO: il componente acquisisce una stringa di 8 bit (fornita attraverso gli switch della board di sviluppo) e la serializza tramite la sezione di trasmissione del dispositivo UART; l'output seriale della UART viene re-inviato in ingresso alla sezione di ricezione dello stesso dispositivo (configurazione a tappo), e il dato deserializzato viene visualizzato sui led della board di sviluppo.

- b) 2\_UART: il componente acquisisce una stringa di 8 bit (fornita dall'utente tramite gli switch della board di sviluppo), la serializza tramite la sezione di trasmissione di un primo dispositivo UART, la deserializza tramite la sezione di ricezione di un secondo dispositivo UART collegato a valle del primo, e mostra le stringa led della board di sviluppo.


- c) UART\_PC (facoltativo): il componente realizza la comunicazione fra la board di sviluppo e un terminale seriale in esecuzione su PC (es. Termite), previa connessione di PC e board tramite dispositivo fisico RS232 (uno degli endpoint di comunicazione è rappresentato dal PC). Il componente deve poter acquisire una stringa di 8 bit che rappresenta un carattere in codifica ASCII (fornita attraverso gli switch della board di sviluppo), ed inviarla tramite il dispositivo UART al terminale in esecuzione sul PC, in cui il carattere viene visualizzato. Allo stesso modo, il componente deve essere in grado di ricevere attraverso lo stesso dispositivo UART (oppure una seconda UART) un carattere trasmesso dal terminale e mostrarlo sui led.
 
### 11.2 UART RS232


L'UART RS232 è un dispositivo di comunicazione asincrona che permette di serializzare il dato in trasmissione, di parallelizzare il dato in ricezione, di gestire il protocollo asincrono verso l'interlocutore collegato e di controllare e segnalare errori.



Il dispositivo possiede due componenti principali : uno per ricevere informazioni seriali e uno per trasmetterle. Il ricevitore prende in ingresso sulla porta RXD un byte in forma seriale e lo converte in una informazione parallela, che viene posta in uscita sulla porta DBOUT. Il blocco trasmettitore prende in ingresso l'uscita di DBOUT e converte il byte in seriale, ritrasmettendolo in uscita su TXD.

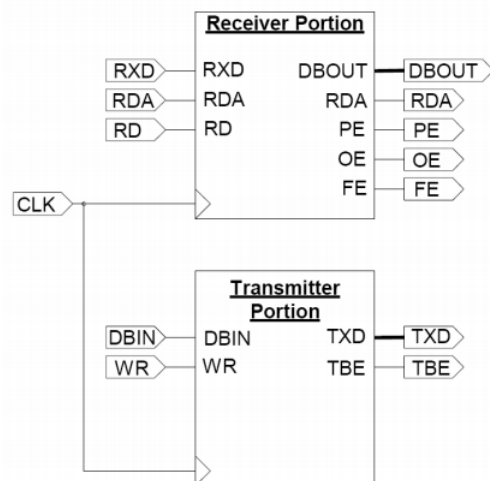

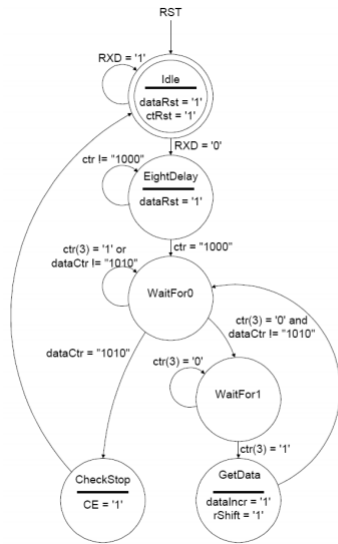
Il comportamento della UART in ricezione e in trasmissione viene descritto tramite dei diagrammi a stati finiti. Il primo che viene mostrato è quello relativo alla ricezione.



Il ricevitore include un controllore seriale, due contatori usati per la sincronizzazione, uno shift register e un controllo dell'errore sui bit. Lo shift register è usato per memorizzare i dati provenienti dalla porta RXD. Quando un ciclo di lettura è chiuso, lo shift register è pronto per acquisire il byte ricevuto. Inoltre un controllore è necessario per sincronizzare la fase di acquisizione.

Il sistema rimane nello stato di idle fin quando RXD è 1. Quando RXD è 0, si passa allo stato di EightDelay, che viene usato per consentire ai dati di essere letti da RXD nel mezzo della trasmissione. Un contatore ctr conta fino a 8 per acquisire il byte in input. Quando il contatore arriva ad 8 si passa allo stato WaitFor0 e successivamente a WaitFor1. Entrambi questi stati controllano il bit più significativo di ctr. Essi inoltre consentono alla macchina di attendere per il periodo di tempo necessario a leggere il segnale proveniente da RXD nel mezzo della prossima trasmissione. Lo stato successivo, Get Data, usa lo shift register per memorizzare i dati provenienti da RXD e usa un contatore DataCtr per tenere traccia di quanti bit sono stati shiftati. Quando il contatore arriva a 10 (8 bit di dati, 1 bit di parità e 1 bit di stop) si passa allo stato CheckStop, che abilita il controllo sull'errore, e una volta terminato torna allo stato di idle ponendo il sistema in attesa di nuovi dati.

 Di seguito si mostra il diagramma a stati finiti per quando riguarda la trasmissione.




Il trasmettitore comprende un controllore per la trasmissione, due contatori per la sincronizzazione

e uno shift register di trasferimento. Esso accetta in ingresso i byte provenienti dalla porta DBIN e li trasmette come dati seriali sulla porta TXD. Similmente a come visto per la precedente macchina a stati, il trasmettitore rimane in uno stato di idle finché WR è basso. Quando WR è alto, passa allo stato di Transfer che prepara lo shift register al trasferimento. Ponendo Load = 1, lo shift register è caricato con un bit di start, il byte in DBIN, un bit di parità e un bit di stop. I due segnali di reset vengono posti ad 1 per i due contatori di sincronizzazione.

Il prossimo stato è ShiftState, che pone il segnale di shift a 1 per effettuare l'operazione di shift a destra e tflncr viene anch'esso posto ad 1 per incrementare il contatore dei dati. Quando questo contatore è pari a 9 se non tutti i dati sono stati trasferiti si va nello stato di Delay, da cui si ritorna quando il tDelayCtr è uguale al baudRate.

Una volta entrati nello stato di WaitWrite, la trasmissione è completata. Questo stato è necessario ad assicurarsi che il segnale WR sia stato mantenuto alto durante il processo di trasferimento.

### 11.2.1 Schematici

 

### 11.2.2 Codice

Viene mostrata l'implementazione fornita del RS232RefComp così come descritta.

#### 11.2.2.1 RS232RefComp2

```

1  -----
2  --
3  -- uartcomponent.vhd
4  -----
5  -- Author:   Dan Pederson
6  --           Copyright 2004 Digilent, Inc.
7  -----
8  -- Description: This file defines a UART which transfers data to and
9  --               from serial and parallel information. It requires two
10 --               major processes: receiving and transferring. The
11 --               receiving portion reads serially transmitted data, and

```

```

12  --      converts it into parallel data, while the transferring
13  --      portion reads parallel data, and transmits it as serial
14  --      data. There are three error signals provided with this
15  --      UART. They are frame error, parity error, and overwrite
16  --      error signals. This UART is configured to use an ODD
17  --      parity bit at a baud rate of 9600.
18  --
19  -----
20  -- Revision History:
21  --      07/15/04 (DanP) Created
22  --      05/24/05 (DanP) Updated commenting style
23  --      06/06/05 (DanP) Synchronized state machines to fix timing bug
24  -----
25
26  library IEEE;
27  use IEEE.STD_LOGIC_1164.ALL;
28  use IEEE.STD_LOGIC_ARITH.ALL;
29  use IEEE.STD_LOGIC_UNSIGNED.ALL;
30
31  -----
32  --
33  --Title:  UARTcomponent entity
34  --
35  --Inputs: 7 : RXD
36  --          CLK
37  --          DBIN
38  --          RDA
39  --          RD
40  --          WR
41  --          RST
42  --
43  --Outputs: 7 : TXD
44  --          DBOUT
45  --          RDA
46  --          TBE
47  --          PE
48  --          FE
49  --          OE
50  --
51  --Description: This describes the UART component entity. The inputs are
52  --              the Pegasus 50 MHz clock, a reset button, The RXD from
53  --              the serial cable, an 8-bit data bus from the parallel
54  --              port, and Read Data Available (RDA) and Transfer Buffer
55  --              Empty(TBE) handshaking signals. The outputs are the TXD
56  --              signal for the serial port, an 8-bit data bus for the
57  --              parallel port, RDA and TBE handshaking signals, and three
58  --              error signals for parity, frame, and overwrite errors.
59  --
60  -----

```

```

61 entity UARTcomponent is
62   Generic (
63     --@48MHz
64     BAUD_DIVIDE_G : integer := 26;  --115200 baud
65     BAUD_RATE_G   : integer := 417
66
67     --@26.6MHz
68     BAUD_DIVIDE_G : integer := 14;  --115200 baud
69     BAUD_RATE_G   : integer := 231
70   );
71   Port (
72     TXD    : out    std_logic    := '1';           -- Transmitted serial data
73             output
74     RXD    : in     std_logic;           -- Received serial data input
75     CLK    : in     std_logic;           -- Clock signal
76     DBIN   : in     std_logic_vector (7 downto 0); -- Input parallel data
77             to be transmitted
78     DBOUT  : out    std_logic_vector (7 downto 0); -- Received parallel
79             data output
80     RDA    : inout  std_logic;           -- Read Data Available
81     TBE    : out    std_logic    := '1';           -- Transfer Buffer Emty
82     RD     : in     std_logic;           -- Read Strobe
83     WR     : in     std_logic;           -- Write Strobe
84     PE     : out    std_logic;           -- Parity error
85     FE     : out    std_logic;           -- Frame error
86     OE     : out    std_logic;           -- Overwrite error
87     RST    : in     std_logic := '0';           -- Reset signal
88
89 end UARTcomponent;
90
91 architecture Behavioral of UARTcomponent is
92
93   -----
94   -- Local Type and Signal Declarations
95   -----
96
97   --Title:  Local Type Declarations
98   --
99   --Description:  There are two state machines used in this entity.  The
100   --               rstate is used to synchronize the receiving portion of
101   --               the UART, and the tstate is used to synchronize the
102   --               sending portion of the UART.
103   -----
104
105   type rstate is (
106     strIdle,
107     strEightDelay,
108     strGetData,

```

```

107     strWaitFor0,
108     strWaitFor1,
109     strCheckStop
110 );
111
112 type tstate is (
113     sttIdle,
114     sttTransfer,
115     sttShift,
116     sttDelay,
117     sttWaitWrite
118 );
119
120 -----
121 --
122 --Title:  Local Signal Declarations
123 --
124 --Description:  The constants and signals used by this entity are
125 --              described below:
126 --
127 --          -baudRate : This is the Baud Rate constant used to
128 --                      synchronize the Pegasus 50 MHz clock with a
129 --                      baud rate of 9600. To get this number, divide
130 --                      50MHz by 9600.
131 --          -baudDivide : This is the Baud Rate divider used to safely
132 --                      read data transmitted at a baud rate of 9600.
133 --                      It is simply the above described baudRate
134 --                      constant divided by 16.
135 --
136 --          -rdReg      : this is the receive holding register
137 --          -rdSReg      : this is the receive shift register
138 --          -tfReg       : this is the transfer holding register
139 --          -tfSReg      : this is the transfer shifting register
140 --          -clkDiv      : counter used to get rClk
141 --          -ctr         : used for delay times
142 --          -tfCtr       : used to delay in the transfer process
143 --          -dataCtr     : counts the number of read data bits
144 --          -parError    : parity error bit
145 --          -frameError  : frame error bit
146 --          -CE          : clock enable bit for the writing latch
147 --          -ctRst       : reset for the ctr
148 --          -load        : load signal used to load the transfer shift
149 --                      register
150 --          -shift       : shift signal used to unload the transfer
151 --                      shift register
152 --          -par         : represents the parity in the transfer
153 --                      holding register
154 --          -tClkRST     : reset for the tfCtr
155 --          -rShift      : shift signal used to load the receive shift

```



```

156 --          register
157 --      -dataRST  : reset for the dataCtr
158 --      -dataIncr : signal to increment the dataCtr
159 --      -tfIncr   : signal to increment the tfCtr
160 --      -tDelayCtr : counter used to delay the transfer state
161 --          machine.
162 --      -tDelayRst : reset signal for the tDelayCtr counter.
163 --
164 --      The following signals are used by the two state machines
165 --      for state control:
166 --      -Receive State Machine : strCur, strNext
167 --      -Transfer State Machine : sttCur, sttNext
168 --
169 -----
170
171 -- @26.7MHz
172 -- constant baudRate : std_logic_vector(12 downto 0) := "1 0100 0101 1000";
173 -- constant baudRate : std_logic_vector(12 downto 0) :=
174 --     conv_std_logic_vector(1406,13); -- 19200
175 -- constant baudRate : std_logic_vector(12 downto 0) :=
176 --     conv_std_logic_vector(703,13); -- 38400
177 -- constant baudRate : std_logic_vector(12 downto 0) :=
178 --     conv_std_logic_vector(469,13); -- 57600
179 -- constant baudRate : std_logic_vector(12 downto 0) :=
180 --     conv_std_logic_vector(417,13); --115200
181
182 -- @26.7MHz
183 -- constant baudDivide : std_logic_vector(8 downto 0) :=
184 --     conv_std_logic_vector(1,9); -- Used for simulation
185 -- constant baudDivide : std_logic_vector(8 downto 0) :=
186 --     conv_std_logic_vector(88,9); -- Used for 19 200 baud
187 -- constant baudDivide : std_logic_vector(8 downto 0) :=
188 --     conv_std_logic_vector(44,9); -- Used for 38 400 baud
189 -- constant baudDivide : std_logic_vector(8 downto 0) :=
190 --     conv_std_logic_vector(29,9); -- Used for 57 600 baud
191 -- constant baudDivide : std_logic_vector(8 downto 0) :=
192 --     conv_std_logic_vector(26,9); -- Used for 115 200 baud
193
194 constant baudRate : std_logic_vector(12 downto 0) :=
195     conv_std_logic_vector(BAUD_RATE_G,13); --115200
196 constant baudDivide : std_logic_vector(8 downto 0) :=
197     conv_std_logic_vector(BAUD_DIVIDE_G-1,9); -- Used for 115 200 baud
198
199 signal rdReg      : std_logic_vector(7 downto 0) := "00000000";
200 signal rdSReg     : std_logic_vector(9 downto 0) := "1111111111";
201 signal tfReg      : std_logic_vector(7 downto 0);
202 signal tfSReg     : std_logic_vector(10 downto 0) := "111111111111";
203 signal clkDiv     : std_logic_vector(9 downto 0) := "0000000000";
204 signal ctr        : std_logic_vector(3 downto 0) := "0000";

```

```

194 signal tfCtr      : std_logic_vector(3 downto 0)      := "0000";
195 signal dataCtr    : std_logic_vector(3 downto 0)      := "0000";
196 signal parError   : std_logic;
197 signal frameError : std_logic;
198 signal CE        : std_logic;
199 signal ctRst      : std_logic := '0';
200 signal load       : std_logic := '0';
201 signal shift      : std_logic := '0';
202 signal par        : std_logic;
203 signal tClkRST    : std_logic := '0';
204 signal rShift     : std_logic := '0';
205 signal dataRST    : std_logic := '0';
206 signal dataIncr   : std_logic := '0';
207 signal tfIncr     : std_logic := '0';
208 signal tDelayCtr  : std_logic_vector (12 downto 0);
209 signal tDelayRst  : std_logic := '0';
210
211 signal strCur     : rstate := strIdle;
212 signal strNext    : rstate;
213 signal sttCur     : tstate := sttIdle;
214 signal sttNext    : tstate;
215
216 -----
217 -- Module Implementation
218 -----
219 begin
220 -----
221 --
222 --Title:   Initial signal definitions
223 --
224 --Description: The following lines of code define 4 internal and 1
225 --             external signal. The most significant bit of the rdSReg
226 --             signifies the frame error bit, so frameError is tied to
227 --             that signal. The parError is high if there is a parity
228 --             error, so it is set equal to the inverse of rdSReg(8)
229 --             XOR-ed with the data bits. In this manner, it can
230 --             determine if the parity bit found in rdSReg(8) matches
231 --             the data bits. The parallel information output is equal
232 --             to rdReg, so DBOUT is set equal to rdReg. Likewise, the
233 --             input parallel information is equal to DBIN, so tfReg is
234 --             set equal to DBIN. Because the tfSReg is used to shift
235 --             out transmitted data, the TXD port is set equal to the
236 --             first bit of tfsReg. Finally, the par signal represents
237 --             the parity of the data, so par is set to the inverse of
238 --             the data bits XOR-ed together. This UART can be changed
239 --             to use EVEN parity if the "not" is omitted from the par
240 --             definition.
241 --
242 -----

```

```

243 frameError <= not rdSReg(9);
244 parError <= not ( rdSReg(8) xor ((rdSReg(0) xor rdSReg(1)) xor
245   (rdSReg(2) xor rdSReg(3))) xor ((rdSReg(4) xor rdSReg(5)) xor
246   (rdSReg(6) xor rdSReg(7)))) );
247 DBOUT <= rdReg;
248 tfReg <= DBIN;
249 TXD <= tfsReg(0);
250 par <= not ( ((tfReg(0) xor tfReg(1)) xor (tfReg(2) xor tfReg(3))) xor
251   ((tfReg(4) xor tfReg(5)) xor (tfReg(6) xor tfReg(7))) );
252 -----
253 --
254 --Title: Clock Divide counter
255 --
256 --Description: This process defines clkDiv as a signal that increments
257 --             with the clock up until it is either reset by ctRst, or
258 --             equals baudDivide. This signal is used to define a
259 --             counter called ctr that increments at the rate of the
260 --             divided baud rate.
261 --
262 -----
263 process (CLK, clkDiv)
264 begin
265   if (CLK = '1' and CLK'event) then
266     if (clkDiv = baudDivide or ctRst = '1') then
267       clkDiv <= "0000000000";
268     else
269       clkDiv <= clkDiv +1;
270     end if;
271   end if;
272 end process;
273 -----
274 --
275 --Title: Transfer delay counter
276 --
277 --Description: This process defines tDelayCtr as a counter that runs
278 --             until it equals baudRate, or until it is reset by
279 --             tDelayRst. This counter is used to measure delay times
280 --             when sending data out on the TXD signal. When the
281 --             counter is equal to baudRate, or is reset, it is set
282 --             equal to 0.
283 --
284 -----
285 process (CLK, tDelayCtr)
286 begin
287   if (CLK = '1' and CLK'event) then
288     if (tDelayCtr = baudRate or tDelayRst = '1') then
289       tDelayCtr <= "00000000000000";
290     else
291       tDelayCtr <= tDelayCtr+1;

```

```

292     end if;
293     end if;
294 end process;
295 -----
296 --
297 --Title: ctr set up
298 --
299 --Description: This process sets up ctr, which uses clkDiv to count
300 --             increase at a rate needed to properly receive data in
301 --             from RXD. If ctRst is strobed, the counter is reset. If
302 --             clkDiv is equal to baudDivide, then ctr is incremented
303 --             once. This signal is used by the receiving state machine
304 --             to measure delay times between RXD reads.
305 --
306 -----
307 process (CLK)
308 begin
309     if CLK = '1' and CLK'Event then
310         if ctRst = '1' then
311             ctr <= "0000";
312         elsif clkDiv = baudDivide then
313             ctr <= ctr + 1;
314         else
315             ctr <= ctr;
316         end if;
317     end if;
318 end process;
319 -----
320 --
321 --Title: transfer counter
322 --
323 --Description: This process makes tfCtr increment whenever the tfIncr
324 --             signal is strobed high. If the tClkRst signal is strobed
325 --             high, the tfCtr is reset to "0000." This counter is used
326 --             to keep track of how many data bits have been
327 --             transmitted.
328 --
329 -----
330 process (CLK, tClkRST)
331 begin
332     if (CLK = '1' and CLK'event) then
333         if tClkRST = '1' then
334             tfCtr <= "0000";
335         elsif tfIncr = '1' then
336             tfCtr <= tfCtr + 1;
337         end if;
338     end if;
339 end process;
340 -----

```

```

341 --
342 --Title: Error and RDA flag controller
343 --
344 --Description: This process controls the error flags FE, OE, and PE, as
345 --              well as the Read Data Available (RDA) flag. When CE goes
346 --              high, it means that data has been read into the rdSReg.
347 --              This process then analyzes the read data for errors, sets
348 --              rdReg equal to the eight data bits in rdSReg, and flags
349 --              RDA to indicate that new data is present in rdReg. FE
350 --              and PE are simply equal to the frameError and parError
351 --              signals. OE is flagged high if RDA is already high when
352 --              CE is strobed. This means that unread data was still in
353 --              the rdReg when it was written over with the new data.
354 --
355 -----
356 process (CLK, RST, RD, CE)
357 begin
358     if RD = '1' or RST = '1' then
359         FE <= '0';
360         OE <= '0';
361         RDA <= '0';
362         PE <= '0';
363     elsif CLK = '1' and CLK'event then
364         if CE = '1' then
365             FE <= frameError;
366             PE <= parError;
367             rdReg(7 downto 0) <= rdSReg (7 downto 0);
368             if RDA = '1' then
369                 OE <= '1';
370             else
371                 OE <= '0';
372                 RDA <= '1';
373             end if;
374         end if;
375     end if;
376 end process;
377 -----
378 --
379 --Title: Receiving shift register
380 --
381 --Description: This process controls the receiving shift register
382 --              (rdSReg). Whenever rShift is high, implying that data
383 --              needs to be shifted in, rdSReg is shifts in RXD to the
384 --              most significant bit, while shifting its existing data
385 --              right.
386 --
387 -----
388 process (CLK, rShift)
389 begin

```

```

390     if CLK = '1' and CLK'Event then
391         if rShift = '1' then
392             rdSReg <= (RXD & rdSReg(9 downto 1));
393         end if;
394     end if;
395 end process;
396 -----
397 --
398 --Title: Incoming Data counter
399 --
400 --Description: This process controls the dataCtr to keep track of
401 --              shifted values into the rdSReg. The dataCtr signal is
402 --              incremented once every time dataIncr is strobed high.
403 --
404 -----
405
406 process (CLK, dataRST)
407 begin
408     if (CLK = '1' and CLK'event) then
409         if dataRST = '1' then
410             dataCtr <= "0000";
411         elsif dataIncr = '1' then
412             dataCtr <= dataCtr +1;
413         end if;
414     end if;
415 end process;
416 -----
417 --
418 --Title: Receiving State Machine controller
419 --
420 --Description: This process takes care of the Receiving state machine
421 --              movement. It causes the next state to be evaluated on
422 --              each rising edge of CLK. If the RST signal is strobed,
423 --              the state is changed to the default starting state,
424 --              which is strIdle
425 --
426 -----
427 process (CLK, RST)
428 begin
429     if CLK = '1' and CLK'Event then
430         if RST = '1' then -- najj
431             strCur <= strIdle;
432         else
433             strCur <= strNext;
434         end if;
435     end if;
436 end process;
437 -----
438 --

```

```

439 --Title: Receiving State Machine
440 --
441 --Description: This process contains all of the next state logic for the
442 --      Receiving state machine.
443 --
444 -----
445 process (strCur, ctr, RXD, dataCtr)
446 begin
447     case strCur is
448 -----
449 --
450 --Title: strIdle state
451 --
452 --Description: This state is the idle and startup default stage for the
453 --      Receiving state machine. The machine stays in this state
454 --      until the RXD signal goes low. When this occurs, the
455 --      ctRst signal is strobed to reset ctr for the next state,
456 --      which is strEightDelay.
457 --
458 -----
459     when strIdle =>
460         dataIncr <= '0';
461         rShift <= '0';
462         dataRst <= '1';
463         CE <= '0';
464         ctRst <= '1';
465
466         if RXD = '0' then
467             strNext <= strEightDelay;
468         else
469             strNext <= strIdle;
470         end if;
471 -----
472 --
473 --Title: strEightDelay state
474 --
475 --Description: This state simply delays the state machine for eight clock
476 --      cycles. This is needed so that the incoming RXD data
477 --      signal is read in the middle of each data emission. This
478 --      ensures an accurate RXD signal reading. ctr counts from
479 --      0 to 8 to keep track of rClk cycles. When it equals 8
480 --      (1000) the next state, strWaitFor0, is loaded. During
481 --      this state, the dataRst signal is strobed high to reset
482 --      the shift-in data counter (dataCtr).
483 --
484 -----
485     when strEightDelay =>
486         dataIncr <= '0';
487         rShift <= '0';

```



```

488     dataRst <= '1';
489     CE <= '0';
490     ctRst <= '0';
491
492     if ctr(3 downto 0) = "1000" then
493         strNext <= strWaitFor0;
494     else
495         strNext <= strEightDelay;
496     end if;
497 -----
498 --
499 --Title: strGetData state
500 --
501 --Description: In this state, the dataIncr and rShift signals are
502 --             strobed high for one clock cycle. By doing this, the
503 --             rdSReg shift register shifts in RXD once, while the
504 --             dataCtr is incremented by one. This state simply
505 --             captures the incoming data on RXD into the rdSReg shift
506 --             register. The next state loaded is strWaitFor0, which
507 --             starts the two delay states needed between data shifts.
508 --
509 -----
510     when strGetData =>
511         CE <= '0';
512         dataRst <= '0';
513         ctRst <= '0';
514         dataIncr <= '1';
515         rShift <= '1';
516
517         strNext <= strWaitFor0;
518 -----
519 --
520 --Title: strWaitFor0 state
521 --
522 --Description: This state is a delay state, which delays the receive
523 --             state machine if not all of the incoming serial data has
524 --             not been shifted in yet. If dataCtr does not equal 10
525 --             (1010), the state is stayed in until the fourth bit of
526 --             ctr is equal to 1. When this happens, half of the delay
527 --             has been achieved, and the second delay state is loaded,
528 --             which is strWaitFor1. If dataCtr does equal 10 (1010),
529 --             all of the needed data has been acquired, so the
530 --             strCheckStop state is loaded to check for errors and
531 --             reset the receive state machine.
532 --
533 -----
534     when strWaitFor0 =>
535         CE <= '0';
536         dataRst <= '0';

```



```

537         ctRst <= '0';
538         dataIncr <= '0';
539         rShift <= '0';
540
541         if dataCtr = "1010" then
542             strNext <= strCheckStop;
543         elsif ctr(3) = '0' then
544             strNext <= strWaitFor1;
545         else
546             strNext <= strWaitFor0;
547         end if;
548 -----
549 --
550 --Title: strEightDelay state
551 --
552 --Description: This state is much like strWaitFor0, except it waits for
553 --             the fourth bit of ctr to equal 1. Once this occurs, the
554 --             strGetData state is loaded in order to shift in the next
555 --             data bit from RXD. Because strWaitFor0 is the only state
556 --             that calls this state, no other signals need to be
557 --             checked.
558 --
559 -----
560 when strWaitFor1 =>
561     CE <= '0';
562     dataRst <= '0';
563     ctRst <= '0';
564     dataIncr <= '0';
565     rShift <= '0';
566
567     if ctr(3) = '0' then
568         strNext <= strWaitFor1;
569     else
570         strNext <= strGetData;
571     end if;
572 -----
573 --
574 --Title: strCheckStop state
575 --
576 --Description: This state allows the newly acquired data to be checked
577 --             for errors. The CE flag is strobed to start the
578 --             previously defined error checking process. This state is
579 --             passed straight through to the strIdle state.
580 --
581 -----
582 when strCheckStop =>
583     dataIncr <= '0';
584     rShift <= '0';
585     dataRst <= '0';

```

```

586         ctRst <= '0';
587         CE <= '1';
588         strNext <= strIdle;
589     end case;
590 end process;
591 -----
592 --
593 --Title: Transfer shift register controller
594 --
595 --Description: This process uses the load, shift, and clk signals to
596 --              control the transfer shift register (tfSReg). Once load
597 --              is equal to '1', the tfSReg gets a '1', the parity bit,
598 --              the data bits found in tfReg, and a '0'. Under this
599 --              format, the shift register can be used to shift out the
600 --              appropriate signal to serially transfer the data. The
601 --              data is shifted out of the tfSReg whenever shift = '1'.
602 --
603 -----
604 process (load, shift, CLK, tfSReg)
605 begin
606     if CLK = '1' and CLK'Event then
607         if load = '1' then
608             tfSReg (10 downto 0) <= ('1' & par & tfReg(7 downto 0) & '0');
609         elsif shift = '1' then
610             tfSReg (10 downto 0) <= ('1' & tfSReg(10 downto 1));
611         end if;
612     end if;
613 end process;
614 -----
615 --
616 --Title: Transfer State Machine controller
617 --
618 --Description: This process takes care of the Transfer state machine
619 --              movement. It causes the next state to be evaluated on
620 --              each rising edge of CLK. If the RST signal is strobed,
621 --              the state is changed to the default starting state, which
622 --              is sttIdle.
623 --
624 -----
625 process (CLK, RST)
626 begin
627     if (CLK = '1' and CLK'Event) then
628         if RST = '1' then
629             sttCur <= sttIdle;
630         else
631             sttCur <= sttNext;
632         end if;
633     end if;
634 end process;

```

```

635 -----
636 --
637 --Title: Transfer State Machine
638 --
639 --Description: This process controls the next state logic in the
640 --      transfer state machine. The transfer state machine
641 --      controls the shift and load signals that are used to load
642 --      and transmit the parallel data in a serial form. It also
643 --      controls the Transmit Buffer Empty (TBE) signal that
644 --      indicates if the transmit buffer (tfSReg) is in use or
645 --      not.
646 --
647 -----
648 process (sttCur, tfCtr, WR, tDelayCtr)
649 begin
650     case sttCur is
651 -----
652 --
653 --Title: sttIdle state
654 --
655 --Description: This state is the idle and startup default stage for the
656 --      transfer state machine. The state is stayed in until
657 --      the WR signal goes high. Once it goes high, the
658 --      sttTransfer state is loaded. The load and shift signals
659 --      are held low in the sttIdle state, while the TBE signal
660 --      is held high to indicate that the transmit buffer is not
661 --      currently in use. Once the idle state is left, the TBE
662 --      signal is held low to indicate that the transfer state
663 --      machine is using the transmit buffer.
664 --
665 -----
666     when sttIdle =>
667         TBE <= '1';
668         tClkRST <= '0';
669         tfIncr <= '0';
670         shift <= '0';
671         load <= '0';
672         tDelayRst <= '1';
673
674         if WR = '0' then
675             sttNext <= sttIdle;
676         else
677             sttNext <= sttTransfer;
678         end if;
679 -----
680 --
681 --Title: sttTransfer state
682 --
683 --Description: This state sets the load, tClkRST, and tDelayRst signals

```

```

684 --      high, while setting the TBE signal low. The load signal
685 --      is set high to load the transfer shift register with the
686 --      appropriate data, while the tClkRST and tDelayRst signals
687 --      are strobed to reset the tfCtr and tDelayCtr. The next
688 --      state loaded is the sttDelay state.
689 --
690 -----
691     when sttTransfer =>
692         TBE <= '0';
693         shift <= '0';
694         load <= '1';
695         tClkRST <= '1';
696         tfIncr <= '0';
697         tDelayRst <= '1';
698
699         sttNext <= sttDelay;
700 -----
701 --
702 --Title: sttShift state
703 --
704 --Description: This state strobes the shift and tfIncr signals high, and
705 --      checks the tfCtr to see if enough data has been
706 --      transmitted. By strobing the shift and tfIncr signals
707 --      high, the tfSReg is shifted, and the tfCtr is incremented
708 --      once. If tfCtr does not equal 9 (1001), then not all of
709 --      the bits have been transmitted, so the next state loaded
710 --      is the sttDelay state. If tfCtr does equal 9, the final
711 --      state, sttWaitWrite, is loaded.
712 --
713 -----
714     when sttShift =>
715         TBE <= '0';
716         shift <= '1';
717         load <= '0';
718         tfIncr <= '1';
719         tClkRST <= '0';
720         tDelayRst <= '0';
721
722         if tfCtr = "1010" then
723             sttNext <= sttWaitWrite;
724         else
725             sttNext <= sttDelay;
726         end if;
727 -----
728 --
729 --Title: sttDelay state
730 --
731 --Description: This state is responsible for delaying the transfer state
732 --      machine between transmissions. All signals are held low

```

```

733 --      while the tDelayCtr is tested.  Once tDelayCtr is equal
734 --      to baudRate, the sttShift state is loaded.
735 --
736 -----
737     when sttDelay =>
738         TBE <= '0';
739         shift <= '0';
740         load <= '0';
741         tClkRst <= '0';
742         tfIncr <= '0';
743         tDelayRst <= '0';
744
745         if tDelayCtr = baudRate then
746             sttNext <= sttShift;
747         else
748             sttNext <= sttDelay;
749         end if;
750 -----
751 --
752 --Title: sttWaitWrite state
753 --
754 --Description: This state checks to make sure that the initial WR signal
755 --              that triggered the transfer state machine has been
756 --              brought back low.  Without this state, a write signal
757 --              that is held high for a long time will result in multiple
758 --              transmissions.  Once the WR signal is low, the sttIdle
759 --              state is loaded to reset the transfer state machine.
760 --
761 -----
762     when sttWaitWrite =>
763         TBE <= '0';
764         shift <= '0';
765         load <= '0';
766         tClkRst <= '0';
767         tfIncr <= '0';
768         tDelayRst <= '0';
769
770         if WR = '1' then
771             sttNext <= sttWaitWrite;
772         else
773             sttNext <= sttIdle;
774         end if;
775     end case;
776 end process;
777 end Behavioral;



```

Codice Componente 11.1: RS232RefComp2.vhd

## 11.3 Soluzione a) Uart Tappo

In ingresso al sistema abbiamo il clock, il byte che deve essere acquisito attraverso gli switch e il reset; l'uscita coincide invece con l'uscita in parallelo del componente UART.

### 11.3.1 Schematici

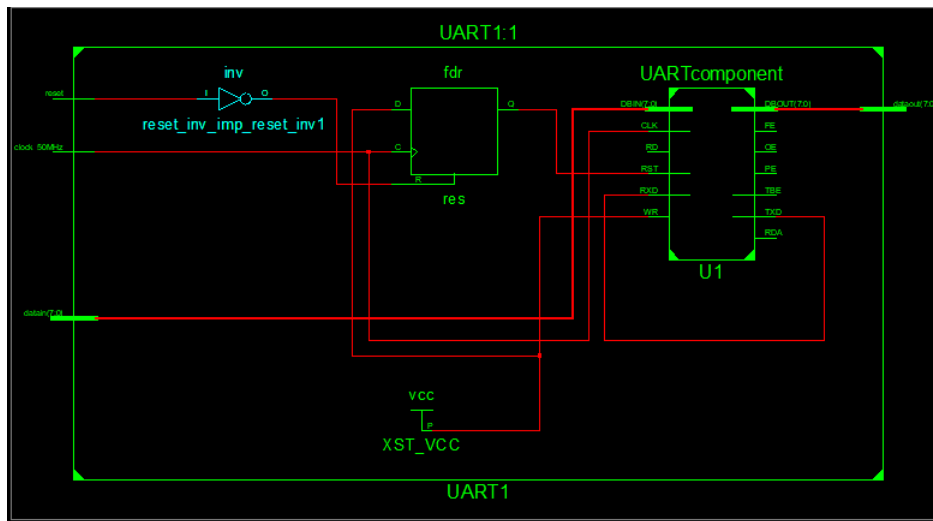 

### 11.3.2 Codice

L'uscita TXD del componente UART viene collegata direttamente all'ingresso RXD in retroazione, in questo modo dati ricevuti saranno pari a quelli trasmessi. Il byte acquisito in parallelo attraverso gli switch viene posto in ingresso a DBIN, l'uscita in parallelo DBOUT è collegata all'uscita dataout del sistema e viene visualizzata attraverso l'accensione dei led della scheda.

#### 11.3.2.1 UART Tappo

```
1
2 library IEEE;
```

```

3 use IEEE.STD_LOGIC_1164.ALL;
4
5 entity UART1 is
6   Port (
7     clock_50MHz : in STD_LOGIC;
8     datain : in STD_LOGIC_VECTOR (7 downto 0);
9     reset : in std_logic;
10    dataout : out STD_LOGIC_VECTOR (7 downto 0) := (others=>'0')
11  );
12
13
14 end UART1;
15
16 architecture Behavioral of UART1 is
17
18   Component UARTcomponent is
19
20     Port (
21       TXD : out std_logic := '1';           -- Transmitted serial data
22         output
23       RXD : in std_logic;                     -- Received serial data input
24       CLK : in std_logic;                     -- Clock signal
25       DBIN : in std_logic_vector (7 downto 0); -- Input parallel data
26         to be transmitted
27       DBOUT : out std_logic_vector (7 downto 0); -- Received parallel
28         data output
29       RDA : inout std_logic;                  -- Read Data Available
30       TBE : out std_logic := '1';            -- Transfer Buffer Emty
31       RD : in std_logic;                      -- Read Strobe
32       WR : in std_logic;                      -- Write Strobe
33       PE : out std_logic;                     -- Parity error
34       FE : out std_logic;                     -- Frame error
35       OE : out std_logic;                     -- Overwrite error
36       RST : in std_logic := '0'
37     );
38   end Component;
39
40   signal din,dout,rd,td :std_logic:= '0';
41
42   signal t1,t_rda,t_tbe,t_pe,t_fe,t_oe: std_logic:= '0';
43
44 begin
45
46   U1: UARTcomponent PORT MAP (
47     TXD => t1,
48     RXD => t1,
49     CLK => clock_50MHz,
50     DBIN => datain,

```

```

49  DBOUT => dataout,
50  RDA => t_rda,
51  TBE => t_tbe,
52  RD => '0',
53  WR => '1',
54  PE => t_pe,
55  FE => t_fe,
56  OE => t_oe,
57  RST => reset
58 );
59
60
61 end Behavioral;

```

Codice Componente 11.2: Definizione del componente UART Tappo

## 11.4 Sintesi su board FPGA

I segnali in ingresso e in uscita sono mappati sulla board Nexys2 tramite switch e led. La UART si comporta da tappo e il segnale inserito tramite switch viene visualizzato correttamente sui led.

```

1
2
3 ##Leds
4
5 NET "dataout<0>" LOC = "J14"; # Bank = 1, Pin name = IO_L14N_1/A3/RHCLK7,
   Type = RHCLK/DUAL, Sch name = JD10/LD0
6 NET "dataout<1>" LOC = "J15"; # Bank = 1, Pin name = IO_L14P_1/A4/RHCLK6,
   Type = RHCLK/DUAL, Sch name = JD9/LD1
7 NET "dataout<2>" LOC = "K15"; # Bank = 1, Pin name = IO_L12P_1/A8/RHCLK2,
   Type = RHCLK/DUAL, Sch name = JD8/LD2
8 NET "dataout<3>" LOC = "K14"; # Bank = 1, Pin name = IO_L12N_1/A7/RHCLK3/
   TRDY1, Type = RHCLK/DUAL, Sch name = JD7/LD3
9 NET "dataout<4>" LOC = "E16"; # Bank = 1, Pin name = N.C., Type = N.C., Sch
   name = LD4? other than s3e500
10 NET "dataout<5>" LOC = "P16"; # Bank = 1, Pin name = N.C., Type = N.C., Sch
   name = LD5? other than s3e500
11 NET "dataout<6>" LOC = "E4"; # Bank = 3, Pin name = N.C., Type = N.C., Sch
   name = LD6? other than s3e500
12 NET "dataout<7>" LOC = "P4"; # Bank = 3, Pin name = N.C., Type = N.C., Sch
   name = LD7? other than s3e500
13
14 NET "clock_50MHz" LOC = "B8"; # Bank = 0, Pin name = IP_L13P_0/GCLK8, Type
   = GCLK, Sch name = GCLK0
15
16
17 ##Switch
18 NET "datain<0>" LOC = "G18"; # Sch name = SW0

```



```

19 NET "datain<1>"          LOC = "H18";    # Sch name = SW1
20 NET "datain<2>"          LOC = "K18";    # Sch name = SW2
21 NET "datain<3>"          LOC = "K17";    # Sch name = SW3
22 NET "datain<4>"          LOC = "L14";    # Sch name = SW4
23 NET "datain<5>"          LOC = "L13";    # Sch name = SW5
24 NET "datain<6>"          LOC = "N17";    # Sch name = SW6
25 NET "datain<7>"          LOC = "R17";    # Sch name = SW7
26
27 ## Buttons
28 #
29 NET "reset" LOC = "B18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name =
    BTN0



```

Codice Componente 11.3: Definizione del file UCF

## 11.5 Soluzione b) 2 UART

La stringa datain di 8 bit viene serializzata tramite il primo dispositivo UART: il segnale viene posto in ingresso a DBIN, viene serializzato dal blocco trasmettitore della prima UART e l'uscita TXD viene posta in ingresso al blocco ricevitore della seconda UART. Il segnale parallelizzato DBOUT ottenuto dalla seconda UART viene collegato all'uscita dataout.

### 11.5.1 Schematici

  

## 11.5.2 Codice

L'entità UART2 contiene due componenti UART dello stesso tipo, RS232. Per consentire il trasferimento dei dati, nel blocco trasmettore della prima UART vengono posti in ingresso WR e RD entrambi pari a '1', mentre nella seconda UART (in ricezione) entrambi pari a 0.

### 11.5.2.1 2UART

```

1
2
3 entity UART2 is
4   Port (
5       reset : in STD_LOGIC;
6       clock_50MHz : in STD_LOGIC;
7       datain : in STD_LOGIC_VECTOR (7 downto 0);
8       dataout : out STD_LOGIC_VECTOR (7 downto 0)
9   );
10
11 end UART2;
12
13 architecture Behavioral of UART2 is
14
15   Component UARTcomponent is
16
17       Port (
18
19           TXD    : out    std_logic    := '1';           -- Transmitted serial data
20               output
21           RXD    : in     std_logic;           -- Received serial data input
22           CLK    : in     std_logic;           -- Clock signal
23           DBIN   : in     std_logic_vector (7 downto 0); -- Input parallel data
24               to be transmitted
25           DBOUT  : out    std_logic_vector (7 downto 0); -- Received parallel
26               data output
27           RDA    : inout  std_logic;           -- Read Data Available
28           TBE    : out    std_logic    := '1';           -- Transfer Buffer Emty
29           RD     : in     std_logic;           -- Read Strobe
30           WR     : in     std_logic;           -- Write Strobe
31           PE     : out    std_logic;           -- Parity error
32           FE     : out    std_logic;           -- Frame error
33           OE     : out    std_logic;           -- Overwrite error
34           RST    : in     std_logic := '0'
35       );
36   end Component;
37
38   signal t_DBout, t_DBin : std_logic_vector(7 downto 0);
39   signal t,t_rda1,t_tbe1,t_rda2,t_tbe2,t_pe1,t_fe1,t_oe1,t_pe2,t_fe2,t_oe2,
40       t_WR2,t_RD2,t_txd2: std_logic:= '0';

```

```

38
39 begin
40
41
42 Tx: UARTcomponent PORT MAP (
43     TXD => t,
44     RXD => '1',
45     CLK => clock_50MHz,
46     DBIN => datain,
47     DBOUT => t_DBout,
48     RDA => t_rda1,
49     TBE => t_tbe1,
50     RD => '1',
51     WR => '1',
52     PE => t_pe1,
53     FE => t_fe1,
54     OE => t_oe1,
55     RST => reset
56 );
57
58 Rx: UARTcomponent PORT MAP (
59     TXD => t_txd2,
60     RXD => t,
61     CLK => clock_50MHz,
62     DBIN => t_DBin,
63     DBOUT => dataout,
64     RDA => t_rda2,
65     TBE => t_tbe2,
66     RD => '0',
67     WR => '0',
68     PE => t_pe2,
69     FE => t_fe2,
70     OE => t_oe2,
71     RST => reset
72 );
73
74
75 end Behavioral;

```

Codice Componente 11.4: Definizione del componente 2 UART

## 11.6 Sintesi su board FPGA

Per sintetizzare le UART su dispositivo NEXYS2 è sufficiente mappare i segnali su led e switch. Il segnale di ingresso DBIN viene inserito tramite gli switch ed è possibile visualizzare l'uscita corretta tramite i led (su cui sono mappati i bit del segnale dataout). Il segnale di reset viene invece collegato ad uno dei 4 bottoni disponibili.

```

1
2 ##Leds
3
4 NET "dataout<0>" LOC = "J14"; # Bank = 1, Pin name = IO_L14N_1/A3/RHCLK7,
   Type = RHCLK/DUAL, Sch name = JD10/LD0
5 NET "dataout<1>" LOC = "J15"; # Bank = 1, Pin name = IO_L14P_1/A4/RHCLK6,
   Type = RHCLK/DUAL, Sch name = JD9/LD1
6 NET "dataout<2>" LOC = "K15"; # Bank = 1, Pin name = IO_L12P_1/A8/RHCLK2,
   Type = RHCLK/DUAL, Sch name = JD8/LD2
7 NET "dataout<3>" LOC = "K14"; # Bank = 1, Pin name = IO_L12N_1/A7/RHCLK3/
   TRDY1, Type = RHCLK/DUAL, Sch name = JD7/LD3
8 NET "dataout<4>" LOC = "E16"; # Bank = 1, Pin name = N.C., Type = N.C., Sch
   name = LD4? other than s3e500
9 NET "dataout<5>" LOC = "P16"; # Bank = 1, Pin name = N.C., Type = N.C., Sch
   name = LD5? other than s3e500
10 NET "dataout<6>" LOC = "E4"; # Bank = 3, Pin name = N.C., Type = N.C., Sch
   name = LD6? other than s3e500
11 NET "dataout<7>" LOC = "P4"; # Bank = 3, Pin name = N.C., Type = N.C., Sch
   name = LD7? other than s3e500
12
13 NET "clock_50MHz" LOC = "B8"; # Bank = 0, Pin name = IP_L13P_0/GCLK8, Type
   = GCLK, Sch name = GCLK0
14
15
16 ##Switch
17 NET "datain<0>" LOC = "G18"; # Sch name = SW0
18 NET "datain<1>" LOC = "H18"; # Sch name = SW1
19 NET "datain<2>" LOC = "K18"; # Sch name = SW2
20 NET "datain<3>" LOC = "K17"; # Sch name = SW3
21 NET "datain<4>" LOC = "L14"; # Sch name = SW4
22 NET "datain<5>" LOC = "L13"; # Sch name = SW5
23 NET "datain<6>" LOC = "N17"; # Sch name = SW6
24 NET "datain<7>" LOC = "R17"; # Sch name = SW7
25
26
27 NET "reset" LOC = "B18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name =
   BTN0


```

Codice Componente 11.5: Definizione del file UCF
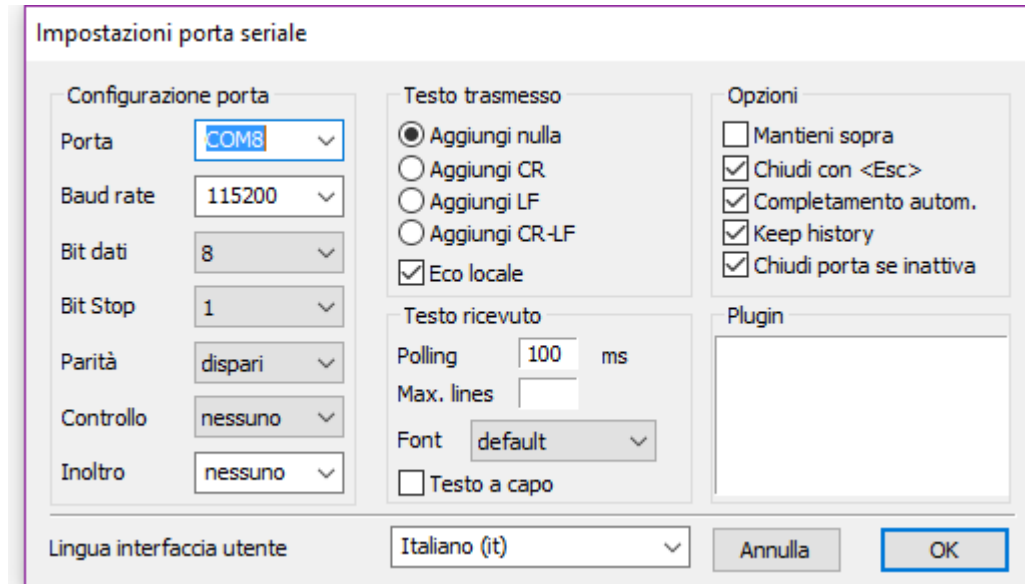
## 11.7 Soluzione c) UART\_PC (facoltativo)


La comunicazione tra PC e UART presente sullo schedino è stata gestita collegando un cavo seriale USB a RS232 alla scheda Nexys2. Il programma utilizzato per osservare i valori codificati in ASCII (e inseriti tramite switch) è Termite, un tool provvisto di terminale in grado di mostrare valori in ingresso e uscita. In configurazione porta si pone la porta COM8 (a cui è stato collegato fisicamente il cavo) e il baud rate a 115200, lo stesso definito per la scheda Nexys2. In questo caso

abbiamo 8 bit di dati da trasferire e 1 bit di stop, parità dispari.




Come esempio si mostrano alcuni dati casuali immessi tramite Nexys2, 11110101 e 11111100 che vengono ricevuti e convertiti in ASCII.


CASO 11110101

 


CASO 11111100

 

### 11.7.1 Schematici

 

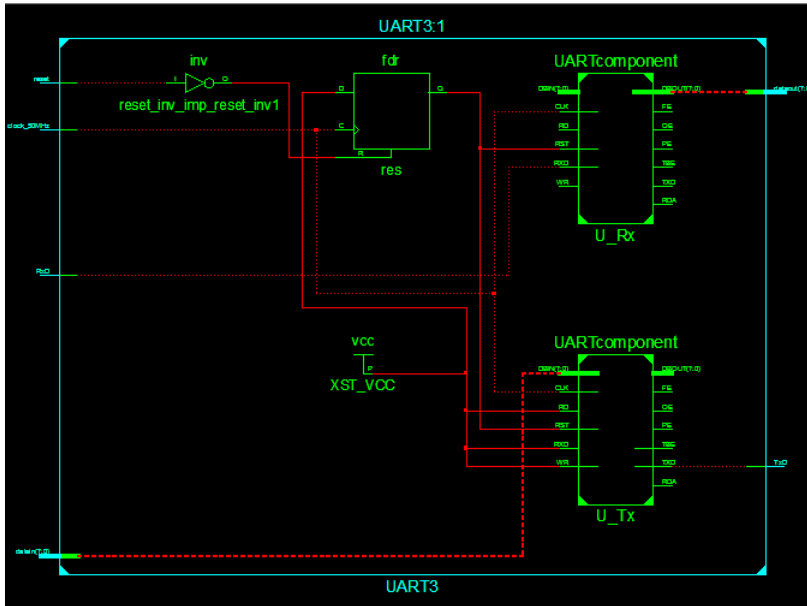

## 11.7.2 Codice

La soluzione viene implementata usando una logica di tipo strutturale. Il componente U\_Tx trasmette il dato al pc e viene letto da Termite. Il componente U\_Rx riceve i dati sulla scheda che vengono visualizzati tramite i led.

### 11.7.2.1 UART\_PC

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4
5 entity UART3 is
6 port (
7     clock_50MHz: in std_logic;
8     reset: in std_logic;
9     TxD: out std_logic;
10    RxD: in std_logic;
11    datain: in std_logic_vector(7 downto 0);
12    dataout: out std_logic_vector(7 downto 0)
13);
14
15 end UART3;
16
17 architecture Behavioral of UART3 is
18
19 Component UARTcomponent is
20 port (
21

```

```

22     TXD    : out    std_logic    := '1';           -- Transmitted serial data
           output
23     RXD    : in     std_logic;           -- Received serial data input
24     CLK    : in     std_logic;           -- Clock signal
25     DBIN   : in     std_logic_vector (7 downto 0); -- Input parallel data
           to be transmitted
26     DBOUT   : out    std_logic_vector (7 downto 0); -- Received parallel
           data output
27     RDA    : inout  std_logic;           -- Read Data Available
28     TBE    : out    std_logic    := '1';           -- Transfer Buffer Empty
29     RD     : in     std_logic;           -- Read Strobe
30     WR     : in     std_logic;           -- Write Strobe
31     PE     : out    std_logic;           -- Parity error
32     FE     : out    std_logic;           -- Frame error
33     OE     : out    std_logic;           -- Overwrite error
34     RST    : in     std_logic := '0'
35
36 );
37 end Component;
38
39 signal t_DBout, t_DBin : std_logic_vector(7 downto 0);
40 signal t,t_rda1,t_tbe1,t_rda2,t_tbe2,t_pe1,t_fe1,t_oe1,t_pe2,t_fe2,t_oe2,
           t_WR2,t_RD2,t_txd2: std_logic:= '0';
41
42
43 begin
44
45
46 U_Tx: UARTcomponent PORT MAP (
47     TXD => TxD,
48     RXD => '1',
49     CLK => clock_50MHz,
50     DBIN => datain,
51     DBOUT => t_DBout,
52     RDA => t_rda1,
53     TBE => t_tbe1,
54     RD => '1',
55     WR => '1',
56     PE => t_pe1,
57     FE => t_fe1,
58     OE => t_oe1,
59     RST => reset
60 );
61
62
63 U_Rx: UARTcomponent PORT MAP (
64     TXD => t_txd2,
65     RXD => RxD,
66     CLK => clock_50MHz,

```



```

67 DBIN => t_DBin,
68 DBOUT => dataout,
69 RDA => t_rda2,
70 TBE => t_tbe2,
71 RD => '0',
72 WR => '0',
73 PE => t_pe2,
74 FE => t_fe2,
75 OE => t_oe2,
76 RST => reset
77 );
78
79
80 end Behavioral;

```

Codice Componente 11.6: Definizione del componente UART<sub>PC</sub>

### 11.7.2.2 File UCF


```

1
2
3 ##Leds
4
5 NET "dataout<0>" LOC = "J14"; # Bank = 1, Pin name = IO_L14N_1/A3/RHCLK7,
   Type = RHCLK/DUAL, Sch name = JD10/LD0
6 NET "dataout<1>" LOC = "J15"; # Bank = 1, Pin name = IO_L14P_1/A4/RHCLK6,
   Type = RHCLK/DUAL, Sch name = JD9/LD1
7 NET "dataout<2>" LOC = "K15"; # Bank = 1, Pin name = IO_L12P_1/A8/RHCLK2,
   Type = RHCLK/DUAL, Sch name = JD8/LD2
8 NET "dataout<3>" LOC = "K14"; # Bank = 1, Pin name = IO_L12N_1/A7/RHCLK3/
   TRDY1, Type = RHCLK/DUAL, Sch name = JD7/LD3
9 NET "dataout<4>" LOC = "E16"; # Bank = 1, Pin name = N.C., Type = N.C., Sch
   name = LD4? other than s3e500
10 NET "dataout<5>" LOC = "P16"; # Bank = 1, Pin name = N.C., Type = N.C., Sch
   name = LD5? other than s3e500
11 NET "dataout<6>" LOC = "E4"; # Bank = 3, Pin name = N.C., Type = N.C., Sch
   name = LD6? other than s3e500
12 NET "dataout<7>" LOC = "P4"; # Bank = 3, Pin name = N.C., Type = N.C., Sch
   name = LD7? other than s3e500
13
14 NET "clock_50MHz" LOC = "B8"; # Bank = 0, Pin name = IP_L13P_0/GCLK8, Type
   = GCLK, Sch name = GCLK0
15
16
17 ##Switch
18 NET "datain<0>" LOC = "G18"; # Sch name = SW0
19 NET "datain<1>" LOC = "H18"; # Sch name = SW1
20 NET "datain<2>" LOC = "K18"; # Sch name = SW2

```

```
21 NET "datain<3>"      LOC = "K17";    # Sch name = SW3
22 NET "datain<4>"      LOC = "L14";    # Sch name = SW4
23 NET "datain<5>"      LOC = "L13";    # Sch name = SW5
24 NET "datain<6>"      LOC = "N17";    # Sch name = SW6
25 NET "datain<7>"      LOC = "R17";    # Sch name = SW7
26
27
28
29 NET "reset" LOC = "B18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name =
    BTN0
30
31
32 ## RS232 connector
33 NET "RxD" LOC = "U6"; # Bank = 2, Pin name = IP, Type = INPUT, Sch name = RS
    -RX
34 NET "TxD" LOC = "P9"; # Bank = 2, Pin name = IO, Type = I/O, Sch name = RS-
    TX
```

 Codice Componente 11.7: Definizione del file UCF



# Capitolo 12

## Esercizio 12


### 12.1 Traccia


A partire dall'implementazione fornita di un processore operante secondo il modello IJVM,

- a) si proceda all'analisi dell'architettura mediante simulazione e si approfondisca lo studio del suo funzionamento per due istruzioni a scelta,
- b) si modifichi un codice operativo a scelta, documentando tutte le modifiche effettuate,
- c) (opzionale) si descriva il funzionamento del processore in merito alle istruzioni di input/output,
- d) (solo ove possibile) si sintetizzi il processore su FPGA.
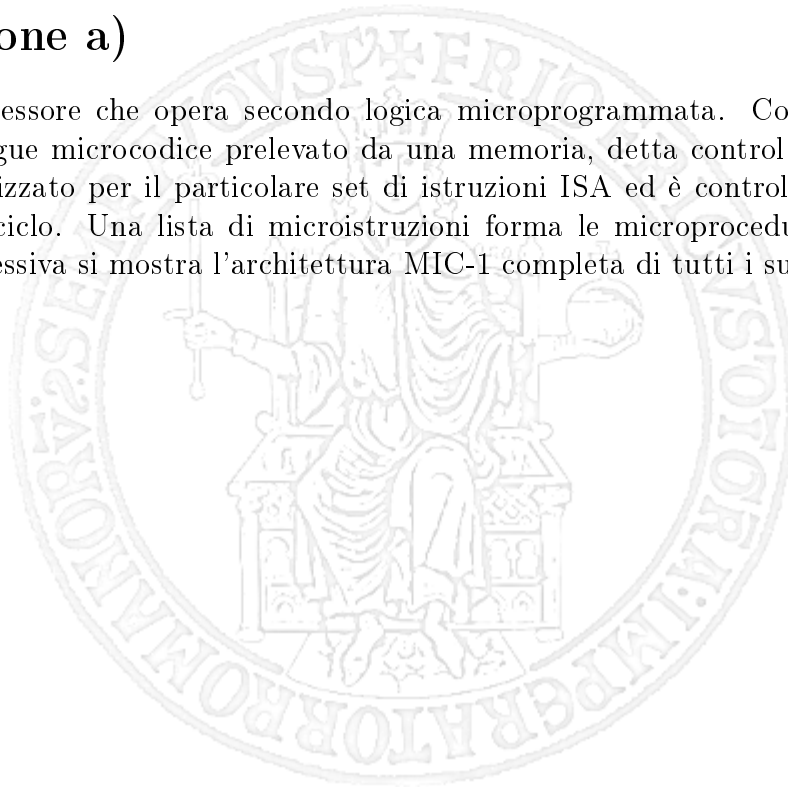
### 12.2 Soluzione a)

Il MIC-1 è un processore che opera secondo logica microprogrammata. Consiste di una unità di controllo che esegue microcodice prelevato da una memoria, detta control store, di 512 word. Il datapath è ottimizzato per il particolare set di istruzioni ISA ed è controllato da una microistruzione per ogni ciclo. Una lista di microistruzioni forma le microprocedure del programma. Nell'immagine successiva si mostra l'architettura MIC-1 completa di tutti i suoi componenti.



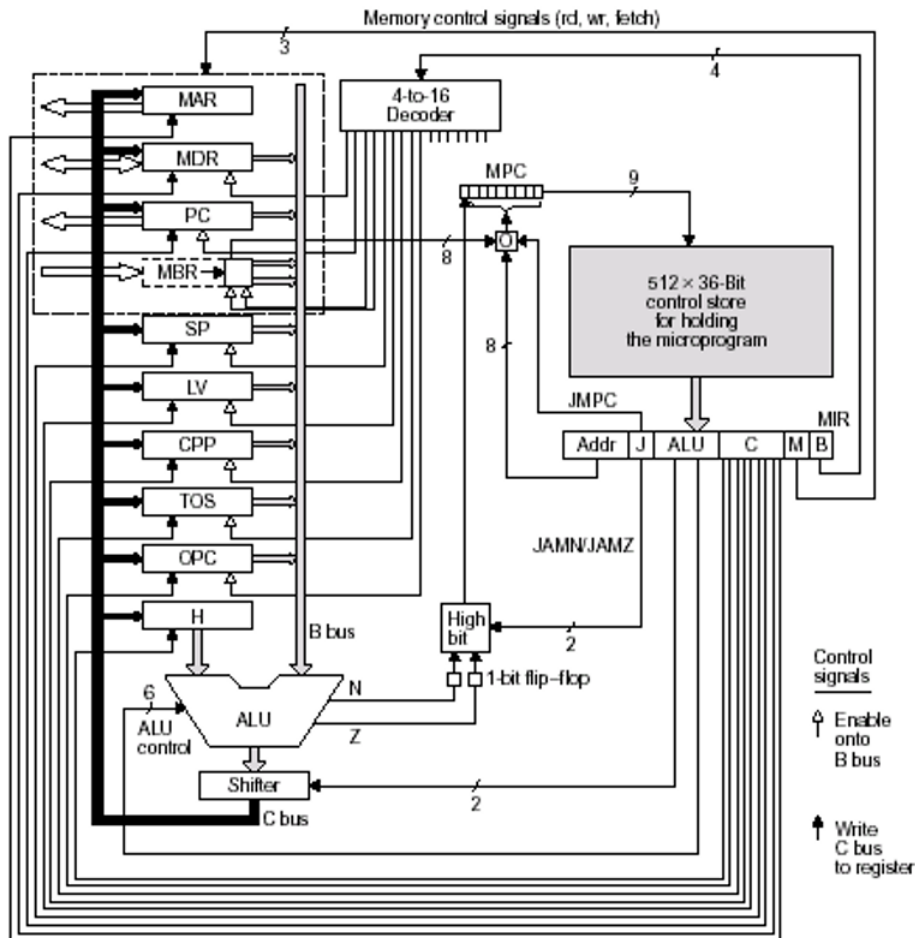

Il datapath contiene registri a 32 bit accessibili solo a livello microarchitetturale e 2 bus, B e C, per lettura e scrittura. L'unità logico aritmetica esegue le operazioni su due operandi : uno contenuto appunto nel registro H e l'altro proveniente dal bus B. Per eseguire una intera istruzione ISA, il control store deve essere in grado di calcolare l'indirizzo della microistruzione successiva da eseguire, che verrà inserita nell' MPC. Quando la ALU termina l'operazione, N e Z vengono salvati e utilizzati per determinare l'istruzione successiva :

1 - Il contenuto dei 9 bit NextAddress viene copiato in MPC

2 - Se JAM = "000", MPC = NextAddress altrimenti viene calcolato MPC;

3 - Se JAMN è settato ad "1" -> il bit più significativo di MPC viene messo in OR con il flag N. Se JAMZ è settato ad "1" -> il bit più significativo di MPC viene messo in OR con il flag Z. Se entrambi sono settati ad "1" -> il bit più significativo di MPC viene messo in OR con entrambi ( $F = (JAMN \text{ AND } N) \text{ OR } (JAMZ \text{ AND } Z) \text{ OR } \text{bitNEXT\_ADDRESS}[8]$ ). Se JAMC è settato ad "1" -> gli 8 bit di MBR sono messi in OR bit a bit con gli 8 bits meno significativi di MIR.

Le istruzioni scelte per la simulazione del processore del MIC1 vengono mostrate nel seguente codice IJVM :

```

1
2 .main
3 .var
4 a

```

```

5 .endvar
6 BIPUSH 0x56
7 ISTORE a
8 .endmethod

```

Codice Componente 12.1: Istruzioni

Il programma fa il push sullo stack del valore esadecimale 0x56, che viene successivamente memorizzato nella variabile “a”.

Per poterlo tradurre in un linguaggio interpretabile dal processore MIC1 si usa il tool fornito su piattaforma Ubuntu lanciando il comando “make create\_ram”, che produce il risultato seguente:

```

1 @128
2 00000000000000000000000000000000
3 @0
4 00000001000000000000000010000000
5 0000000100110110010101011000010000

```


Codice Componente 12.2: Istruzioni

All’indirizzo 128 abbiamo la constant pool e le istruzioni all’indirizzo 0 e 1 (word da 32 bit). I dati vengono letti dal processore da destra verso sinistra a 8 bit alla volta tramite i registri dato e indirizzo.

La RAM viene successivamente caricata con tali valori e viene fatta partire la simulazione.
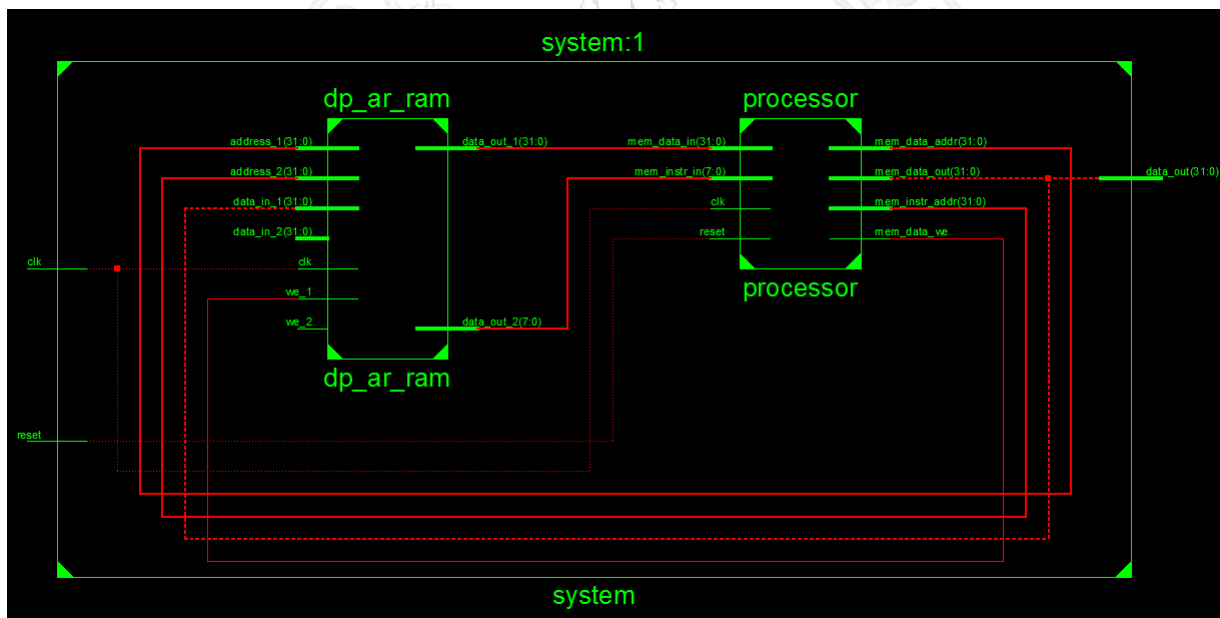
### 12.2.1 Schematici

Si mostra lo schematico relativo ai collegamenti tra RAM e processore MIC1. I due componenti si scambiano dati ed indirizzi permettendo al processore MIC1 di poter elaborare le istruzioni ed eseguirle, fornendo il dato in uscita tramite porta di output data\_out.



### 12.2.2 Codice

Soltanto il file `dp_ar_ram.vhd` è stato modificato e il programma caricato nel blocco contenente le word.

```

1
2
3 library ieee;
4 use ieee.std_logic_1164.all;
5 use ieee.numeric_std.all;
6
7 use work.common_defs.all;
8
9 --! Data memory for amic-0 based systems
10
11 --! Dual port, asynchronous read RAM for amic-0 based systems.
12 entity dp_ar_ram is
13     port (
14         --! Clock
15         clk          : in  std_logic;
16         --! Write enable 1
17         we_1         : in  std_logic;
18         --! Port for memory write 1
19         data_in_1    : in  reg_data_type;
20         --! Port for memory read 1
21         data_out_1   : out reg_data_type;
22         --! Address for memory operations 1
23         address_1    : in  reg_data_type;
24         --! Write enable 2
25         we_2         : in  std_logic;
26         --! Port for memory write 2
27         data_in_2    : in  reg_data_type;
28         --! Port for memory read 2
29         data_out_2   : out mbr_data_type;
30         --! Address for memory operations 2
31         address_2    : in  reg_data_type;
32     );
33 end entity dp_ar_ram;
34
35 --! Dataflow architecture for the control store
36 architecture behavioral of dp_ar_ram is
37
38     -- Signals
39     signal t_address_1 : integer := 0;
40     signal t_address_2 : integer := 0;
41     signal wa_address_2 : reg_data_type;
42     signal t_data_out_2 : reg_data_type;
43
44     -- RAM content
45     signal mem : dp_ar_ram_type := (

```

```

46 --BEGIN_WORDS_ENTRY
47 128 => "00000000000000000000000000000000",
48 0 => "00000001000000000000000010000000",
49 1 => "00000001001101100101011000010000",
50 others => (others => '0')
51 --END_WORDS_ENTRY
52 );
53
54
55
56
57 begin -- architecture behavioral
58
59     wa_address_2 <= "00" & address_2(reg_data_type'high downto 2);
60     t_address_1 <= to_integer(unsigned(address_1));
61     t_address_2 <= to_integer(unsigned(wa_address_2));
62
63     mem_proc : process(clk) is
64     begin
65         if (rising_edge(clk)) then
66             if (we_1 = '1') then
67                 mem(t_address_1) <= data_in_1;
68             elsif (we_2 = '1') then
69                 mem(t_address_2) <= data_in_2;
70             end if;
71         end if;
72     end process;
73
74     data_out_1 <= mem(t_address_1);
75     t_data_out_2 <= mem(t_address_2);
76
77     with address_2(1 downto 0) select data_out_2 <=
78         t_data_out_2(7 downto 0) when "00",
79         t_data_out_2(15 downto 8) when "01",
80         t_data_out_2(23 downto 16) when "10",
81         t_data_out_2(31 downto 24) when "11",
82         (others => '0') when others;
83
84 end architecture behavioral;

```

Codice Componente 12.3: RAM modificata col nuovo programma

## 12.3 Simulazione

Sono stati modificati i valori all'interno del process wavegen\_proc del testbench processor\_tb.

```

1
2 library ieee;

```

```

3 use ieee.std_logic_1164.all;
4
5 use work.common_defs.all;
6
7 --! Empty entity for the testbench
8 entity processor_tb is
9 end entity processor_tb;
10
11 --! Behavioral architecture for the testbench
12 architecture behavioral of processor_tb is
13
14     -- Component ports
15     signal reset          : std_logic;
16     signal mem_data_we    : std_logic;
17     signal mem_data_in    : reg_data_type;
18     signal mem_data_out   : reg_data_type;
19     signal mem_data_addr  : reg_data_type;
20     signal mem_instr_in   : mbr_data_type;
21     signal mem_instr_addr : reg_data_type;
22
23     -- Clock
24     signal clk : std_logic := '1';
25
26     -- Variables
27     shared variable end_run : boolean := false;
28
29 begin -- architecture behavioral
30
31     -- Component instantiation
32     dut : entity work.processor
33         port map (
34             clk          => clk,
35             reset        => reset,
36             mem_data_we  => mem_data_we,
37             mem_data_in  => mem_data_in,
38             mem_data_out => mem_data_out,
39             mem_data_addr => mem_data_addr,
40             mem_instr_in => mem_instr_in,
41             mem_instr_addr => mem_instr_addr);
42
43     dp_ar_ram : entity work.dp_ar_ram
44         port map (
45             clk          => clk,
46             we_1         => mem_data_we,
47             data_in_1    => mem_data_out,
48             data_out_1   => mem_data_in,
49             address_1    => mem_data_addr,
50             we_2         => '0',
51             data_in_2    => (others => '0'),

```




```

52     data_out_2 => mem_instr_in,
53     address_2  => mem_instr_addr);
54
55 -- Clock generation
56 clk_proc : process
57 begin
58     while end_run = false loop
59         clk <= not clk;
60         wait for 5 ns;
61     end loop;
62
63     wait;
64 end process clk_proc;
65
66 -- Waveform generation
67 wavegen_proc: process
68 begin
69     wait until clk = '1';
70     wait for 2 ns;
71
72     reset <= '1';
73     wait for 10 ns;
74     reset <= '0';
75
76     wait until mem_instr_addr = x"00000007" and mem_data_we = '1';
77     assert mem_data_out = x"00000056" report "Bad calculated value" severity
78         failure; -- Se il valore è diverso da 0x56
79
80     end_run := true;
81     wait;
82 end process wavegen_proc;
83
84 end architecture behavioral;

```

Codice Componente 12.4: Simulazione delle due istruzioni IJVM

 Le istruzioni vengono correttamente elaborate e il valore in uscita a `mem_data_out` è la conversione in binario del valore esadecimale 0x56.



## 12.4 Soluzione b) IADD modificata

La prima modifica eseguita nei codici operativi IJVM è stata sulla IADD, che viene modificata in modo che essa funzioni come una sottrazione ISUB. Per far ciò è sufficiente modificare l'ultima istruzione, in modo che la ALU esegua una sottrazione invece che un'addizione tra i due operandi H e Memory Data Register.

```

1
2 iadd = 0x65:
3     MAR = SP = SP - 1; rd
4     H = TOS
5     MDR = TOS = MDR - H; wr; goto main

```

Codice Componente 12.5: Istruzione IADD modificata

Come possiamo notare, l'istruzione IADD adesso si comporta esattamente come una ISUB.

```

1
2 isub = 0x5C:
3     MAR = SP = SP - 1; rd
4     H = TOS
5     MDR = TOS = MDR - H; wr; goto main

```

Codice Componente 12.6: Istruzione ISUB

Si testa il corretto funzionamento della IADD modificata facendo il push sullo stack di due valori esadecimali (entrambi 0x56) e memorizzandoli in due variabili a e b. Successivamente tali variabili vengono caricate e si richiama la nuova IADD che effettuerà la sottrazione tra i due elementi, il cui risultato previsto è 0. Il risultato della sottrazione viene memorizzato poi in b.


```

1 .main
2 .var
3 a
4 b
5 .endvar
6 BIPUSH    0x56
7 ISTORE    a
8 BIPUSH    0x56
9 ISTORE    b
10
11 ILOAD     a
12 ILOAD     b
13 IADD
14 ISTORE    b
15
16 .endmethod

```

Codice Componente 12.7: Programma assembler

### 12.4.1 Schematici

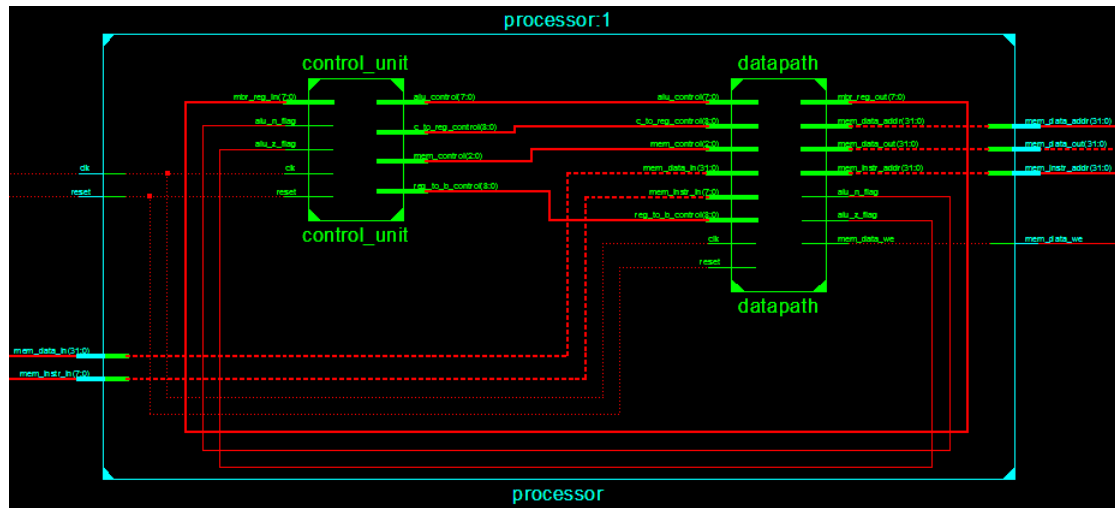

### 12.4.2 Codice

Il componente del MIC-1 Control Store contiene le definizioni di tutte le istruzioni IJVM composte da un codice operativo e in alcuni casi da un operando. Utilizzando i tool forniti e lanciando il comando “make create\_control\_store” tali istruzioni vengono ridefinite aggiungendo la nuova IADD. Il control store nell’implementazione fornita del MIC-1 è composto da 512 word da 32 bit che codificano le 112 istruzioni IJVM. Ne riportiamo una parte:

```

1
2 0 => "0000001100000000000000000000000000001001",
3 1 => "0101111000000000000000000000000000001001",
4 2 => "0000000000000000000000000000000000000000",
5 3 => "0000000000000000000000000000000000000000",
6 4 => "0000000000000000000000000000000000000000",
7 5 => "0000000000000000000000000000000000000000",
8 6 => "000000000100001101010000001000010001",
9 7 => "000001000000001101010000001000000001",
10 8 => "000001001000001101010000001000010001",
11 9 => "0000001100000000000000000000000000001001",
12 10 => "0000000000000000000000000000000000000000",
13 11 => "0000000000000000000000000000000000000000",
14 12 => "0000000000000000000000000000000000000000",
15 13 => "0000000000000000000000000000000000000000",
16 14 => "0000000000000000000000000000000000000000",
17 15 => "0000000000000000000000000000000000000000",
18 16 => "0000100010000011010100000010010000100",
19 17 => "000010010000001101010000001000010001",
20 18 => "000000110000000101000010000101000010",
21 19 => "0000000000000000000000000000000000000000",
22 20 => "0000000000000000000000000000000000000000",
23 21 => "000010110000000101001000000000000101",
24 22 => "000010111000001111000000000010100011",

```

```
25 23 => "000011000000001101010000010010000100",
26 24 => "00001100100000110101000001001010001",
27 25 => "000000110000000101000010000000000000",
28 26 => "000000000000000000000000000000000000",
29 27 => "000000000000000000000000000000000000",
30 28 => "000000000000000000000000000000000000",
31 29 => "000000000000000000000000000000000000",
32 30 => "000000000000000000000000000000000000",
33 31 => "000000000000000000000000000000000000",
34 32 => "000100001000001101010000001000010001",
35 33 => "000100010000100101001000000000000011",
36 33 => "000100010000100101001000000000000011",
37 34 => "000100011000000111001000000000000011",
38 35 => "000010111000001111000000000010100110",
39 36 => "000000000000000000000000000000000000",
40 37 => "000000000000000000000000000000000000",
41 38 => "000000000000000000000000000000000000",
42 39 => "000000000000000000000000000000000000",
43 40 => "000000000000000000000000000000000000",
44 41 => "000000000000000000000000000000000000",
45 42 => "000000000000000000000000000000000000",
46 43 => "000000000000000000000000000000000000",
47 44 => "000000000000000000000000000000000000",
48 45 => "000000000000000000000000000000000000",
49 46 => "000000000000000000000000000000000000",
50 47 => "000000000000000000000000000000000000",
51 48 => "000000000000000000000000000000000000",
52 49 => "000000000000000000000000000000000000",
53 50 => "000000000000000000000000000000000000",
54 51 => "000000000000000000000000000000000000",
55 52 => "000000000000000000000000000000000000",
56 53 => "000000000000000000000000000000000000",
57 54 => "000110111000000101001000000000000101",
58 55 => "000111000000001111000000000010000011",
59 56 => "000111001000000101000000000101000111",
60 57 => "000111010000001101100000010010100100",
61 58 => "000111011000001101010000001000010001",
62 59 => "000000110000000101000010000000000000",
63 60 => "000000000000000000000000000000000000",
64 61 => "000000000000000000000000000000000000",
65 62 => "000000000000000000000000000000000000",
66 63 => "000000000000000000000000000000000000",
67 64 => "000000000000000000000000000000000000",
68 65 => "000000000000000000000000000000000000",
69 66 => "000000000000000000000000000000000000",
70 67 => "000000000000000000000000000000000000",
71 68 => "000000000000000000000000000000000000",
72 69 => "000000000000000000000000000000000000",
73 70 => "000000000000000000000000000000000000",
```

```

74 71 => "00000000000000000000000000000000",
75 72 => "00000000000000000000000000000000",
76 73 => "00000000000000000000000000000000",
77 74 => "00000000000000000000000000000000",
78 75 => "00000000000000000000000000000000",
79 76 => "00000000000000000000000000000000",
80 77 => "00000000000000000000000000000000",
81 78 => "00000000000000000000000000000000",
82 79 => "00000000000000000000000000000000",
83 80 => "00000000000000000000000000000000",
84 81 => "00000000000000000000000000000000",
85 82 => "00000000000000000000000000000000",
86 83 => "00000000000000000000000000000000",
87 84 => "00000000000000000000000000000000",
88 85 => "00000000000000000000000000000000",
89 86 => "00000000000000000000000000000000",
90 87 => "00101100000000110101000001001000100",
91 88 => "00000011000000010100000000101000111",
92 89 => "001011010000001101100000010010100100",
93 90 => "001011011000000000000000000000001001",
94 91 => "000000110000000101000010000000000000",
95 92 => "001011101000001101100000010010100100",
96 93 => "00101111000000010100100000000000111",
97 94 => "000000110000001111110010000101000000",
98 95 => "00110000000000110110000000010100100",
99 96 => "00110000100000010100000000010000100",
100 97 => "001100010000000101001000000001000000",
101 98 => "001100011000000101000000000100000111",
102 99 => "00110010000000110110000000011000100",
103 100 => "000000110000000110000010000000001001",
104 101 => "001100110000001101100000010010100100",
105 102 => "00110011100000010100100000000000111",
106 103 => "000000110000001111110010000101000000",
107 104 => "0000000000000000000000000000000000",
108 105 => "0000000000000000000000000000000000",
109 106 => "0000000000000000000000000000000000",
110 107 => "0000000000000000000000000000000000",
111 108 => "0000000000000000000000000000000000",
112 109 => "0000000000000000000000000000000000",
113 110 => "0000000000000000000000000000000000",
114 111 => "0000000000000000000000000000000000",
115 112 => "0000000000000000000000000000000000",
116 113 => "0000000000000000000000000000000000",
117 114 => "0000000000000000000000000000000000",
118 115 => "0000000000000000000000000000000000",
119 116 => "0000000000000000000000000000000000",
120 117 => "0000000000000000000000000000000000",
121 118 => "0000000000000000000000000000000000",
122 119 => "0000000000000000000000000000000000",

```

```

123 120 => "00000000000000000000000000000000",
124 121 => "00000000000000000000000000000000",
125 122 => "00000000000000000000000000000000",
126 123 => "00000000000000000000000000000000",
127 124 => "00000000000000000000000000000000",
128 125 => "00000000000000000000000000000000",
129 126 => "00111111100000110110000010010100100",
130 127 => "01000000000000010100100000000000111",
131 128 => "000000110000000011000010000101000000",
132 129 => "0000000000000000000000000000000000",
133 130 => "0000000000000000000000000000000000",
134 131 => "0000000000000000000000000000000000",
135 132 => "01000010100000010100100000000000101",
136 133 => "01000011000000111100000000010100011",
137 134 => "010000111000001101010000001000010001",
138 135 => "01000100000000010100100000000000000",
139 136 => "010001001000001101010000001000010001",
140 137 => "00000011000000111100000000101000010",
141 138 => "0000000000000000000000000000000000",
142 139 => "0000000000000000000000000000000000",
143 140 => "0000000000000000000000000000000000",
144 141 => "0000000000000000000000000000000000",
145 142 => "0000000000000000000000000000000000",
146 143 => "0000000000000000000000000000000000",
147 144 => "0000000000000000000000000000000000",
148 145 => "0000000000000000000000000000000000",
149 146 => "0000000000000000000000000000000000",
150 147 => "0000000000000000000000000000000000",
151 148 => "0000000000000000000000000000000000",
152 149 => "0000000000000000000000000000000000",
153 150 => "0000000000000000000000000000000000",
154
155 ...

```

Codice Componente 12.8: Nuovo Controllore

Il programma infine è stato tradotto e caricato in RAM come visto nel paragrafo precedente.

```

1
2
3 library ieee;
4 use ieee.std_logic_1164.all;
5 use ieee.numeric_std.all;
6
7 use work.common_defs.all;
8
9 --! Data memory for amic-0 based systems
10
11 --! Dual port, asynchronous read RAM for amic-0 based systems.
12 entity dp_ar_ram is

```

```

13  port (
14      --! Clock
15      clk          : in  std_logic;
16      --! Write enable 1
17      we_1         : in  std_logic;
18      --! Port for memory write 1
19      data_in_1    : in  reg_data_type;
20      --! Port for memory read 1
21      data_out_1   : out reg_data_type;
22      --! Address for memory operations 1
23      address_1    : in  reg_data_type;
24      --! Write enable 2
25      we_2         : in  std_logic;
26      --! Port for memory write 2
27      data_in_2    : in  reg_data_type;
28      --! Port for memory read 2
29      data_out_2   : out mbr_data_type;
30      --! Address for memory operations 2
31      address_2    : in  reg_data_type;
32  );
33  end entity dp_ar_ram;
34
35  --! Dataflow architecture for the control store
36  architecture behavioral of dp_ar_ram is
37
38      -- Signals
39      signal t_address_1 : integer := 0;
40      signal t_address_2 : integer := 0;
41      signal wa_address_2 : reg_data_type;
42      signal t_data_out_2 : reg_data_type;
43
44      -- RAM content
45      signal mem : dp_ar_ram_type := (
46  --BEGIN_WORDS_ENTRY
47
48  128 => "00000000000000000000000000000000",
49  0  => "0000001000000000000000000100000000",
50  1  => "00000001001101100101011000010000",
51  2  => "00000010001101100101011000010000",
52  3  => "00000010000101010000000100010101",
53  4  => "000000000000000100011011001100101",
54
55  others => (others => '0')
56  --END_WORDS_ENTRY
57  );
58
59
60
61  begin  -- architecture behavioral

```

```


62
63 wa_address_2 <= "00" & address_2(reg_data_type'high downto 2);
64 t_address_1 <= to_integer(unsigned(address_1));
65 t_address_2 <= to_integer(unsigned(wa_address_2));
66
67 mem_proc : process(clk) is
68 begin
69     if (rising_edge(clk)) then
70         if (we_1 = '1') then
71             mem(t_address_1) <= data_in_1;
72         elsif (we_2 = '1') then
73             mem(t_address_2) <= data_in_2;
74         end if;
75     end if;
76 end process;
77
78 data_out_1 <= mem(t_address_1);
79 t_data_out_2 <= mem(t_address_2);
80
81 with address_2(1 downto 0) select data_out_2 <=
82     t_data_out_2(7 downto 0)    when "00",
83     t_data_out_2(15 downto 8)   when "01",
84     t_data_out_2(23 downto 16)  when "10",
85     t_data_out_2(31 downto 24)  when "11",
86     (others => '0')            when others;
87
88 end architecture behavioral;

```

Codice Componente 12.9: *dp<sub>ar</sub>ram.vhd*
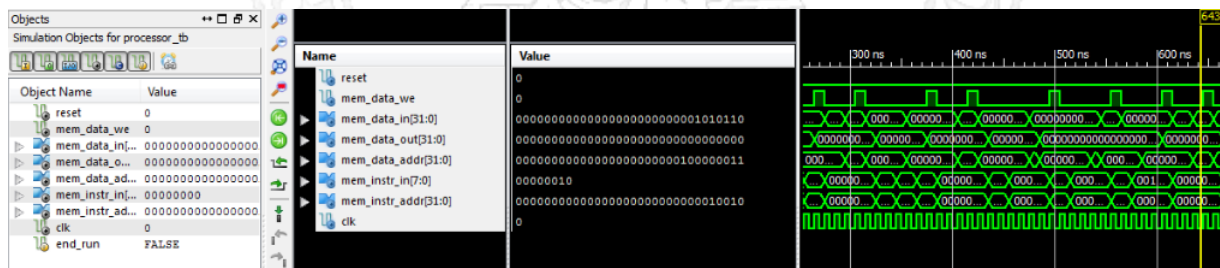
## 12.5 Simulazione

Il testbench utilizzato è *processor\_tb*, che simula il comportamento del processore e della RAM. Esso è del tutto simile a quello del paragrafo precedente e per questo non viene mostrato. E' sufficiente osservare direttamente il comportamento delle forme d'onda, una volta lanciata la simulazione con ISim.



Dopo aver eseguito tutte le istruzioni IJVM del programma, il dato in uscita da *mem\_data\_out* è 0, come atteso.



## 12.6 Soluzione b) ISUB modificata

La ISUB è stata modificata in questo modo : i due operandi vengono immessi nello stack e viene effettuata la sottrazione, tuttavia essi non vengono rimossi e il risultato finale dell'operazione viene posto in cima allo stack. Per far ciò si è incrementato il puntatore SP di 1 subito dopo aver messo il contenuto di SP-1 in MAR per la lettura dell'operando.

Poichè le istruzioni IJVM sono memorizzate in una porzione di memoria limitata bisogna modificare gli indirizzi di partenza. Lanciare il comando senza effettuare le modifiche agli indirizzi porterà ad un errore di “Invalid control store region”. Nel nostro caso l'istruzione IJVM immediatamente successiva alla ISUB è la swap, che è stata rimossa .

```

1
2 isub = 0x5C:
3     MAR = SP - 1; rd
4     MAR = SP = SP + 1
5     H = TOS
6     MDR = TOS = MDR - H; wr; goto main

```

Codice Componente 12.10: Istruzione ISUB modificata

Si effettua il push sullo stack dei valori esadecimali 0x56 e 0x55. La sottrazione tra essi darà come risultato 1. I valori vengono inseriti nello stack e vengono memorizzati in a e b. La ISUB modificata fa in modo tale da non rimuoverli dallo stack e posizionare il risultato in cima.

```

1 .main
2 .var
3 a
4 b
5 .endvar
6
7 BIPUSH    0x56
8 ISTORE    a
9 BIPUSH    0x55
10 ISTORE    b
11
12 ILOAD     a
13 ILOAD     b
14 ISUB
15
16 .endmethod

```

Codice Componente 12.11: Programma assembler

### 12.6.1 Codice

Come nel precedente esempio sono state ricreate le word del Control Store e il file control\_store.vhd è stato modificato.

```

1
2 library ieee;

```

```

3   use ieee.std_logic_1164.all;
4   use ieee.numeric_std.all;
5
6   use work.common_defs.all;
7
8   --! Processor control store
9
10  --! The control store is a ROM used to store the processor microprogram.
11  entity control_store is
12    port (
13      --! Address of the desired word
14      address : in  ctrl_str_addr_type;
15      --! Content of the addressed word
16      word    : out ctrl_str_word_type
17    );
18  end entity control_store;
19
20  --! Dataflow architecture for the control store
21  architecture dataflow of control_store is
22
23    -- Constants
24    constant words : ctrl_str_type := (
25      --BEGIN_WORDS_ENTRY0 => "0000001100000000000000000000000001001",
26
27
28      0 => "0000010010000000000000000000000000001001",
29      1 => "01011110000000000000000000000000000001001",
30      2 => "0000000000000000000000000000000000000000",
31      3 => "0000000000000000000000000000000000000000",
32      4 => "0000000000000000000000000000000000000000",
33      5 => "0000000000000000000000000000000000000000",
34      6 => "0000001110000011010100000010000000001",
35      7 => "000001000000001101010000001000010001",
36      8 => "000001001000000000000000000000000001001",
37      9 => "000000000100001101010000001000010001",
38      10 => "00000000000000000000000000000000000000",
39      11 => "00000000000000000000000000000000000000",
40      12 => "00000000000000000000000000000000000000",
41      13 => "00000000000000000000000000000000000000",
42      14 => "00000000000000000000000000000000000000",
43      15 => "00000000000000000000000000000000000000",
44      16 => "000010001000001101010000010010000100",
45      17 => "000010010000001101010000001000010001",
46      18 => "000001001000000101000010000101000010",
47      19 => "00000000000000000000000000000000000000",
48      20 => "00000000000000000000000000000000000000",
49      21 => "000010110000000101001000000000000101",
50      22 => "000010111000001111000000000010100011",
51      23 => "000011000000001101010000010010000100",

```

```

52 24 => "000011001000001101010000001001010001",
53 25 => "000001001000000101000010000000000000",
54 26 => "000000000000000000000000000000000000",
55 27 => "000000000000000000000000000000000000",
56 28 => "000000000000000000000000000000000000",
57 29 => "000000000000000000000000000000000000",
58 30 => "000000000000000000000000000000000000",
59 31 => "000000000000000000000000000000000000",
60 32 => "000100001000001101010000001000010001",
61 33 => "000100010000100101001000000000000011",
62 34 => "000100011000000111001000000000000011",
63 35 => "000010111000001111000000000010100110",
64 36 => "000000000000000000000000000000000000",
65 37 => "000000000000000000000000000000000000",
66 38 => "000000000000000000000000000000000000",
67 39 => "000000000000000000000000000000000000",
68 40 => "000000000000000000000000000000000000",
69 41 => "000000000000000000000000000000000000",
70 42 => "000000000000000000000000000000000000",
71 43 => "000000000000000000000000000000000000",
72 44 => "000000000000000000000000000000000000",
73 45 => "000000000000000000000000000000000000",
74 46 => "000000000000000000000000000000000000",
75 47 => "000000000000000000000000000000000000",
76 48 => "000000000000000000000000000000000000",
77 49 => "000000000000000000000000000000000000",
78 50 => "000000000000000000000000000000000000",
79 51 => "000000000000000000000000000000000000",
80 52 => "000000000000000000000000000000000000",
81 53 => "000000000000000000000000000000000000",
82 54 => "000110111000000101001000000000000101",
83 55 => "000111000000001111000000000010000011",
84 56 => "00011100100000010100000000101000111",
85 57 => "000111010000001101100000010010100100",
86 58 => "0001110110000001101010000001000010001",
87 59 => "000001001000000101000010000000000000",
88 60 => "000000000000000000000000000000000000",
89 61 => "000000000000000000000000000000000000",
90 62 => "000000000000000000000000000000000000",
91 63 => "000000000000000000000000000000000000",
92 64 => "000000000000000000000000000000000000",
93 65 => "000000000000000000000000000000000000",
94 66 => "000000000000000000000000000000000000",
95 67 => "000000000000000000000000000000000000",
96 68 => "000000000000000000000000000000000000",
97 69 => "000000000000000000000000000000000000",
98 70 => "000000000000000000000000000000000000",
99 71 => "000000000000000000000000000000000000",
100 72 => "000000000000000000000000000000000000",

```

```
101 73 => "00000000000000000000000000000000",
102 74 => "00000000000000000000000000000000",
103 75 => "00000000000000000000000000000000",
104 76 => "00000000000000000000000000000000",
105 77 => "00000000000000000000000000000000",
106 78 => "00000000000000000000000000000000",
107 79 => "00000000000000000000000000000000",
108 80 => "00000000000000000000000000000000",
109 81 => "00000000000000000000000000000000",
110 82 => "00000000000000000000000000000000",
111 83 => "00000000000000000000000000000000",
112 84 => "00000000000000000000000000000000",
113 85 => "00000000000000000000000000000000",
114 86 => "00000000000000000000000000000000",
115 87 => "00101100000000110101000001001000100",
116 88 => "000001001000000101000000000101000111",
117 89 => "001011010000001101100000010010100100",
118 90 => "00101101100000000000000000000001001",
119 91 => "000001001000000101000010000000000000",
120 92 => "001011101000001101100000000010100100",
121 93 => "00101111000000110101000001001000100",
122 94 => "00101111100000010100100000000000111",
123 95 => "000001001000001111110010000101000000",
124 96 => "0000000000000000000000000000000000",
125 97 => "0000000000000000000000000000000000",
126 98 => "0000000000000000000000000000000000",
127 99 => "0000000000000000000000000000000000",
128 100 => "0000000000000000000000000000000000",
129 101 => "001100110000001101100000010010100100",
130 102 => "00110011100000010100100000000000111",
131 103 => "000001001000001111000010000101000000",
132 104 => "0000000000000000000000000000000000",
133 105 => "0000000000000000000000000000000000",
134 106 => "0000000000000000000000000000000000",
135 107 => "0000000000000000000000000000000000",
136 108 => "0000000000000000000000000000000000",
137 109 => "0000000000000000000000000000000000",
138 110 => "0000000000000000000000000000000000",
139 111 => "0000000000000000000000000000000000",
140 112 => "0000000000000000000000000000000000",
141 113 => "0000000000000000000000000000000000",
142 114 => "0000000000000000000000000000000000",
143 115 => "0000000000000000000000000000000000",
144 116 => "0000000000000000000000000000000000",
145 117 => "0000000000000000000000000000000000",
146 118 => "0000000000000000000000000000000000",
147 119 => "0000000000000000000000000000000000",
148 120 => "0000000000000000000000000000000000",
149 121 => "0000000000000000000000000000000000",
```

```

150 122 => "00000000000000000000000000000000",
151 123 => "00000000000000000000000000000000",
152 124 => "00000000000000000000000000000000",
153 125 => "00000000000000000000000000000000",
154 126 => "001111111000001101100000010010100100",
155 127 => "01000000000000010100100000000000111",
156 128 => "000001001000000011000010000101000000",
157 129 => "00000000000000000000000000000000",
158 130 => "00000000000000000000000000000000",
159 131 => "00000000000000000000000000000000",
160 132 => "010000101000000101001000000000000101",
161 133 => "010000110000001111000000000010100011",
162 134 => "010000111000001101010000001000010001",
163 135 => "010001000000000101001000000000000000",
164 136 => "010001001000001101010000001000010001",
165 137 => "000001001000001111000000000101000010",
166 138 => "00000000000000000000000000000000",
167 139 => "00000000000000000000000000000000",
168 140 => "00000000000000000000000000000000",
169 141 => "00000000000000000000000000000000",
170 142 => "00000000000000000000000000000000",
171 143 => "00000000000000000000000000000000",
172 144 => "00000000000000000000000000000000",
173 145 => "00000000000000000000000000000000",
174 146 => "00000000000000000000000000000000",
175 147 => "00000000000000000000000000000000",
176 148 => "00000000000000000000000000000000",
177 149 => "00000000000000000000000000000000",
178 150 => "00000000000000000000000000000000",
179 151 => "00000000000000000000000000000000",
180 152 => "00000000000000000000000000000000",
181 153 => "010011010000001101100000010010100100",
182 154 => "010011011000000101000100000000000111",
183 155 => "010011100000000101000010000000000000",
184 156 => "0000001100010000101000000000000001000",
185 157 => "010011110000001101100000010010100100",
186 158 => "010011111000000101000100000000000111",
187 159 => "010100000000000101000010000000000000",
188 160 => "0000001100100001010000000000000001000",
189 161 => "010100010000001101100000010010100100",
190 162 => "010100011000001101100000010010000100",
191 163 => "0101001000000001010010000000000100000",
192 164 => "010100101000000101000100000000000111",
193 165 => "010100110000000101000010000000000000",
194 166 => "0000001100010011111100000000000001000",
195 167 => "010101000000001101100100000000000001",
196 168 => "010101001000001101010000001000010001",
197 169 => "010101010000100101001000000000000010",
198 170 => "010101011000000111001000000000000011",

```

```
199 171 => "010101100000001111000000001000011000",
200 172 => "000001001000000000000000000000000001001",
201 173 => "010101110000000101000000010010100101",
202 174 => "0101011110000000000000000000000000001001",
203 175 => "0101100000000000101000000100010100000",
204 176 => "010110001000001101010000000010000101",
205 177 => "010110010000000101000000001000110000",
206 178 => "010110011000000101000000000010000100",
207 179 => "010110100000000101000000100000000000",
208 180 => "010110101000000101000000000101000111",
209 181 => "000001001001001101100000000000000001",
210 182 => "010110111000001101100000010010100100",
211 183 => "0101110000000001010010000000000000111",
212 184 => "00000100100000011100001000010100000",
213 185 => "010111010000001101010000001000010001",
214 186 => "010111011000100101001000000000000011",
215 187 => "010111100000000111001000000000000011",
216 188 => "010111101000001111000000000010100110",
217 189 => "010111110000001101010100000000000001",
218 190 => "010111111000000101000000001000010000",
219 191 => "0110000000000001101010000001000010001",
220 192 => "011000001000100101001000000000000011",
221 193 => "011000010000000111001000000000000011",
222 194 => "011000011000001101010000001000010001",
223 195 => "011000100000001111110010000000000100",
224 196 => "011000101000001101010010000010000111",
225 197 => "011000110000001101010000001000010001",
226 198 => "011000111000100101001000000000000011",
227 199 => "011001000000000111001000000000000011",
228 200 => "011001001000001111010000000101000100",
229 201 => "01100101000000010100000001001000000",
230 202 => "011001011000000101000000000101001000",
231 203 => "011001100000001101010000010010000100",
232 204 => "011001101000000101000000000101000101",
233 205 => "011001110000001101010000001000010001",
234 206 => "000001001000000101000000100000000111",
235 207 => "100000000100001101010000001000010001",
236 208 => "00000000000000000000000000000000000",
237 209 => "00000000000000000000000000000000000",
238 210 => "00000000000000000000000000000000000",
239 211 => "00000000000000000000000000000000000",
240 212 => "00000000000000000000000000000000000",
241 213 => "00000000000000000000000000000000000",
242 214 => "00000000000000000000000000000000000",
243 215 => "00000000000000000000000000000000000",
244 216 => "00000000000000000000000000000000000",
245 217 => "00000000000000000000000000000000000",
246 218 => "00000000000000000000000000000000000",
247 219 => "00000000000000000000000000000000000",
```

```
248 220 => "00000000000000000000000000000000",
249 221 => "00000000000000000000000000000000",
250 222 => "00000000000000000000000000000000",
251 223 => "00000000000000000000000000000000",
252 224 => "00000000000000000000000000000000",
253 225 => "00000000000000000000000000000000",
254 226 => "00000000000000000000000000000000",
255 227 => "00000000000000000000000000000000",
256 228 => "00000000000000000000000000000000",
257 229 => "00000000000000000000000000000000",
258 230 => "00000000000000000000000000000000",
259 231 => "00000000000000000000000000000000",
260 232 => "00000000000000000000000000000000",
261 233 => "00000000000000000000000000000000",
262 234 => "00000000000000000000000000000000",
263 235 => "00000000000000000000000000000000",
264 236 => "00000000000000000000000000000000",
265 237 => "00000000000000000000000000000000",
266 238 => "00000000000000000000000000000000",
267 239 => "00000000000000000000000000000000",
268 240 => "00000000000000000000000000000000",
269 241 => "00000000000000000000000000000000",
270 242 => "00000000000000000000000000000000",
271 243 => "00000000000000000000000000000000",
272 244 => "00000000000000000000000000000000",
273 245 => "00000000000000000000000000000000",
274 246 => "00000000000000000000000000000000",
275 247 => "00000000000000000000000000000000",
276 248 => "00000000000000000000000000000000",
277 249 => "00000000000000000000000000000000",
278 250 => "00000000000000000000000000000000",
279 251 => "00000000000000000000000000000000",
280 252 => "00000000000000000000000000000000",
281 253 => "00000000000000000000000000000000",
282 254 => "00000000000000000000000000000000",
283 255 => "00000000000000000000000000000000",
284 256 => "00000000000000000000000000000000",
285 257 => "00000000000000000000000000000000",
286 258 => "00000000000000000000000000000000",
287 259 => "00000000000000000000000000000000",
288 260 => "00000000000000000000000000000000",
289 261 => "00000000000000000000000000000000",
290 262 => "01010100000000110110010000000010001",
291 263 => "00000000000000000000000000000000",
292 264 => "00000000000000000000000000000000",
293 265 => "10000100100000000000000000000001001",
294 266 => "00000000000000000000000000000000",
295 267 => "00000000000000000000000000000000",
296 268 => "00000000000000000000000000000000",
```



```
297 269 => "00000000000000000000000000000000",
298 270 => "00000000000000000000000000000000",
299 271 => "00000000000000000000000000000000",
300 272 => "00000000000000000000000000000000",
301 273 => "00000000000000000000000000000000",
302 274 => "00000000000000000000000000000000",
303 275 => "00000000000000000000000000000000",
304 276 => "00000000000000000000000000000000",
305 277 => "100010110000001101010000001000010001",
306 278 => "10001011100010010100100000000000011",
307 279 => "10001100000000011100100000000000011",
308 280 => "000010111000001111000000000010100101",
309 281 => "00000000000000000000000000000000",
310 282 => "00000000000000000000000000000000",
311 283 => "00000000000000000000000000000000",
312 284 => "00000000000000000000000000000000",
313 285 => "00000000000000000000000000000000",
314 286 => "00000000000000000000000000000000",
315 287 => "00000000000000000000000000000000",
316 288 => "00000000000000000000000000000000",
317 289 => "00000000000000000000000000000000",
318 290 => "00000000000000000000000000000000",
319 291 => "00000000000000000000000000000000",
320 292 => "00000000000000000000000000000000",
321 293 => "00000000000000000000000000000000",
322 294 => "00000000000000000000000000000000",
323 295 => "00000000000000000000000000000000",
324 296 => "00000000000000000000000000000000",
325 297 => "00000000000000000000000000000000",
326 298 => "00000000000000000000000000000000",
327 299 => "00000000000000000000000000000000",
328 300 => "00000000000000000000000000000000",
329 301 => "00000000000000000000000000000000",
330 302 => "00000000000000000000000000000000",
331 303 => "00000000000000000000000000000000",
332 304 => "00000000000000000000000000000000",
333 305 => "00000000000000000000000000000000",
334 306 => "00000000000000000000000000000000",
335 307 => "00000000000000000000000000000000",
336 308 => "00000000000000000000000000000000",
337 309 => "00000000000000000000000000000000",
338 310 => "100110111000001101010000001000010001",
339 311 => "10011100000010010100100000000000011",
340 312 => "10011100100000011100100000000000011",
341 313 => "00011100000000111100000000010000101",
342 314 => "00000000000000000000000000000000",
343 315 => "00000000000000000000000000000000",
344 316 => "00000000000000000000000000000000",
345 317 => "00000000000000000000000000000000",
```



```

346 318 => "00000000000000000000000000000000",
347 319 => "00000000000000000000000000000000",
348 320 => "00000000000000000000000000000000",
349
350 ...
351
352 others => (others => '0')
353 --END_WORDS_ENTRY
354 );
355
356 begin -- architecture dataflow
357
358     word <= words(to_integer(unsigned(address)));
359
360 end architecture dataflow;

```

Codice Componente 12.12: Nuovo Controlstore

Il programma infine è stato tradotto e caricato in RAM come visto nel paragrafo precedente.

```

1
2 library ieee;
3 use ieee.std_logic_1164.all;
4 use ieee.numeric_std.all;
5
6 use work.common_defs.all;
7
8 --! Data memory for amic-0 based systems
9
10 --! Dual port, asynchronous read RAM for amic-0 based systems.
11 entity dp_ar_ram is
12     port (
13         --! Clock
14         clk          : in  std_logic;
15         --! Write enable 1
16         we_1         : in  std_logic;
17         --! Port for memory write 1
18         data_in_1    : in  reg_data_type;
19         --! Port for memory read 1
20         data_out_1   : out reg_data_type;
21         --! Address for memory operations 1
22         address_1    : in  reg_data_type;
23         --! Write enable 2
24         we_2         : in  std_logic;
25         --! Port for memory write 2
26         data_in_2    : in  reg_data_type;
27         --! Port for memory read 2
28         data_out_2   : out mbr_data_type;
29         --! Address for memory operations 2
30         address_2    : in  reg_data_type

```

```

31     );
32 end entity dp_ar_ram;
33
34 --! Dataflow architecture for the control store
35 architecture behavioral of dp_ar_ram is
36
37     -- Signals
38     signal t_address_1  : integer := 0;
39     signal t_address_2  : integer := 0;
40     signal wa_address_2 : reg_data_type;
41     signal t_data_out_2 : reg_data_type;
42
43     -- RAM content
44     signal mem : dp_ar_ram_type := (
45 --BEGIN_WORDS_ENTRY
46
47 128 => "00000000000000000000000000000000",
48 0 => "00000010000000000000000010000000",
49 1 => "00000001001101100101011000010000",
50 2 => "00000010001101100101010100010000",
51 3 => "00000010000101010000000100010101",
52 4 => "0000000000000000000000001011100",
53
54 others => (others => '0')
55 --END_WORDS_ENTRY
56     );
57
58 begin -- architecture behavioral
59
60     wa_address_2 <= "00" & address_2(reg_data_type'high downto 2);
61     t_address_1 <= to_integer(unsigned(address_1));
62     t_address_2 <= to_integer(unsigned(wa_address_2));
63
64     mem_proc : process(clk) is
65     begin
66         if (rising_edge(clk)) then
67             if (we_1 = '1') then
68                 mem(t_address_1) <= data_in_1;
69             elsif (we_2 = '1') then
70                 mem(t_address_2) <= data_in_2;
71             end if;
72         end if;
73     end process;
74
75     data_out_1 <= mem(t_address_1);
76     t_data_out_2 <= mem(t_address_2);
77
78     with address_2(1 downto 0) select data_out_2 <=
79         t_data_out_2(7 downto 0)   when "00",

```

```

80     t_data_out_2(15 downto 8)  when "01",
81     t_data_out_2(23 downto 16) when "10",
82     t_data_out_2(31 downto 24) when "11",
83     (others => '0')           when others;
84
85 end architecture behavioral;

```

Codice Componente 12.13: Istruzioni

## 12.7 Simulazione

Il testbench utilizzato è `processor_tb`, simile al precedente, resetta il processore che elabora il programma caricato nella memoria RAM.

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  use work.common_defs.all;
5
6  --! Empty entity for the testbench
7  entity processor_tb is
8  end entity processor_tb;
9
10 --! Behavioral architecture for the testbench
11 architecture behavioral of processor_tb is
12
13     -- Component ports
14     signal reset          : std_logic;
15     signal mem_data_we    : std_logic;
16     signal mem_data_in    : reg_data_type;
17     signal mem_data_out   : reg_data_type;
18     signal mem_data_addr  : reg_data_type;
19     signal mem_instr_in   : mbr_data_type;
20     signal mem_instr_addr : reg_data_type;
21
22     -- Clock
23     signal clk : std_logic := '1';
24
25     -- Variables
26     shared variable end_run : boolean := false;
27
28 begin -- architecture behavioral
29
30     -- Component instantiation
31     dut : entity work.processor
32         port map (
33         clk          => clk,
34         reset        => reset,

```

```

35     mem_data_we      => mem_data_we,
36     mem_data_in      => mem_data_in,
37     mem_data_out     => mem_data_out,
38     mem_data_addr    => mem_data_addr,
39     mem_instr_in     => mem_instr_in,
40     mem_instr_addr   => mem_instr_addr);
41
42 dp_ar_ram : entity work.dp_ar_ram
43     port map (
44         clk          => clk,
45         we_1         => mem_data_we,
46         data_in_1    => mem_data_out,
47         data_out_1   => mem_data_in,
48         address_1    => mem_data_addr,
49         we_2         => '0',
50         data_in_2    => (others => '0'),
51         data_out_2   => mem_instr_in,
52         address_2    => mem_instr_addr);
53
54 -- Clock generation
55 clk_proc : process
56 begin
57     while end_run = false loop
58         clk <= not clk;
59         wait for 5 ns;
60     end loop;
61
62     wait;
63 end process clk_proc;
64
65 -- Waveform generation
66 wavegen_proc: process
67 begin
68     wait until clk = '1';
69     wait for 2 ns;
70
71     reset <= '1';
72     wait for 10 ns;
73     reset <= '0';
74
75     wait;
76 end process wavegen_proc;
77
78 end architecture behavioral;

```

Codice Componente 12.14: Simulazione delle due istruzioni IJVM

Alla fine dell'elaborazione il processore fornisce in output (mem\_data\_out) il valore di sottrazione di 0x56 e 0x55, cioè 1.

Name	Value	1500 ns	1600 ns	1700 ns	1800 ns	1900 ns
reset	0					
mem_data_we	0					
mem_data_in[31:0]	000000000000000000000000000000000001					
mem_data_out[31:0]	000000000000000000000000000000000001					
mem_data_addr[31:0]	00000000000000000000000000000000000100001000					
mem_instr_in[7:0]	00000000					
mem_instr_addr[31:0]	00000000000000000000000000000000000100100					
clk	0					

# Capitolo 13


## Esercizio 13

### 13.1 Traccia

Progettare ed implementare in VHDL uno switch multistadio secondo il modello omega network, descritto nelle dispense fornite nella cartella “SWITCH”. Lo switch progettato deve consentire lo scambio di messaggi di 2 bit ciascuno fra 4 nodi diversi, tra i quali deve essere realizzato un handshaking semplice regolato da una coppia di segnali (pronto a inviare/pronto a ricevere). L'indirizzo del nodo destinazione, espresso su 2 bit, viene inviato insieme ai 2 bit di informazione per consentire l'avanzamento dei messaggi. Qualora fosse necessario gestire possibili conflitti, il sistema può operare perdendo uno dei messaggi in conflitto (sistema con perdita).

 
### 13.2 Soluzione

In un'architettura multicomputer la logica a n-stadi viene progettata utilizzando degli switch a due ingressi e due uscite in grado di deviare il traffico proveniente da una sorgente verso una destinazione. L'immagine sottostante mostra un esempio di nodi collegati gli uni agli altri attraverso 12 switch differenti.




Nel nostro caso avremo 4 nodi codificati con 00, 01, 10, 11. Ognuno di essi può essere sorgente o destinazione di un messaggio di 2 bit che viene inviato attraverso la rete di switch. Si è scelto

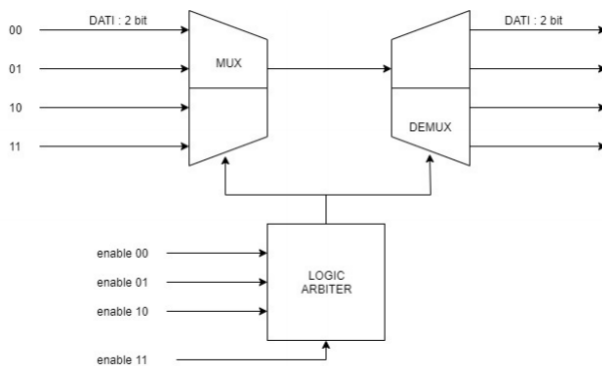
di utilizzare una rete a 4 switch (profondità 2) per la rete da implementare. Il progetto presenta una parte di controllo (PC) e una parte operativa (PO)



La parte di controllo in figura è composta da un multiplexer e un demultiplexer regolati da un logic arbiter, che ha il compito di stabilire la priorità tra i vari nodi. In tal modo all'interno della rete passerà sempre un solo dato alla volta e viene evitato alcun tipo di collisione tra i pacchetti di 2 bit inviati. Il segnale di selezione passato al demultiplexer indica quale dei dati entra nella rete.

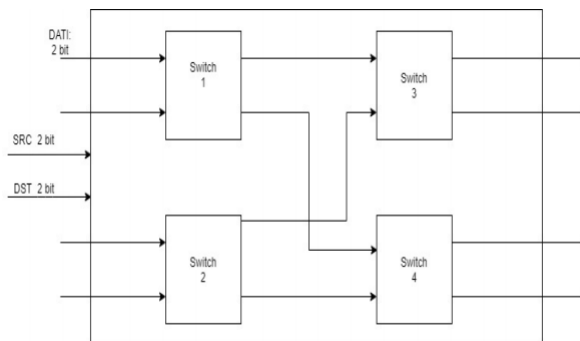

 La parte operativa è formata dalla rete e prende in ingresso i 2 bit di dati, sorgente e destinazione. Questi ultimi servono allo switch per scegliere una delle due direzioni di uscita.




Gli switch sono composti da un multiplexer e un demultiplexer collegati tra loro e i cui segnali di selezione corrispondono al primo o al secondo bit di SRC e DST a seconda del livello a cui si trova il pacchetto. Ad esempio se avessimo SRC = '00' e DST = '01' il multiplexer dello switch selezionerà i dati provenienti dalla prima linea di input (SRC(0) = 0) e il demultiplexer li porrà


in uscita sulla prima porta di output ( $DST(1) = 1$ ). Dallo switch1, quindi, passiamo allo switch3 e quest'ultimo selezionerà la seconda uscita ( $DST(0) = '0'$ ) consegnando il dato alla destinazione '01'.
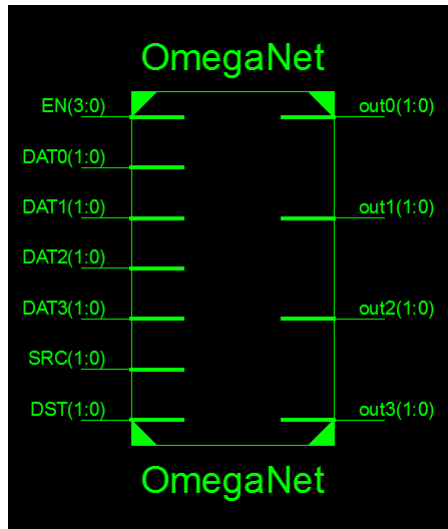
### 13.2.1 Schematici

Come descritto, un ingresso enable da 4 bit, 4 linee dati da 2 bit, sorgente e destinazione e 4 linee dati di uscita.




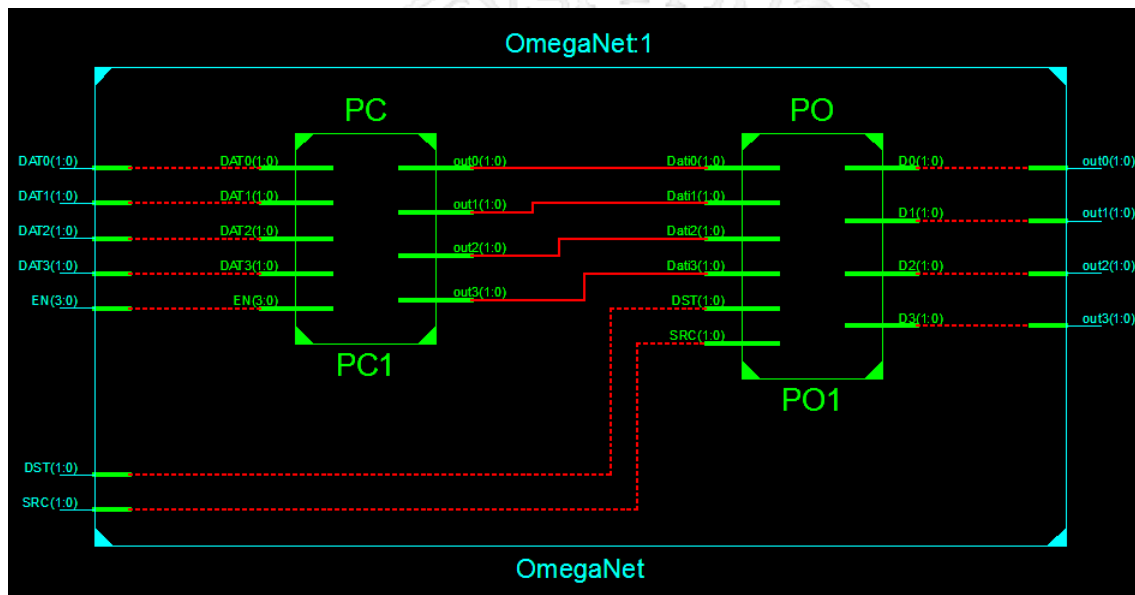La parte di controllo è direttamente collegata con la parte operativa:




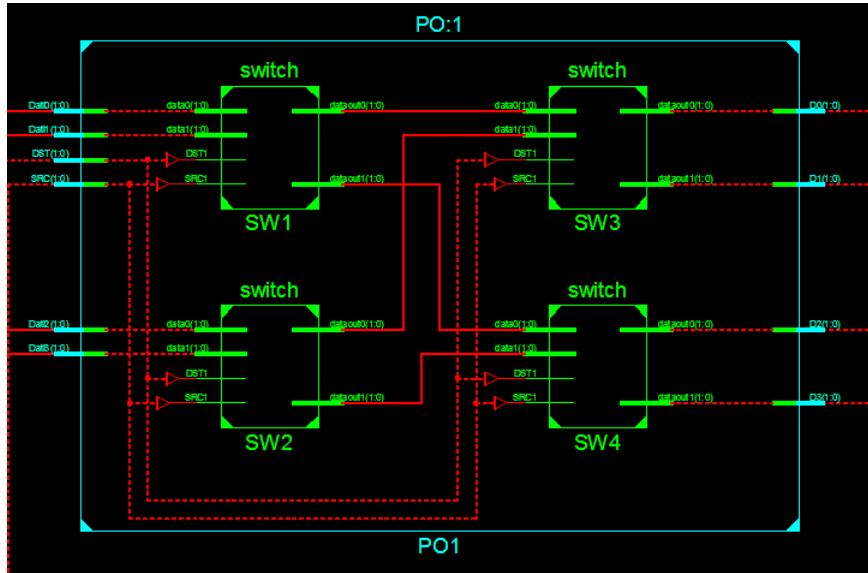La parte di controllo è costituita da 4 switch per i percorsi dei dati:





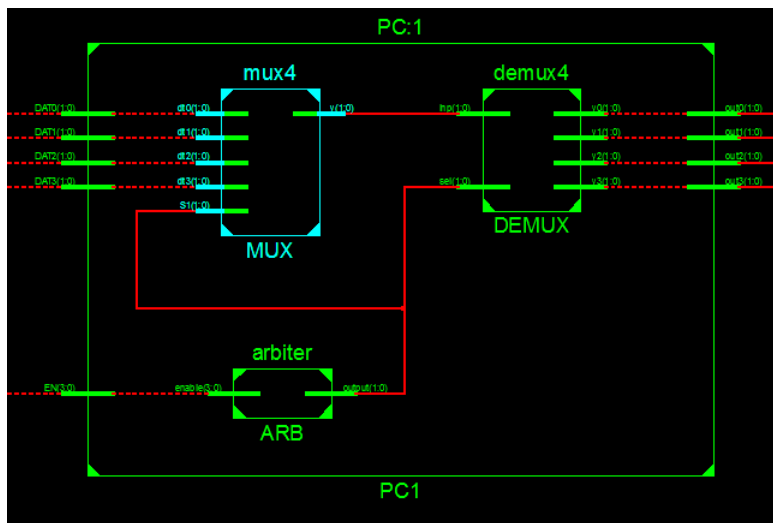Parte di controllo costituita da un mux, un demux e un arbitro:



### 13.2.2 Codice

Il tutto è stato implementato con una logica di tipo strutturale. Parte operativa e parte di controllo sono racchiuse in OmegaNetwork che prende in ingresso le 4 linee di dati, il segnale di abilitazione EN, sorgente e destinazione. In uscita vi è il dato che attraversa la rete. Sono stati definiti i componenti PC e PO e le uscite del demultiplexer del PC sono collegate agli ingressi dati del PO. Come già detto gli switch sono composti da un multiplexer 2:1 e un demultiplexer 1:2 e i segnali di selezione sono i bit di SRC e DST. Il demultiplexer pone il segnale in ingresso su una delle due uscite in base al valore di SEL.

#### 13.2.2.1 OmegaNetwork

```

2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4
5 entity OmegaNet is
6
7 port (
8
9     EN: in std_logic_vector(3 downto 0);
10    DAT0,DAT1,DAT2,DAT3: in std_logic_vector (1 downto 0);
11    out0,out1,out2,out3: out std_logic_vector (1 downto 0);
12    SRC, DST: in std_logic_vector(1 downto 0)
13
14 );
15
16
17 end OmegaNet;
18
19 architecture Structural of OmegaNet is
20
21 Component PC
22 port (
23
24     EN: in std_logic_vector(3 downto 0);
25     DAT0,DAT1,DAT2,DAT3: in std_logic_vector (1 downto 0);
26     out0,out1,out2,out3: out std_logic_vector (1 downto 0)
27
28 );
29 end component;
30
31
32 Component PO is
33 port (
34     Dati0,Dati1,Dati2,Dati3 : in std_logic_vector(1 downto 0);
35     SRC, DST: in std_logic_vector(1 downto 0);
36     D0,D1,D2,D3 : out std_logic_vector(1 downto 0)
37
38 );
39 end component;
40
41
42 signal t_out0,t_out1,t_out2,t_out3: std_logic_vector (1 downto 0);
43
44 begin
45
46 PC1: PC port map(
47
48     EN=>EN,
49     DAT0=> DAT0,
50     DAT1=>DAT1,

```

```

51  DAT2=>DAT2,
52  DAT3=>DAT3,
53  out0 => t_out0,
54  out1 => t_out1,
55  out2 => t_out2,
56  out3 => t_out3
57
58 );
59
60 PO1: PO port map(
61
62   Dati0 => t_out0,
63   Dati1 => t_out1,
64   Dati2 => t_out2,
65   Dati3 => t_out3,
66   SRC => SRC,
67   DST => DST,
68   D0 => out0,
69   D1 => out1,
70   D2 => out2,
71   D3 => out3
72
73 );
74
75
76
77 end Structural;

```

Codice Componente 13.1: Definizione del componente OmegaNetwork

### 13.2.2.2 PO (Parte Operativa)

```

1
2
3  library IEEE;
4  use IEEE.STD_LOGIC_1164.ALL;
5
6
7
8  entity PO is
9  port (
10     Dati0,Dati1,Dati2,Dati3 : in std_logic_vector(1 downto 0);
11     SRC, DST: in std_logic_vector(1 downto 0);
12     D0,D1,D2,D3 : out std_logic_vector(1 downto 0)
13
14 );
15 end PO;
16

```

```
17 architecture STRUCTURAL of PO is
18
19 Component switch
20 port (
21     data0,data1: in std_logic_vector(1 downto 0);
22     SRC1, DST1: in std_logic;
23     dataout0,dataout1: out std_logic_vector(1 downto 0)
24 );
25 end component;
26
27 signal t0,t1,t2,t3: std_logic_vector(1 downto 0) :=(others=>'0');
28
29 begin
30
31
32 SW1: switch port map(
33
34     data0=> Dati0,
35     data1=> Dati1,
36     SRC1=> SRC(0),
37     DST1=> DST(1),
38     dataout0=> t0,
39     dataout1=>t1
40
41 );
42
43 SW2: switch port map(
44
45     data0=> Dati2,
46     data1=> Dati3,
47     SRC1=> SRC(0),
48     DST1=> DST(1),
49     dataout0=> t2,
50     dataout1=>t3
51
52 );
53
54
55 SW3: switch port map(
56
57     data0=> t0,
58     data1=> t2,
59     SRC1=> SRC(1),
60     DST1=> DST(0),
61     dataout0=> D0,
62     dataout1=>D1
63
64
65 );
```

```

66
67
68 SW4: switch port map(
69
70     data0=> t1,
71     data1=> t3,
72     SRC1=> SRC(1),
73     DST1=> DST(0),
74     dataout0=> D2,
75     dataout1=>D3
76
77 );
78
79 end STRUCTURAL;

```

Codice Componente 13.2: Definizione del componente PO

### 13.2.2.3 Switch

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4
5 entity switch is
6 port (
7     data0,data1: in std_logic_vector(1 downto 0);
8     SRC1, DST1: in std_logic;
9     dataout0,dataout1: out std_logic_vector(1 downto 0)
10 );
11 end switch;
12
13 architecture structural of switch is
14
15 Component MUX2
16     PORT (
17         s0 : in std_logic;
18         a0,b0: in std_logic_vector(1 downto 0);
19         y : out std_logic_vector(1 downto 0)
20     );
21 end component;
22
23 Component DEMUX2
24     PORT (
25         X : in std_logic_vector(1 downto 0);
26         s1 : in std_logic;
27         A1,A2: out std_logic_vector(1 downto 0)
28     );
29 end component;

```

```

30
31 signal t: std_logic_vector(1 downto 0) :=(others=>'0');
32
33 begin
34
35 MUX_1: mux2 port map(
36     s0=>SRC1,
37     a0=>data0,
38     b0=>data1,
39     y=>t
40
41 );
42
43 DEMUX_1: demux2 port map(
44
45     X=>t,
46     s1=>DST1,
47     A1=>dataout0,
48     A2=>dataout1
49
50 );
51
52 end structural;

```

Codice Componente 13.3: Definizione del componente Switch

#### 13.2.2.4 Demultiplexer 1:2

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4
5 entity DEMUX2 is
6     PORT (
7         X : in  std_logic_vector(1 downto 0);
8         s1 : in  std_logic;
9         A1,A2: out std_logic_vector(1 downto 0)
10    );
11 end DEMUX2;
12
13 architecture dataflow of DEMUX2 is
14
15 begin
16
17 A1<= X when s1='0' else "--";
18 A2<= X when s1='1' else "--";
19
20 end dataflow;

```

## Codice Componente 13.4: Definizione del componente Demux 1:2

## 13.2.2.5 PC (Parte di Controllo)

```
1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4
5 entity PC is
6
7 port (
8     EN: in std_logic_vector(3 downto 0);
9     DAT0,DAT1,DAT2,DAT3: in std_logic_vector (1 downto 0);
10    out0,out1,out2,out3: out std_logic_vector (1 downto 0)
11 );
12
13
14 end PC;
15
16 architecture structural of PC is
17
18 Component arbiter
19 port (
20     enable: in STD_LOGIC_VECTOR(3 downto 0);
21     output: out STD_LOGIC_VECTOR(1 downto 0)
22 );
23
24 end component;
25
26 Component mux4
27 port (
28     S1 : in std_logic_vector(1 downto 0);
29     dt0,dt1,dt2,dt3 : in std_logic_vector(1 downto 0);
30     y : out std_logic_vector(1 downto 0)
31 );
32
33 end component;
34
35 Component demux4
36 port (
37     inp, sel: in std_logic_vector(1 downto 0);
38     y0,y1,y2,y3: out std_logic_vector(1 downto 0)
39 );
40
41 end component;
42
43 signal f1, t1: std_logic_vector(1 downto 0);
```

```
44 begin
45
46
47 MUX: mux4 port map (
48
49     S1=>f1,
50     dt0=> DAT0,
51     dt1=>DAT1,
52     dt2=>DAT2,
53     dt3=>DAT3,
54     y=>t1
55
56
57 );
58
59
60 DEMUX: demux4 port map (
61     inp=>t1,
62     sel=>f1,
63     y0=>out0,
64     y1=>out1,
65     y2=>out2,
66     y3=>out3
67
68 );
69
70 ARB: arbiter port map (
71
72     enable=>EN,
73     output=>f1
74
75 );
76
77
78
79 end structural;
```

Codice Componente 13.5: Definizione del componente PC

#### 13.2.2.6 Arbiter

```
1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4
5 entity arbiter is
6 port (
7     enable: in STD_LOGIC_VECTOR(3 downto 0);
```



```

8      output: out STD_LOGIC_VECTOR(1 downto 0));
9
10 end arbiter;
11
12 architecture dataflow of arbiter is
13
14 begin
15
16 output <=      "00" when enable(3) = '1' else
17      "01" when (enable(3) = '0' and enable(2)='1') else
18      "10" when (enable(3) = '0' and enable(2)='0' and enable(1)='1') else
19      "11" when (enable(3) = '0' and enable(2)='0' and enable(1)='0' and
20      enable(0)='1') else
21      "--";
22 end dataflow;

```

Codice Componente 13.6: Definizione del componente Arbiter

### 13.2.2.7 Demultiplexer 1:4

```

1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4
5 entity demux4 is
6 port (
7     inp, sel: in std_logic_vector(1 downto 0);
8     y0,y1,y2,y3: out std_logic_vector(1 downto 0)
9 );
10
11 end demux4;
12
13 architecture dataflow of demux4 is
14
15 begin
16
17 y0<= inp when sel="00" else (others=>' ');
18 y1<= inp when sel="01" else (others=>' ');
19 y2<= inp when sel="10" else (others=>' ');
20 y3<= inp when sel="11" else (others=>' ');
21
22 end dataflow;
23

```

Codice Componente 13.7: Definizione del componente Demux 1:4

## 13.3 Simulazione

I test sono stati effettuati secondo i valori presenti nella tabella sottostante (a sinistra gli input e a destra gli output attesi).

EN	D0	D1	D2	D3	SRC	DST	OUT0	OUT1	OUT2	OUT3
1000	01	11	10	11	00	10	–	–	01	–
1000	11	11	10	11	00	10	–	–	11	–
0100	00	01	10	11	01	00	01	–	–	–
0001	00	01	10	11	11	01	–	11	–	–
1100	11	00	10	01	00	10	–	–	11	–

### 13.3.1 Codice

Viene mostrato il codice per un singolo caso di test. Per tutti gli altri si modificano i valori nello `stim_process`.

```

1
2
3  LIBRARY ieee;
4  USE ieee.std_logic_1164.ALL;
5
6  -- Uncomment the following library declaration if using
7  -- arithmetic functions with Signed or Unsigned values
8  --USE ieee.numeric_std.ALL;
9
10 ENTITY test_omega IS
11 END test_omega;
12
13 ARCHITECTURE behavior OF test_omega IS
14
15     COMPONENT OmegaNet
16     PORT (
17         EN : IN  std_logic_vector(3 downto 0);
18         DAT0 : IN  std_logic_vector(1 downto 0);
19         DAT1 : IN  std_logic_vector(1 downto 0);
20         DAT2 : IN  std_logic_vector(1 downto 0);
21         DAT3 : IN  std_logic_vector(1 downto 0);
22         out0 : OUT std_logic_vector(1 downto 0);
23         out1 : OUT std_logic_vector(1 downto 0);
24         out2 : OUT std_logic_vector(1 downto 0);
25         out3 : OUT std_logic_vector(1 downto 0);
26         SRC : IN  std_logic_vector(1 downto 0);
27         DST : IN  std_logic_vector(1 downto 0)
28     );
29     END COMPONENT;
30
31
32

```

```

33  --Inputs
34  signal EN : std_logic_vector(3 downto 0) := (others => '0');
35  signal DAT0 : std_logic_vector(1 downto 0) := (others => '0');
36  signal DAT1 : std_logic_vector(1 downto 0) := (others => '0');
37  signal DAT2 : std_logic_vector(1 downto 0) := (others => '0');
38  signal DAT3 : std_logic_vector(1 downto 0) := (others => '0');
39  signal SRC : std_logic_vector(1 downto 0) := (others => '0');
40  signal DST : std_logic_vector(1 downto 0) := (others => '0');
41
42  --Outputs
43  signal out0 : std_logic_vector(1 downto 0);
44  signal out1 : std_logic_vector(1 downto 0);
45  signal out2 : std_logic_vector(1 downto 0);
46  signal out3 : std_logic_vector(1 downto 0);
47
48
49  BEGIN
50
51  -- Instantiate the Unit Under Test (UUT)
52  uut: OmegaNet PORT MAP (
53      EN => EN,
54      DAT0 => DAT0,
55      DAT1 => DAT1,
56      DAT2 => DAT2,
57      DAT3 => DAT3,
58      out0 => out0,
59      out1 => out1,
60      out2 => out2,
61      out3 => out3,
62      SRC => SRC,
63      DST => DST
64  );
65
66
67  -- Stimulus process
68  stim_proc: process
69  begin
70      wait for 100 ns;
71
72      EN <= "1000";
73      DAT0 <= "01";
74      DAT1 <= "11";
75      DAT2 <= "10";
76      DAT3 <= "11";
77      SRC <= "00";
78      DST <= "10";
79
80
81      wait;

```

```


82   end process;
83
84   END;

```


Codice Componente 13.8: Definizione del testbench per OmegaNetwork

### 13.3.2 Risultati


Test 1 : L'output ottenuto corrisponde a quello atteso. L'informazione proveniente dal nodo 1 (00) viene consegnata correttamente al nodo 3 (10).

 


Test 2 : L'output ottenuto corrisponde a quello atteso. L'informazione proveniente dal nodo 1 (00) viene consegnata correttamente al nodo 3 (10).

 


Test 3 : Il dato viene consegnato dal secondo nodo al primo nodo.

 

Test 4 : Il dato viene consegnato al secondo nodo dal quarto nodo.

 

 Test 5 : La priorità viene rispettata e viene inviato il dato 11 (dat0) alla terza uscita out2.



## 13.4 Sintesi su board FPGA

Due componenti sono stati aggiunti alla OmegaNetwork per la sintesi su FPGA Nexys2 : il debouncer e il display a 7 segmenti per indicare l'input da inserire. Due process regolano il comportamento della macchina : uno per la macchina a stati finiti e uno per l'inserimento dei bit in input sulla corretta linea dati. Gli stati sono Enable, Source, Dest, Dati e Fine. Tutti questi stati regolano l'immissione dei dati tramite gli switch e il bottone Load in ingresso al debouncer (che ha uscita c1). Nello stato di Enable si inserisce il valore di ingresso dell'arbiter. Successivamente si passa allo stato di Source in cui si inserisce la sorgente del dato e così via con destinazione e dati. Lo stato di Fine permette di visualizzare sui led l'uscita della omega network.

```

1
2 entity FPGAOmega is
3 port (
4     clock_50MHz: in std_logic;
5     Load,reset: in std_logic;
6     SW:in std_logic_vector (3 downto 0);
7     LED: out std_logic_vector (7 downto 0):= (others=>'0');
8     Anode_Activate: out STD_LOGIC_VECTOR (3 downto 0);
9     LED_out : out STD_LOGIC_VECTOR (6 downto 0)
10 );
11 end FPGAOmega;
12
13
14 architecture Behavioural of FPGAOmega is
15
16
17 signal t0,t1,t2,t3,s0,s1,s2,s3: std_logic_vector (1 downto 0):= (others
    =>'0');

```

```

18 signal c1: std_logic:='0';
19 signal O1,O2,O3,O4 :std_logic_vector (3 downto 0):= (others=>'0');
20 signal st :std_logic_vector (15 downto 0):= (others=>'0');
21
22
23 type State_type is (En,Source,Dest,Dati,Fine);
24 signal State: State_type:= En;
25
26 Component OmegaNet is
27 port (
28
29     EN: in std_logic_vector(3 downto 0);
30     DAT0,DAT1,DAT2,DAT3: in std_logic_vector (1 downto 0);
31     out0,out1,out2,out3: out std_logic_vector (1 downto 0);
32     SRC, DST: in std_logic_vector(1 downto 0)
33
34 );
35 end Component;
36
37 Component debouncer is
38 port (
39     clock, reset: in std_logic;
40     data_in: in std_logic;
41     data_out: out std_logic
42
43 );
44 end Component;
45
46 Component SEV_SEG_DISP is
47 port (
48     clock_50Mhz : in STD_LOGIC;
49     reset : in STD_LOGIC;
50     X: in STD_LOGIC_VECTOR (15 downto 0);
51     Anode_Activate : out STD_LOGIC_VECTOR (3 downto 0);
52     LED_out : out STD_LOGIC_VECTOR (6 downto 0)
53
54 );
55
56 end Component;
57
58
59 begin
60
61 O: OmegaNet port map(
62     EN=>O1,
63     DAT0=>t0,
64     DAT1=>t1,

```

```

67     DAT2=>t2,
68     DAT3=>t3,
69     SRC(1)=> O2(1),
70     SRC(0)=>O2(0),
71     DST(1)=>O3(1),
72     DST(0)=>O3(0),
73     out0=>s0,
74     out1=>s1,
75     out2=>s2,
76     out3=>s3
77
78
79 );
80
81
82 DB: debouncer port map(
83     clock=>clock_50MHz,
84     reset=>reset,
85     data_in=>Load,
86     data_out=>c1
87
88
89 );
90
91 DISP:SEV_SEG_DISP port map(
92
93     clock_50MHz=>clock_50MHz,
94     reset=>reset,
95     X=>st,
96     Anode_Activate=>Anode_Activate,
97     LED_out=>LED_out
98
99 );
100
101 p: process(clock_50MHz)
102
103 begin
104
105 if (rising_edge(clock_50MHz)) then
106
107 if (O2="--00") then
108     t0(1)<=O4(1);
109     t0(0)<=O4(0);
110
111 elsif (O2="--01") then
112     t1(1)<=O4(1);
113     t1(0)<=O4(0);
114
115 elsif (O2="--10") then

```

```

116     t2(1)<=O4(1);
117     t2(0)<=O4(0);
118
119 elsif (O2="--11") then
120     t3(1)<=O4(1);
121     t3(0)<=O4(0);
122
123 end if;
124 end if;
125
126 end process;
127
128
129
130
131 p1:process(clock_50MHz)
132 begin
133
134
135 if (reset='1') then
136     State<=En;
137     O1<=(others=>'0');
138     O2<=(others=>'0');
139     O3<=(others=>'0');
140     O4<=(others=>'0');
141     LED<=(others=>'0');
142
143 elsif (rising_edge(clock_50MHz)) then
144
145 case State is
146
147     when En =>
148         --INSERIMENTO ENABLE
149         st<="1110100110101011"; --Sul display viene visualizzata la
150             scritta Enable
151         if (cl='1') then
152             O1 <= SW;
153             State<=Source;
154         end if;
155
156     when Source=>
157         --INSERIMENTO SORGENTE
158         st<="0101000001000110"; --Sul display viene visualizzata la
159             scritta SORG
160         if (cl='1') then
161             O2 <= SW;
162             State<=Dest;
163         end if;

```



```

163
164
165     when Dest=>
166         --INSERIMENTO DESTINAZIONE
167         st<="0000111001010011";      --Sul display viene visualizzata la
            scritta Dest
168         if (c1='1') then
169             O3 <= SW;
170             State<=Dati;
171         end if;
172
173
174     when Dati=>
175         --INSERIMENTO DATI
176         st<="0000101000110010";      --Sul display viene visualizzata la
            scritta Dati
177         if (c1='1') then
178             O4 <= SW;
179             State<=Fine;
180         end if;
181
182
183     when Fine=>
184         st<="1111001010011000";      --Sul display viene visualizzata la
            scritta Fine
185         LED<= s3 & s2 & s1 & s0;
186
187     end case;
188
189 end if;
190
191 end process;
192
193 end Behavioural;

```

Codice Componente 13.9: Definizione del componente FPGAOmega

### 13.4.1 File UCF

Il file UCF permette di mappare led, display, switch e bottoni per l'immissione degli input e la visualizzazione degli output.

```

1
2 NET "LED_out<6>" LOC = "L18"; # Bank = 1, Pin name = IO_L10P_1, Type = I/O,
   Sch name = CA
3 NET "LED_out<5>" LOC = "F18"; # Bank = 1, Pin name = IO_L19P_1, Type = I/O,
   Sch name = CB
4 NET "LED_out<4>" LOC = "D17"; # Bank = 1, Pin name = IO_L23P_1/HDC, Type =
   DUAL, Sch name = CC

```

```

5 NET "LED_out<3>" LOC = "D16"; # Bank = 1, Pin name = IO_L23N_1/LDC0, Type =
  DUAL, Sch name = CD
6 NET "LED_out<2>" LOC = "G14"; # Bank = 1, Pin name = IO_L20P_1, Type = I/O,
  Sch name = CE
7 NET "LED_out<1>" LOC = "J17"; # Bank = 1, Pin name = IO_L13P_1/A6/RHCLK4/
  IRDY1, Type = RHCLK/DUAL, Sch name = CF
8 NET "LED_out<0>" LOC = "H14"; # Bank = 1, Pin name = IO_L17P_1, Type = I/O,
  Sch name = CG
9 NET "clock_50Mhz" LOC = "B8"; # Bank = 0, Pin name = IP_L13P_0/GCLK8, Type
  = GCLK, Sch name = GCLK0
10 NET "Anode_Activate<0>" LOC = "F17"; # Bank = 1, Pin name = IO_L19N_1, Type
  = I/O, Sch name = AN0
11 NET "Anode_Activate<1>" LOC = "H17"; # Bank = 1, Pin name = IO_L16N_1/A0,
  Type = DUAL, Sch name = AN1
12 NET "Anode_Activate<2>" LOC = "C18"; # Bank = 1, Pin name = IO_L24P_1/LDC1,
  Type = DUAL, Sch name = AN2
13 NET "Anode_Activate<3>" LOC = "F15"; # Bank = 1, Pin name = IO_L21P_1, Type
  = I/O, Sch name = AN3
14
15
16 NET "SW<0>" LOC = "G18"; # Sch name = SW0
17 NET "SW<1>" LOC = "H18"; # Sch name = SW1
18 NET "SW<2>" LOC = "K18"; # Sch name = SW2
19 NET "SW<3>" LOC = "K17"; # Sch name = SW3
20
21 NET "Load" LOC = "B18";
22 NET "reset" LOC = "D18";
23
24
25 NET "LED<0>" LOC = "J14";
26 NET "LED<1>" LOC = "J15";
27 NET "LED<2>" LOC = "K15";
28 NET "LED<3>" LOC = "K14";
29 NET "LED<4>" LOC = "E16";
30 NET "LED<5>" LOC = "P16";
31 NET "LED<6>" LOC = "E4";
32 NET "LED<7>" LOC = "P4";

```

Codice Componente 13.10: Definizione del file UCF